

# Electronics Today



September 1984

\$2.95  
MM70924



Canada's Magazine for Electronics & Computing Enthusiasts


## Radio: What's Happening

- AM Stereo
- Shortwave and Computers
- Mediumwave
- Direct Broadcast Satellites

Audio Test Set



Offbeat Metronome

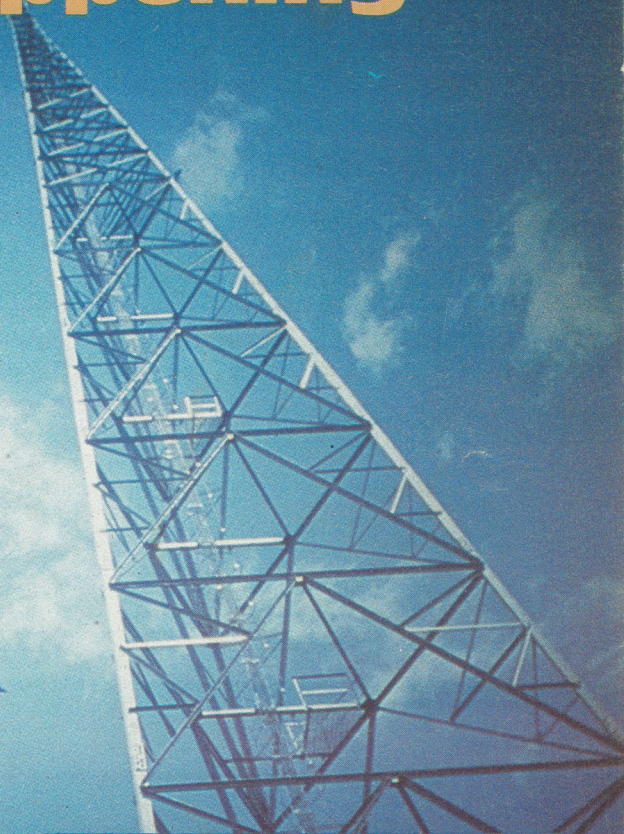

**Computer  
Review**  
IBM PCjr



**Join us in our 6th birthday celebration and take advantage of our Spectacular Specials. We now have 3 locations to serve you better!**

**TORONTO**  
319 College  
1(416)921-8941

**HAMILTON**  
72 James St. N.  
1(416)521-4124

**OTTAWA**  
217 Bank  
1(613)230-9000

Special prices available only til September 30th, 1984

### Super savings on

8" SSDD **\$79.00**  
Siemens drives  
(final sale, no returns)

### 5" Monitors Grn \$59

(Brand new open frame from Electrohome)  
KEPCO Heavy Duty

### Switching Power Supply

(90 watts max.)

115V or 220V provision filter and fuse on board, provides you with +5, +12, -12, gives you enough power to handle your system plus several drives with 3.8A on +12

Brand New **\$55.00**  
Buy 5 or more **\$49.00**  
Ideal for hard disk drives

### Packaged Power Supply with Fan

and hydro approved, 175 Watts

**Only \$149.00**

Provides +5, +12, -12 (Optional -5V)

### Peripherals for your Apple

120 Day Warranty

16K RAM Card ..... **\$54.95**  
Z80 Card ..... **\$52.00**  
Parallel Printer Card ..... **\$65.00**  
80 x 24 Video with soft switch card ..... **\$73.95**  
128K Card - 64K of RAM ..... **\$117.00**  
128K Card - 128K of RAM ..... **\$185.00**  
EPROM Programmer (with software) ..... **\$69.00**  
(programs 2716, 2732, 2764)  
Serial Card ..... **\$79.00**  
Modem Card ..... **\$199.00**

### Disk Drives for your Apple \$245

1 Year Warranty Special price  
Buy Two or More ..... **\$139**

### Maxiswitch Keyboard IBM Compatible Only \$159

### Cherry Keyboard \$169

ABS Case keyboard & numeric keypad ..... **\$139**  
Power Supply to Match ..... **\$69**  
Case, Numeric Keyboard & Supply ..... **\$199**

### 3" Drive for your Apple

to be released soon at an unbelievable low price!

### Systems

Apple IIc ..... **\$1549**  
Apple Macintosh from ..... **\$3195**

### 10 Meg Hard Disk Drive & Controller \$1498

which plugs right into your machine

### System Mate Fan \$85

### SYSTEM • MATE\*

PREVENT DOWNTIME, LOST DATA, CIRCUIT DAMAGE, SERVICING.

#### BENEFITS:

- Eliminates dangerous voltage transients, even those generated by LIGHTNING! — Reduced amp/hi.
- Quiet, efficient fan removes dangerous HEAT build up.
- Improves system reliability.
- Computer, monitor, printer are all controlled by ONE LIGHTED front switch.

THOUSANDS SOLD\*

MADE IN CANADA BY:  
CANADIAN COMPUTER DESIGNERS



## Peripherals for your IBM or IBM Compatible Computer our Peripheral Cards carry a 120 Day Warranty

### Floppy Controller Card

With serial port built-in and provision for real time clock ..... **\$189**

### Floppy Controller Card

With serial port and real time clock and clock software ..... **\$219**

### Peripheral Board

With 2 serial ports, 1 parallel port, 1 game port (provision for optional real time clock) **\$169**. With all above options including the real time clock ..... **\$199**

### Colour Video Board

512 Memory Board with 64K of RAM ..... **\$179**

512 Memory with 128K ..... **\$250**

512 Memory with 256K ..... **\$399**

512 Loaded Memory with 512K ..... **\$659**

### Expansion Board

includes serial port, parallel port, game port, up to 256K of RAM and a real time clock, all of the above with 64K of RAM ..... **\$289**

With 128K ..... **\$359**

With 256K ..... **\$499**

### Brand new from Shugart SA455 D.S.D.D.

Disk Drive slim line, ideal for IBM or compatible computer ..... **\$249**

6809 Board as described in May '84 Catalogue with 48K ..... **\$389**

**EPROM Programmer** + Software (programs 2716, 2732, 2764, 27128) with ordinary sockets ..... **\$99** With two ZIF Sockets ..... **\$149**

Extension Board & Cable with two sockets (this card allows you to be able to have the ZIF sockets beside your computer for easy access.

Parallel Card & Game Port ..... **\$49**

### Navy — soon to be released

### 512 Bubble Memory Card

At a knockout low price! 300/1200 baud auto dial/ answer, direct connect modem, newest technology, price so low that you'll be sorry if you don't wait for it.

### Multiflex Z80A Starter Kit

As described in May '84 Catalogue pg. 16 ..... **\$289**

### Monitors

Zenith 122 Amber 12" ..... **\$139**  
Zenith 123 Green 12" ..... **\$129**

### Printers

Gemini 10X ..... **\$379**  
Panasonic Printers now available at a bargain price.  
TTX (Daisy Wheel) Letter quality ..... **\$599**  
Epson FX100 ..... **\$1069**

### Diskettes

CDC, S.S.D.D. 10 disks for ..... **\$21.95**  
Acutrack S.S.D.D. 10 disks w. plastic case ..... **\$26.00**  
Verbatim S.S.D.D. 10 disks for ..... **\$32.95**  
**Paper** 500 sheets ..... **\$9.95**

We have a huge selection of parts, check out our May '84 catalogue. Here are a few examples:

### Memories

4116 150 ps ..... **\$1.95**  
4164 150 ps ..... **\$8.49**  
4164 TI 150 NS (ideal for IBM Compatibles) ..... **\$7.95**  
2114 ..... **\$2.99**  
6116 150 NS ..... **\$8.95**  
6514 ..... **\$2.99**  
2716 350 NS ..... **\$8.50**  
2716 450 NS ..... **\$6.50**  
2732 450 NS ..... **\$8.95**  
2764 300 NS ..... **\$12.95**  
27128 300 NS ..... **\$49.00**  
DIN Connectors ..... **\$1.25**  
Most XTALS ..... **\$4.50**  
8088 ..... **\$32.95**  
8253A-5 Intel ..... **\$19.50**  
8253A-5 NEC ..... **\$11.95**  
8259A Intel ..... **\$12.95**  
8259A NEC ..... **\$11.50**  
8237A-5 ..... **\$43.95**

8250 ..... **\$14.95**  
8255A-5 Intel ..... **\$14.95**  
8255A-5 Other brand ..... **\$7.95**  
8284 Intel ..... **\$14.30**  
8284 Siemens ..... **\$7.95**  
8288 ..... **\$27.95**  
Delay Line 100 nano sec ..... **\$7.49**  
Z80A CPU ..... **\$5.50**  
6502 CPU ..... **\$6.50**  
6845 ..... **\$11.95**

Zenith 133 monitor RGB colour ..... **\$749.00**  
Gemini 15X Printer ..... **\$599.00**  
The Basic Best ..... **\$1795.00**  
The Loaded Best ..... **\$2395.00**  
The Executive Best ..... **\$3895.00**

**IBM is a registered trademark of International Business Machines Apple is a registered trademark of Apple Canada**  
After 7 days No Refund, No Exchange.



**Exceltronix Computer Division Computers at unbeatable prices! (416) 921-8941, 319 College St., Toronto, Ontario**

# EXCELTRONIX

No returns or exchanges after 7 days. 15% restocking charge.

Telex 065-24218 1-800-268-3798 — Order line only

**M5T 152**



# SURPLUSTRONICS

we will not be undersold

(416) 960-1350

## GIVE AWAY PRICES!!

Consider  
yourself  
a winner  
if you  
buy now

NOTE

We must clear out a large inventory of merchandise before our (Sept. 30, 1984) Fiscal year end. Therefore we urge you to take advantage of this one time sale. Prices are so low that we doubt you can build it cheaper yourself.

Due to the popular demand of our customers, we will now give you a choice between buying goods with a 120-day warranty, or you can buy the same quality goods without warranties as final sale, and SAVE MONEY! If any of the goods without warranty fail, we will be glad to fix them for you, but at your cost.

DON'T  
MISS  
IT

All goods listed on this page are manufactured using only prime, high quality components and PC Boards, all PC Board products are wave soldered, ultrasonically cleaned, and finished goods are thoroughly tested.

## ALL PRICES ON THIS PAGE ARE FINAL SALE PRICES! NO WARRANTY

Should you wish to have a 120 day warranty, all you have to do is ask, and pay a bit more; it is available for almost everything we advertise here.

### Peripherals for Apple™ Assembled & fully tested FINAL SALE!

16K RAM card . . . . .	\$49.95	touch tone or pulse dial • com-
Z80A Card . . . . .	\$47.00	patible with MODEM sold by our
80 x 24 card (with built-in soft		competitors for over \$220.
switch) . . . . .	\$73.95	
Parallel printer card . . . . .	\$49.95	<b>OUR PRICE . . . . . \$169.00</b>
128K card with 64K RAM . . . . .	\$109.00	If someone can sell it cheaper to
128K card with 128K RAM . . . . .	\$169.00	you, buy it!
EPROM Programmer		
(with software) . . . . .	\$65.95	Apple Compatible disk drives (bas-
Serial card . . . . .	\$59.00	ed on the Shugart SA390 disk drive
Floppy controller (controls 2-5 1/4"		mechanism . . . . . \$229.
SS/SD floppies . . . . .	\$44.95	Case & Numeric
8" Floppy controller . . . . .	\$109.00	keyboard . . . . . \$129.
6 MHz Z80 with 64K RAM		Power Supply (6502)
on board . . . . .	\$139.95	(Hydro approved) . . . . . \$69.
Prototyping Card . . . . .	\$15.00	

#### MODEM

**\$169.00**

Apple II & IIe compatible • power supply (defective) fix it  
Full/half duplex autodial/answer • yourself . . . . . \$29.95

#### SYSTEMS:

### FAMOUS KEYBOARD WITH 6502 SYSTEM \$499.00

Keyboard with numeric keypad includes ABS case, great power supply, 64K of RAM, floppy controller, 80 x 24 video board with a built-in softswitch (comes with blank EPROMS and no proprietary software). Fully tested and professionally assembled

#### 6502 Board

Packaged in 8088 case with provision for two SA390 disk drives. Includes: 64K RAM, 80 x 24 video with softswitch, floppy controller, powerful (90 W mx) power supply (enough power to handle up to four drives), along with a built-in fan for ventilation of system, serial to parallel keyboard adaptor, and Maxiswitch keyboard.

DON'T  
MISS  
IT

**ALL THIS FOR ONLY \$699.00**  
**Above system with one drive \$899.00**

#### 8088 Systems

Attractive case, power supply, fan and provision for 256K 8088 Board with 64K (fully tested). One blank 2764 (No proprietary software included). Maxiswitch or Cherry keyboard.

**All this for an Unthinkable Price of \$949.00**

### Panasonic Printers SPECIAL \$379.00

After 7 days no refund, no exchange! \*Price subject to change

### Peripherals for IBM™ or compatibles Assembled & fully tested FINAL SALE!

**Note: Read the above definition of final sale.**

#### Colour Video board

Compositor RGB . . . . . \$179.00

#### Floppy controller

(Handles up to 4-5 1/4" DS/DD IBM compatible disk drives)  
Provision for clock & serial port (not included) . . . . . \$139.95

**Floppy controller** as described above with RS232 Interface . . . . . \$159.95

**Floppy controller** (as described above) with RS232 & real time clock . . . . . \$189.95

#### EPROM programmer

Normal sockets . . . . . \$79.95  
2 ZIF sockets . . . . . \$99.95  
(Programs EPROMS from 2716 thru to 27128 software included.

#### Parallel port & game port card . . . . . \$69.95

Peripheral card . . . . . \$149.00  
Includes 2 serial ports, 1 parallel port, game port (optional real time clock).

Optional real time clock and software . . . . . \$29.00

#### Loaded peripheral card

with all (serial ports, parallel port, game port) on-board & real time clock software . . . . . \$176.00

#### 512 Memory board with:

64K RAM on board . . . . . \$179.00  
256K RAM on board . . . . . \$365.00  
512K RAM on board . . . . . \$599.00

**256K RAM card** with only 64K of RAM on board, parallel port, serial port, game port, and optional real time clock . . . . . \$189.00

**IBM compatible disk drives** (brand new fresh from factory) SA455 Shugart 40 Track DSDD Slimline (we ordered 10,000 from Shugart, that is why we pass the savings to you!) . . . . . \$239.95

**IBM compatible keyboards** (brand new) Maxiswitch (IBM compatible) Extra Special . . . \$149.00

**Cherry IBM compatible** Keyboard Super Special \$159.00

High quality cases for your 8080 . . . . . \$59.00

IBM is a registered Trade Mark of IBM Canada  
Apple is a registered Trade Mark of Apple

**Telex No.**  
**065-24218**

Mail Orders add \$5.00 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard and American Express cards accepted: send card number, expiry data, name of bank and signature. Send certified cheque or money order, do not send cash.

Circle No. 29 on Reader Service Card  
More lines to serve you better  
**(416) 960-1350**

**Surplustronics, 310 College Street, Toronto, Ontario, M5T 1S3**





# Electro-Tech


Call Our Toll Free Hot-Line 1-800-263-9245

To receive our monthly mailing list send \$1.50 with your name and address.

MEGURO  
ELECTRONICS  
CORPORATION

2 Years  
Warranty!

NEW

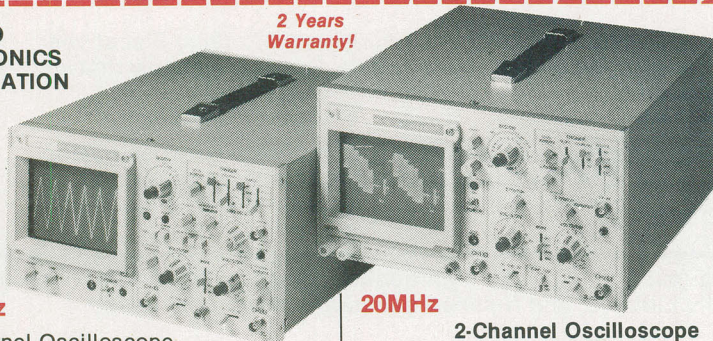

35MHz

2-Channel Oscilloscope  
MO-1252

Only \$889.95 FST + Probes Incl.!!

- Dual Trace 35 MHz
- Trigger Delay
- 5 KV Acceleration Voltage
- Hold off & Trace Rotation
- Single Sweep Function
- 1 mV/div. Sensitivity
- 20 nS/div. Sweep Speed

20MHz

2-Channel Oscilloscope  
MO-1251

Only \$689.95  
FST + Probes Incl.!!

- Dual Trace 20 MHz
- 1mV/Div. Sensitivity
- 20nS/Div. Sweep Speed
- H.V. Measurements to 600 V. Peak to Peak
- PLUS at no extra cost — Unique component Tester!

## Complete Electronic Supply

### Super Special!!

#### COMMODORE 64 PROGRAMMER'S REFERENCE GUIDE

A creative programmer's working tool and reference source, packed with professional tips and special information. Includes a complete, detailed dictionary of all Commodore BASIC commands, statements, and functions, followed by BASIC program samples showing how each item works. Also tells you how to mix machine language with BASIC, use hi-res effectively, and much more. Commodore Computer

Only \$19.95!!

(Reg. \$29.95)

While Quantities Last!

#### 5 1/4' DISKETTE FILE

- Stores 50 diskettes
- Library Index Divider
- Woodgrain & Cover

Only \$19.95

#### LENLINE SOLID STATE SPIKE PROTECTORS 40-400

Only \$7.95

HIOKI



#### 3212 Digital Hi Tester

- Auto Ranging
- 3 1/2 digit LCD
- Overload protection
- Low battery indicator
- High current capability
- Continuity test




#### 3102 Clamp-On Hi Tester

- Drop proof
- For both 50 & 60 MHz
- Ohmeter circuit tested to 250 V overvoltage
- Convenient meter lock
- Includes carrying case

Your choice Only \$79.95 plus F.S.T.
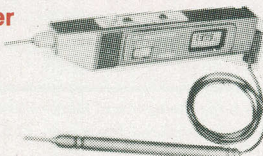
#### 3211 Pencil Hi Tester


- Auto Ranging
- "Hold" display feature
- Continuity test
- Overload protection
- Low battery indicator



### AP PRODUCTS INCORPORATED
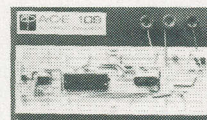
#### ACE 109 \$29.95

This is our newest and lowest priced ACE breadboard. It is ideal for designing, testing and modifying small circuits. The universal matrix of 840 solderless plug-in tie-points consists of 128 separate 5-tie-point terminals and 8 separate distribution buses of 25 tie-points



each. Buses can be used for power, ground, and signal lines and more.


#### JUMPER WIRES

EVERYTHING YOU NEED  
FOR QUICK, NEAT CIRCUIT  
CONNECTIONS

\$19.95
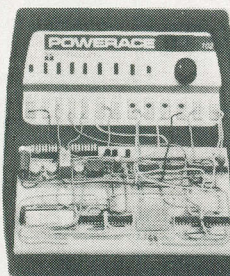
#923351

Kit contains 350 pieces cut to 14 different lengths packed in a compartment plastic box




Only \$189.95

- Regulated power supply
- Pulse detection with memory
- Three logic indicator
- Two logic switches
- Four data switches
- Clock generator
- One-shot pulse generator
- 1680 plug-in tie points
- Up to 18 14-pin DIPs
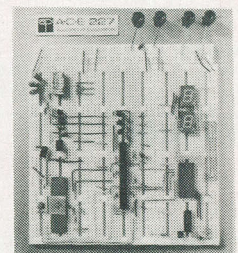
#### POWERACE 102

923102 120 VAC  
923222 220 VAC

A Complete Digital Prototyping Lab with a Built-in Pulse Detector




ACE 227 \$95.95

Universal Matrix 2712, tie-points, plus more!!

...Full line of interconnection products and Accessories, test clips, tie-point blocks, DIP jumpers, Edge cards, headers, etc...

MOVIT  
Do-It-Yourself Educational Kits!

#### AVOIDER MV912K

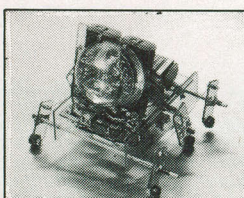


- 6 Leg movement
- Infra-red Sensor

An Intelligent Robot which knows how to avoid hitting walls. This robot emits an infra-red beam which detects obstacles.

\$69.95  
(kit)

#### MONKEY MV-919K

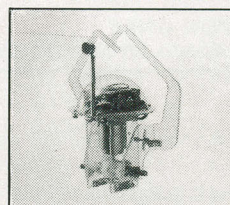

- Two Gripper Arms
- Sound Sensor

Order your "MONKEY" to move with a loud voice or clap of hands and the robot starts romping along a rope and stops by itself!!

Memocon Crawler ..... \$119.95  
Line Tracer ..... \$64.95  
Turnbacker ..... \$59.95  
Piper Mouse ..... \$69.95  
Sound Skipper ..... \$39.95

\$39.99 (kit)

MAIL ORDERS: add \$3.00 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard accepted: Send card number, expiry date, name of bank and signature. Send certified cheque or money order, do not send cash.

Electro-Tech 319 Nash Rd. N., Hamilton, Ontario L8H 7P4 (416)560-2283



# Electronics Today



Audit Bureau  
of Circulation


September 1984

INTERNATIONAL


Vol. 8. No. 9 ISSN 07038984



10

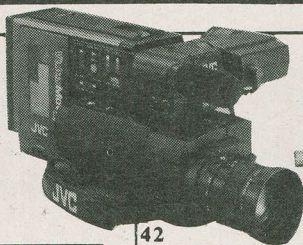

42

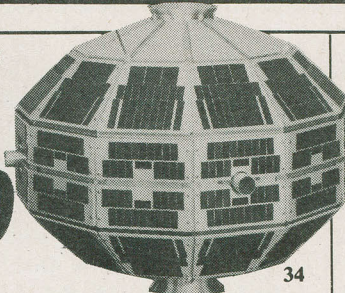

34

## Features

10

**What's Happening In Shortwave**  
Shortwave hasn't gone away.

14

**Audio Recording Technology**  
How your audio gets onto tape.

18

**AM Stereo Update,**  
Almost like FM!

26

**Computer Review: IBM PCjr**  
Bill Markwick tests the PC's little brother.

30

**Hot Ice**  
Roger Allan probes into what's going on in the world of remote sensing of ice floes.

33

**DX: The Dying Hobby**  
Listen to the world on an AM radio.

34

**Direct Broadcasting Satellites**  
Roger Allan reports on high-powered satellites.

42

**Electronics in Action**  
More hi-tech widgets and gadgets.

55

**Computing Today!**  
Yin Pun sheds some light on ProDos: Apple's new disk operating system.

57

**Designer's Notebook**  
VMOS circuits. Give 'em a try.

62

**Machine Code Programming, Part 4**  
Addressing and how it works.

67

**Circuit Ideas**  
Suggestions for the advanced experimenter.

## Projects

19

**Audio Test Set**  
Condense your bench with this amp/generator.

45

**Offbeat Metronome**  
Accent the beat, beat the accent.

## Columns, News and Information

For Your Information	7
Binders	23
Next Month	23
ETI Bookshelf	49
Order Form	53
Subscriptions	54
Book of the Month	54
Product Mart	69

## Our Cover

A new computerized Sony shortwave receiver is dwarfed by an RCA radio of yesteryear. The IBM PCjr is reviewed on page 26. Photos by Bill Markwick.

### Electronics Today is Published by:

**Moorshead Publications**  
Editorial and Advertising Offices  
Suite 601, 25 Overlea Boulevard,  
Toronto, Ontario, M4H 1B1  
Telephone (416) 423-3262

Editor:  
Editorial Assistant:  
Director of Production:  
Creative Manager:  
Production:

**William Markwick**  
**Edward Zapletal**  
**Erik Blomkwist**  
**Ann Rodrigues**  
**Douglas Goddard**  
**Neville Williams**  
**Naznin Sunderji**  
**Lisa Salvatori**  
**Omar Vogt**  
**Rick May**  
**Claire Zyvitski**  
Advertising (Que.): **John McGowan & Associates**  
(514)735-5191

Circulation Manager:  
Advertising:

Advertising (Que.): **John McGowan & Associates**  
(514)735-5191

**Publisher:** H.W. Moorshead; **Executive Vice-President:** V.K. Marskell; **General Manager:** S. Harrison; **Controller:** B. Shankman; **Accounts:** P. Dunphy; **Reader Service:** C. Wyatt, S. Halladay, H. Brooks, K. Adams; **Advertising Services:** D. Whitehead; **Dealer Services:** A. Nagels.

**Newsstand Distribution:**  
Master Media, Oakville, Ontario

**Subscriptions**  
\$19.95 (one year), \$34.95 (two years). For US add \$3.00 per year, other countries add \$5.00 per year. Please specify if subscription is new or a renewal.

**Postal Information**  
Second Class Mail Registration No. 3955. Mailing address for subscription orders, undeliverable copies and change of address notice is:  
Electronics Today International, Suite 601, 25 Overlea Blvd., Toronto, Ontario, M4H 1B1.

## Advertiser's Index

Active Components Sales Corp.	41
BCS Electronics Limited	7, 68
Brunelle Instruments Inc.	67
BTW Electronic Parts	61
Computer Mail Order	63
Computer Parts Galore Inc.	8, 9
Daetron	39
Duncan Instruments	12
Electronic Control Systems	44
Electrotech	4
Exceltronix	2
Infinite Canada Inc.	66
Kaientai Electronics Merchants Ltd.	61
Kitstronic International Ltd.	32
McGraw-Hill	29
Metermaster	71
Philips Test and Measure	11
Protec Microsystems Inc.	33
Smith Corona	6
Surplustronics	3
Sweet Electronics	39
Tektronic	72



# SMITH-CORONA JUST NARROWED YOUR CHOICE OF COMPUTER PRINTERS DOWN TO FIVE.

Introducing the personal computer printers you've been waiting for. From Smith-Corona.

Each one is remarkable. Each one affordable. Each one designed to meet very particular needs. Starting with the need for speed.

**They're fast workers.** Put words and numbers on paper at the crisp rate of 140 characters per second with the new Smith-Corona D-300 Dot Matrix Printer. Or as fast as 120 characters per second with the D-200 and D-100.

**Compatible partners.** The new Smith-Corona printers work perfectly with most major computers. Including IBM, Apple, Commodore and more. Four of these printers

feature a Dual Interface to ensure wide compatibility. The fifth, the Smith-Corona Fastex 80 Dot Matrix Printer, offers Parallel Interface.


**High quality printers.** As you can see, the new Smith-Coronas deliver outstanding results. Even at high speeds. **This Dot Matrix print out is as close to letter quality as you can get.** While the L-1000 Daisy Wheel model produces documents that satisfy your most critical needs. Naturally, since document

sizes vary, our paper capacity varies too. From standard 8½" computer paper to 15" widths. (And even smaller sizes when sheet-fed.)

**And a reliable investment, all down the line.** Because we're Smith-Corona, you get reliability and workmanship second to none. Our national service network is as near as your phone.

So why waste time? To get down to serious computing around your home or office, look into the new line of personal printers from Smith-Corona. Your choice will be easier than you think.

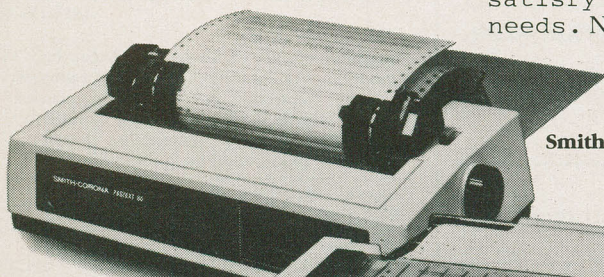
For more information about the full line of new Smith-Corona printers, call your nearest authorized Smith-Corona dealer. Or fill in and mail the coupon below.



Smith-Corona Fastex 80



Smith-Corona D-200

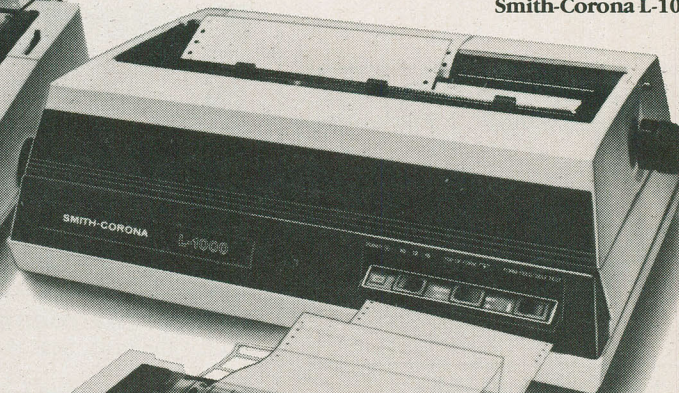

Smith-Corona L-1000



Smith-Corona D-300



Smith-Corona D-100

- ☐ Please send me more information about Smith-Corona printers for in-home use.
- ☐ Please send me more information about Smith-Corona printers for office use.

NAME: \_\_\_\_\_

COMPANY NAME: \_\_\_\_\_

BUSINESS ADDRESS: \_\_\_\_\_

CITY \_\_\_\_\_ PROV. \_\_\_\_\_ POSTAL CODE \_\_\_\_\_

TYPE OF BUSINESS \_\_\_\_\_

Send to: Bryce Buskard



**SMITH  
CORONA**

DIVISION OF SCM (CANADA) LIMITED  
29 GERRAIS DRIVE, DON MILLS, ONT.  
M3C 1Z1 (416) 449-0164



## for your information



### PSU Filter Caps

A new long life, high performance computer grade aluminum electrolytic capacitor for use as an input filter capacitor, in off-line, switch-mode power supply applications, is now available from Mepeco/Electra. Designated the Series 3194, this new product features: operating life — 2000 hrs. at 85°C with full rated ripple; operating temperature — -55° to 105°C; 3 voltage ratings — 150, 200, and

250 WVDC; capacitance — 290 to 17,000  $\mu$ F; 39 standard case sizes from 1-3/8" to 3" diameter; available in PCB mounting configuration or with standard screw terminals. For further vendor information on the Mepeco/Electra Series 3194, contact: Mepeco/Electra, 6071 St. Andrews Road, Columbia, SC 29210, (803)772-2500, or local Philips distributors.

Circle No. 48 on Reader Service Card.

### Component Tracer

Heathkit's IT-2232 Component Tracer allows a user to test individual components or entire circuits without the need of circuit power. On a 3-inch CRT, the Tracer displays the electrical characteristics of a component or a circuit under test. Dual displays allow comparisons between good and suspect devices for quick, easy and reliable checks. Two voltage ranges are provided for varying test situations and are current limited to protect the circuit or component under test. Two sets of colour-coded test leads are supplied. The IT-2232 Component Tracer features two separate inputs that can be viewed as individual traces or together in a superimposed display. One channel is seen as a solid line, while the second is converted into a unique dotted line display by a special patent-pending circuit. In the A/B mode of opera-


tion, the superimposed solid- and dotted-line traces allow the user to compare good and suspect units. Any differences in electrical characteristics are clearly identified, providing a visual check of the condition of the circuit. Write to Heath Company, 1020 Islington Ave., Dept. 3100, Toronto, Ontario, M8Z 5Z3. Free catalogues are also available at 65 Heathkit Electronic Centers in the U.S. and Canada.

Circle No. 47 on Reader Service Card.

**Sparkomatic Canada, Inc., Markham, Ont.,** has added a 13-item accessory package program to its car stereo line. Included in the program are 3 noise filter kits, a universal in-dash car stereo mounting trim kit that fits Ford, Chrysler and GM cars for use with virtually any car stereo unit, a line of cable kits for high power car stereo systems and speaker wire kits, replacement speaker grilles, and other accessories.

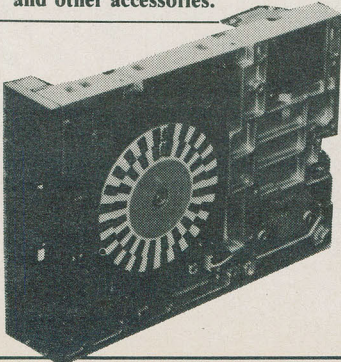
### Toshiba Floppy

Offering IBM PC and Xt users an alternative to disk drives, Toshiba America, Inc.'s Information Systems Division (ISD) has announced the addition of an IBM-compatible, 5.25-inch floppy disk drive to its family of dot matrix printers and personal/business computers. Suggested retail on the double-density ND-04D disk drive, with 500 KB per floppy is \$375.00 U.S. From Toshiba computer centres.



## HAMEG® Oscilloscopes

*For Field Service  
and Laboratory*

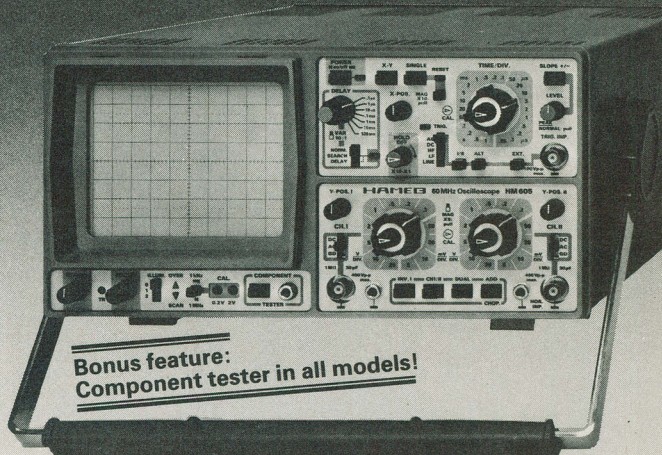

### HM605 60MHz Dual Trace

**\$1550.00**

Sensitivity 5mV-20V/div at 60 MHz, 1mV at 5MHz • Automatic peak-value or normal triggering to 80 MHz • Delay line • Variable sweep delay from 100 ns-1 s • Timebase range from 2.5s/div to max. 5ns/div • Unique fast-rise-time 1 kHz/1 MHz calibrator • Bright high-resolution 14kV CRT.

### HM204 20MHz Dual Trace

**\$1120.00**

Sensitivity 5mV-20V/div • 1mV at 5MHz • Timebase range 1.25s/div-10ns/div • Automatic peak-value triggering to 50 MHz • Delay line • Variable sweep delay • Single sweep mode • Y-Output • Z-modulation • Overscan indicator • Unique 1kHz/1 MHz calibrator.

### HM203 20MHz Dual Trace

**\$835.00**

Western Europe's best selling 20MHz-Scope! • Sensitivity 2mV-20V/div • Triggerbandwidth 40 MHz • Timebase range 0.2s - max. 20ns/div


### HM103 10MHz Single Trace

**\$550.00**

Small, compact service scope • Sensitivity 2mV-20V/div • Timebase range 0.2 $\mu$ s-0.2s/div • TV-V and TV-H triggering.
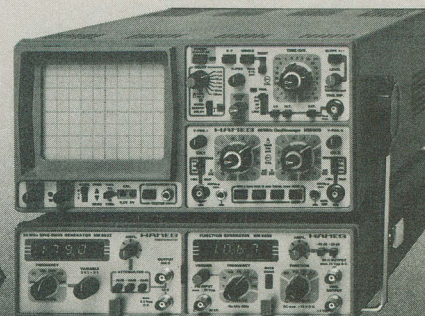
### Modular System HM 8000

An expanding range of signal generators, multimeters, counter/timers, etc. ...



For more details  
write or call collect:

**BCS**  
ELECTRONICS  
LIMITED®


980 Alness St. Unit 7,  
Downsview, Ontario  
M3J 2S2  
(416) 661-5585  
TELEX 065-28169

Hours: Monday to Friday 8:00 a.m. to 5:00 p.m., Saturday 10:00 a.m. to 1:00 p.m.




**COMPUTER**  
**PARTS GALORE INC.**  
316 College St.  
Toronto, Ontario M5T 1S3


## SOLID ABS CASE NUMERIC \$59.95

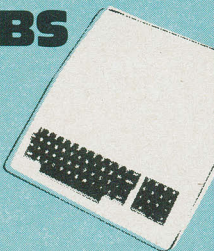

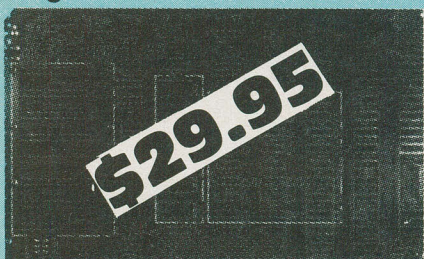**OUR 6502 BOARD**  
Now only \$29.95 still with  
all the versatility of the  
original and a full 8 slots.



## ASCII KEYBOARDS

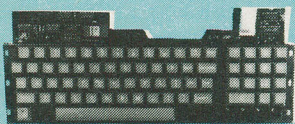

Now, we have a new keyboard, micro  
controlled with 3 levels of pre-coded  
functions for Basic, CPM etc. and at the  
same old price as before

Function Keyboard, Numeric . . . \$99.00  
Function Keyboard, Standard . . . \$89.00

## NEW STORE IN HAMILTON

Computer Parts Galore has opened a new  
store in Hamilton. Surplus oriented, it has  
most of the items we have in Toronto and a lot  
of surplus equipment that we do not have room  
to stock. Located at 11 Ferguson Ave, right  
across the street from Steel City Surplus, it is  
easy to get to and well worth the trip.

11 FERGUSON AVE. NORTH  
HAMILTON, ONT., L8R 1L1  
(416)523-6559

## MAIL ORDERS

We accept personal cheques, postal money orders, cer-  
tified cheques, traveller's cheques, VISA, American Ex-  
press, Mastercard, bank drafts. We ship C.O.D. only by  
CANPAR and truck. We do not use Canada Post C.O.D.  
We will send your goods via CANPAR or Canada Post  
unless you say otherwise. You will be charged a min.  
\$3.00 for delivery and handling or more if your goods are  
heavier than the \$3.00 weight or if you specify another  
delivery service that charges more. All Ont. res add 7%  
sales tax. We sell wholesale to any retail store or other  
reseller with a sales tax exemption so long as a realistic  
quantity is bought. We ship within a week if in stock,  
and we will cancel any backorders over 4 weeks unless  
otherwise instructed. 20% Restocking charge. All prices  
subject to change without notice. C.O.D. charge \$4.00  
extra.

**Toll Free Orders Only**  
**1-800-387-1385**  
Order Checking (416)925-8291  
Technical Data (416)925-1105

### BARE PCB FOR APPLE®

Real Time Clock	\$14.95	WILD II	\$14.95
RANA, 4 drive	\$14.95	SAM TALKS	\$12.95
9 Voice music	\$14.95	RS232 printer	\$12.95
Buffer printer	\$14.95	RS232 modem	
Graphic printer	\$14.95	Com	\$12.95
cable D or E(say)	\$24.95	RS232 asynch	\$14.95
80 column	\$14.95	Sprite graphics	\$17.95
80 column w.SS.	\$14.95		
Disc controller	\$ 9.95	Buy any 5 cards and	
Disc controller		deduct 10% • Buy any	
13/16 sector		10 cards and deduct	
autoselect	\$14.95	20% • Buy any 25	
SSM Modem	\$24.95	cards and deduct 25%	
Z-80	\$14.95	• Buy any 50 cards	
Multifunction		and deduct 35% •	
MNTN	\$14.95	Buy any 100 cards and	
128K Saturn	\$19.95	deduct 45% • Any	
EPROM	\$14.95	combination of the	
PIA	\$14.95	above cards	

### FIRM WARE ETC FOR PCB

Real time clock		HARD TO GET PARTS	
disc	\$8.00	MPSA13 transistor	75¢
9 voice music,		2N3904 transis.	20¢
2 discs	\$15.00	2N3906 transis.	30¢
Graphic printer		MPSU51 transis.	\$1.00
EPROM	\$10.00	2N4258 transis.	75¢
80 column		1K,9 pin SIP	\$1.00
3 EPROMS	\$24.00	1K,8 pin SIP	\$1.00
SSM EPROM	\$10.00	10K,10 pin SIP	\$1.00
Multifunction		4 POS dip switch	\$1.00
EPROM	\$8.00	8 POS dip switch	\$2.50
128K 3 disks	\$20.00	Disc male headers	\$2.00
Disc drive PROMS,		Disc fem flat	
Set	\$18.00	cable	\$2.00
EPROM program		6 pin power inline	\$1.00
EPROM	\$ 8.00	6 pin power	
Wild card EPROM	\$8.00	square	\$1.00
Wild card disc	\$8.00	RCA jack, PC	
SAM disc	\$8.00	mount	75¢
Sprite disc	\$8.00	50 Pf trimcap	\$1.00
RS232		220 Ohm trimpot	75¢
Proms set	\$18.00	68A45 for 80 col.	\$16.00
		MC3242 for 128K	\$16.00

### CRYSTALS

1.000 MHz HC33	\$8.95	6.144 MHz HC18	\$4.95
1.8432 MHz HC33	\$4.95	8.000 MHz HC18	\$3.95
4.000 MHz HC33	\$4.95	10.000 MHz HC18	\$3.95
3.579545 Mhz		14.318 MHz HC18	\$2.95
HC33	\$2.95	16.000 MHz HC18	\$4.95
3.579545 Mhz		17.430 MHz HC18	\$4.95
HC18	\$3.95	18.000 MHz HC18	\$4.95
4.032 MHz HC18	\$4.95	18.432 MHz HC18	\$4.95
6.000 MHz HC18	\$4.95		

## Vep 46 EPROM PROGRAMMER/ ERASER

**\$449.00 Specify IBM®  
or Apple Host Adaptor**

The VEP 46 is a totally new concept in EPROM programmers that gives a high degree of freedom to the programmer. Software supplied allows access to the entire memory array of the host computer so that sections of ROM can be examined, moved, edited, and copied to up to 4 EPROMS at one time. Novel BIOS programs can be composed and tested easily and rapidly, the built-in UV lamp allows erasure of up to 10 EPROMS at one time in 20 minutes. Any 5 V EPROM, with few exceptions can be programmed. Currently host adaptors are available for the Apple and IBM machines with Commodore to be ready soon. The VEP 46 comes with an extensive manual with step by step instructions showing how to do everything simply and easily. Some features are:


- CSA approved power supply
- Compares up to 4 EPROMS to reference EPROM, lists all errors
- Verifies up to 4 blank EPROMS
- IBM® version now ready
- Takes no power from host
- 2716, 2732, 2732A, 2764, and 27128 EPROMS programmed
- Built-in UV erasing lamp
- Edits
- Apple® version now ready
- Commodore® version soon ready
- Programs up to 4 at once
- Uses ZIF sockets
- Bleaches 10 EPROMS at once
- Disc driven
- Examines all Host memory data
- Priced at a very low price
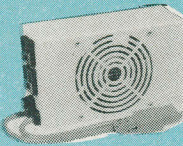
## GREAT DEAL

THE GREAT DEAL  
CARRIES ON FOREVER AND GETS BETTER



Our proven 6502 motherboard plus a numeric case plus  
a black beauty powersupply plus a numeric keyboard  
plus any 4 bare pcb for \$275.00.



## SYSTEM SAVIOUR


2 grounded 3 wire switched sockets, pilot light, surge  
protector and on-off switch to turn off your system and  
two plugged in items . . . . . \$45.00

## POWER SUPPLY




Our Famous "BLACK BEAUTY" power supply, now  
reduced in price but not in quality. Our ratings are  
5V-5A; 12V-2.5A; 5A-½ A; 12V-½ A for real . . . . . \$79.95
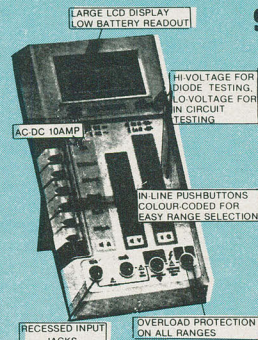
## DIGITAL MULTI-METER AMAZINE QUALITY AT LOW COST \$69.96



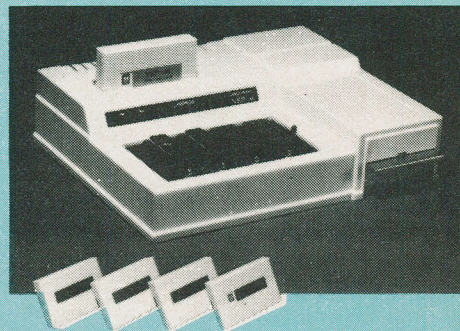
### EXTRA FEATURE

- Diode test circuit • Lo voltage ohms, 0.5v • Lo bat-  
tery indicator • Auto-Zero • Auto polarity • Overload  
protection, all ranges • ABS case (will not crack) •  
One hand push buttons.






new!

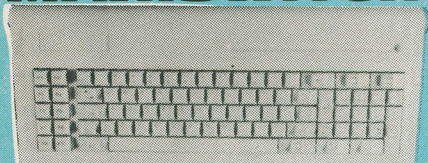DTC™ DISPLAY  
TELECOMMUNICATIONS  
CORPORATION**MEGA-BOARD™****NEW FROM  
MAXISWITCH™**

The famous Maxi keyboard . . . . . **\$189.00**  
We also have a Taiwanese keyboard using capacitive keyswitches that we can offer at a very competitive price, has all the same features, only . . . . . **\$159.00**  
Specify Apple™ or IBM™ compatible . . **\$159.00**

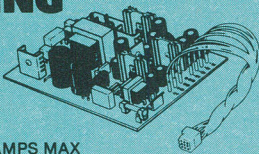**SWITCHING  
POWER  
SUPPLY**

SPECS: +5 VDC 5 AMPS MAX  
#1 +12 VDC 2.8 AMPS MAX  
#2 +12 VDC 2.0 AMPS MAX  
-12 VDC .5 AMPS MAX  
INPUT: 115 or 230 VAC 60Hz


**A Best Buy at  
\$49.95 each**

**MEGABOARD/MBE-XT PARTS**

- |                                  |                                  |
|----------------------------------|----------------------------------|
| a) Maxi keyboard . . . \$189.00  | n) 6-35pf trimcap . . . \$1.00   |
| b) IBM case hinged . . \$89.95   | o) 62 pin edge con . . \$2.95    |
| c) Intel/AMD IC set . . \$159.00 | p) 5 pin DIN . . . . . \$1.95    |
| d) 8253-5 . . . . . \$11.95      | q) power con M/F . . . \$2.50    |
| e) 8259A . . . . . \$11.95       | r) 4.7K x 6 SIP . . . . . \$ .75 |
| f) 8237A-5 . . . . . \$34.95     | s) 4.7K 16 pin NTWK . . \$1.00   |
| g) 8255A-5 . . . . . \$29.95     | t) 8.2K(10K) 16PNTWK\$1.50       |
| h) 8284 . . . . . \$8.95         | u) 330Ohm res NTWK . . \$1.50    |
| i) 8288 . . . . . \$29.95        | v) TBP24S10 PROM . . \$9.95      |
| j) 8088 . . . . . \$34.95        | w) BUS bars, ea. . . . . \$1.50  |
| k) 8087 . . . . . \$399.00       | x) header pins, ea. . . . \$ .05 |
| l) 100 NS delay . . . \$14.95    | y) speaker (2-3") . . . \$2.95   |
| m) 7 NS delay . . . . \$14.95    | z) 0.1uF (1 or 2") . . . \$ .17  |

**BARE PCB FOR IBM™**

- (A) Colour graphics board, similar to the PER-SYST board, but not quite the same, has all the same features and is easy to build complete with parts list and placement diagram . . . **\$34.95**  
(B) IBM disc controller board, similar to the original, runs 2-4 DS/DD drives . . . . . **\$24.95**  
(C) IBM disk controller I/O board, like the above but will also control a printer via a parallel port . . . **\$29.95**  
(D) Multifunction board, has 14 functions including calendar, time, serial ports, parallel ports, etc. . . . . **\$29.95**  
All boards come with a parts list and a placement diagram for easy assembly.

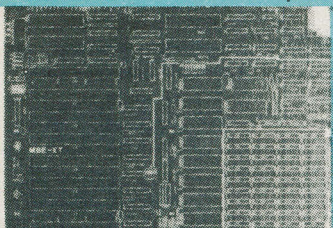**MBE-XT****\$49.95**

At last, an affordable high-tech IBM PC/XT workalike. Has full 256K memory and the same size as the original, 8 slots, plus space for 8 ROMs, or EPROMs holding the language of choice and a BIOS, fully IBM compatible and works perfectly with the MEGA-BIOS listed on this page. It is not expandable on board to 1M, nor does it have all the features of the MEGABOARD, but it is smaller and works like a champ.

MBE-XT, with assembly data . . . . . **\$49.95**

IBM is a registered trademark of  
International Business Machines


**Eight Compatible  
I/O Interface  
Connectors**  
(Full PC compatible)  
(compatible with all  
IBM-PC\* plug-in cards)

**Special J1  
Interface**  
(Allows horizontal mounting of compatible expansion cards for easy bus expansion and custom configuring) (Board has 62 pin gold plated compatible connector)

**Extended ROM  
Capability**  
(Runs all compatible PC ROMs) (Jumper programmable to accommodate all popular 8K, 16K, 32K and 64K ROM chips and NEW EE ROMs! VPP power pin available for EP ROM burning!) (External VPP voltage required)

**Full Mega-Byte Ram Capacity!  
On board!**  
(With parity)  
□ 256K Bytes using 64K chips  
□ 1 Mega Bytes using 256K chips

**Mega-Board®** . . . . . **\$99.95**  
With full assembly data.  
**Mega-Board®**, Users manual with schematic, ap. notes and theory, etc. . . . . **\$19.95**  
**MEGA-BIOS®**, a fully MS-DOS, PC-DOS compatible non-infringing BIOS . . . . . **\$29.95**

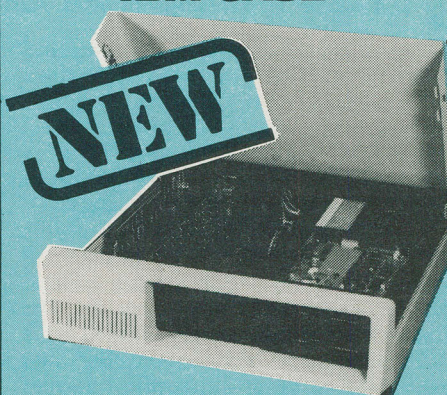**IBM CASE**

At last, a nice new case for the 5 slot or 8 slot IBM workalike boards. Fits our power supply and most others, and has either 5-6 slots or 8 slots (please specify when ordering). Comes with all rubber feet, drive blind plugs, card guides and has the best feature of all, a hinged lid that allows quick and easy access to the insides for service; the top opens when two spring clips are pushed and re-latches automatically . . . **\$89.95**

**WIRED N TESTED  
MEGA-BOARD™**

- (A) Socketed and tested with no IC's, all soldered in parts are included, just buy the IC's, and memory . . . . . **\$299.00**  
(B) Socketed and tested with all IC's, BIOS, 64K of RAM and complete manual and schematics . . . **\$595.00**  
(C) As above, each 64K increase . . . . . **\$75.00**  
Up to 256K, for 256K RAMs, price on request.  
(D) Minimum system, 1 DS/DD drive, Disk controller, colour graphics, 100W power supply, full cabled, 64K . . . . . **\$1995.00**  
Each 64K up to 256K . . . . . **\$95.00**

**Standard Key-board Interface**  
(Full PC compatible)

**Hardware Reset**  
(Overcomes reset flaw in PC)

**Power Connector**  
(Full IBM\* pinout compatible)

**8088 Processor**  
(Same as PC)

**8087 Numeric Processor**  
(Same as PC)

**Peripheral Support Circuits**  
(Same as PC)

**Configuration Switches**  
(Same as PC)

**Speaker/Audio Port**  
(Same as PC)

**Wire Wrap Area**  
To facilitate special custom applications!

**FULL IBM - PC\*  
COMPATIBILITY!**

**ONLY!  
\$99.95**  
Evaluation Board Kit

**MEGA-BOARD™ Evaluation Board Kit!**

(Blank board with full assembly instructions and parts list.)

Includes highest quality PC board with gold plating, silk screen, solder mask

**MAIL ORDERS**


We accept: Personal cheques, postal money orders, certified cheques, traveller's cheques, Visa, American Express, Mastercard, bank drafts. We ship C.O.D. only by CANPAR and truck. We do not use Canada Post C.O.D. We will send your goods via CANPAR or Canada Post unless you say otherwise. You will be charged a min. \$3.00 for delivery and handling or more if your goods are heavier than the \$3.00 weight or if you specify another delivery service that charges more. All Ont. res. add 7% sales tax. We sell wholesale to any retail store or other reseller with a sales tax exemption no. as long as a realistic quantity is bought. We ship within a week if in stock and we will cancel any backorders over 4 weeks unless otherwise instructed. 20% restocking charge. All prices are subject to change without notice. C.O.D. charge \$4.00 extra.

**WE'VE GOT EM!  
5-1/4" HALF SIZE DRIVES**

- 40 Track per side
- Double-sided, double density
- Same as SA455
- Latest head & drive technology
- Fast access time



Two of These Half Size Drives will  
Fit in the Same Space as 1 Full Size Drive! **\$249.00**

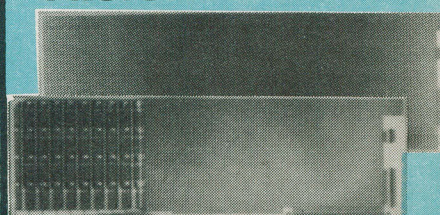**PROTOTYPING CARDS**

Wire Wrap, DB-25, DB-9, all holes . . . . . **\$29.95**

Memory, wire wrap, with 256K/1M memory gridded onto card front, rest holes . . . . . **\$34.95**

Card extender, lifts any plug in card up by about 6" for easy service . . . . . **\$29.95**



# What's Happening in Shortwave

Despite satellites and other hi-tech, shortwave broadcasting remains one of the most useful communications methods.

## Computer Weather Maps

Fax, or facsimile, is the process of sending images by shortwave radio. It's like an extremely slow television broadcast, with the limited bandwidth restricting the printout speed to one frame every few minutes. In the case of weather maps, data from satellites is collected by various weather services and a map produced. The map is then scanned with a photocell; the resulting electrical impulses can then be re-transmitted via shortwave (or landlines) to mariners, airports, etc. The maps can then be reconstructed mechanically by beaming the received pulses onto a rotating drum of photosensitive paper, or electronically by decoding them via a computer/printer.

Electronics Today is investigating a project (and software) that will display weather maps using a shortwave receiver, a demodulator, and a micro. In the meantime, dedicated tinkers may want to experiment with the broadcasts: you can find the map service from Washington, DC, on 3356, 4975, 8080, and 10865 KHz. Australia broadcasts on 5100, 11030, 13920, and 19690 KHz. The maps are generally scanned at 120 lines per minute, though there isn't any international standard, and the rates may vary.

## RTTY

Radio-teletype is used by news services to send text; the system is a bit antiquated,

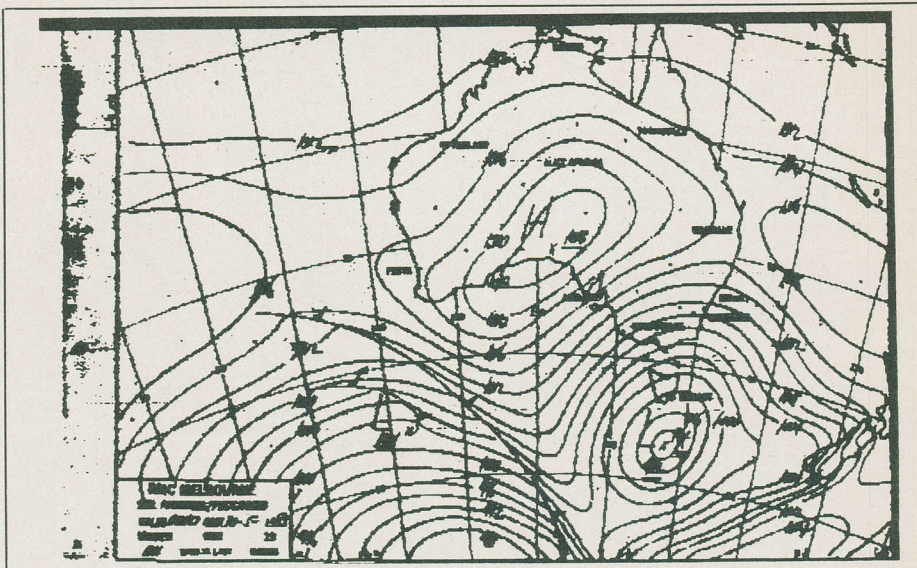


Fig. 1. A weather map from station AXM, Australia, decoded by microcomputer.

being designed around the mechanical teletypes of yester-year, but there's a lot of information on the airwaves if you care to experiment. Again, Electronics Today is considering a project and software to allow the display of RTTY text on a computer screen. Stay tuned, so to speak.

RTTY uses a frequency-shift-keying method to encode the stream of high and low bits; two audio tones are transmitted, one for a high and another for a low. The frequency shifting can be detected by a discriminator or phase-locked-loop and converting to serial bitstream. Teletypes use various standards for the encoding, from 45 to 100 baud. However, they don't resemble the usual 10-bit "byte" sent by computer modems; a 5-bit code called

BAUDOT is used, giving 32 possible alphabetic characters. To send numbers, a special character is sent to let the equipment know that the next byte to be transmitted will represent a numeral.

Converting this to computer-readable form is a challenge, but until our PLL project is ready, diehards can find text on, for instance, 13779 KHz (Voice of America) or 16100 KHz (Chinese News Agency).

## Commercial Shortwave

Despite all the publicity received by satellites, shortwave remains the simplest way to get broadcasts to remote areas. Canada's northland is served by several sources: the Canadian Broadcasting Cor-


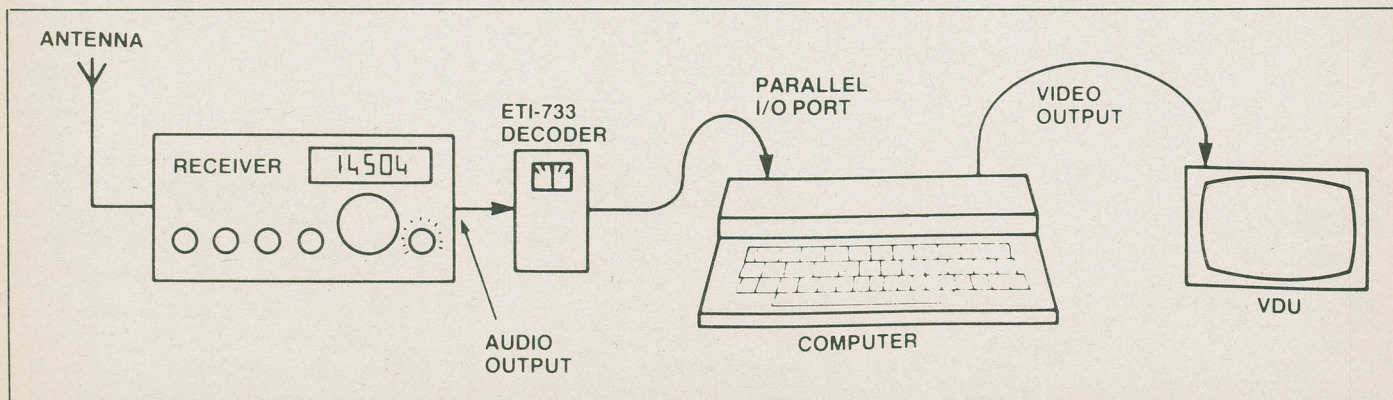


Fig. 2. A typical hookup for decoding radio-teletype via computer.

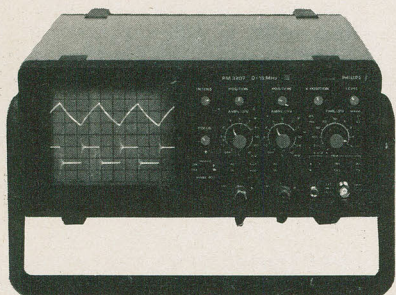


# "Scopes from Philips..."

## BRAND NAME SCOPES AT GENERIC PRICES



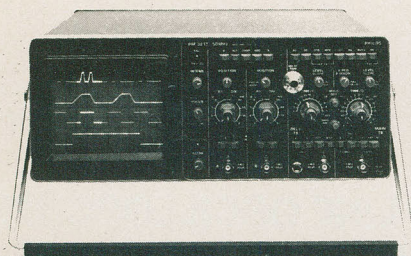
**PM 3207 \$780.00**

The PM 3207 exhibits many features associated with more sophisticated, expensive, oscilloscopes, yet remains an extremely compact and lightweight instrument. Whilst ideal for a very wide range of field applications, it is equally acceptable for workshop use, because of its small size.



**PM 3215 \$1,710.00**  
**PM 3217 \$2,160.00**

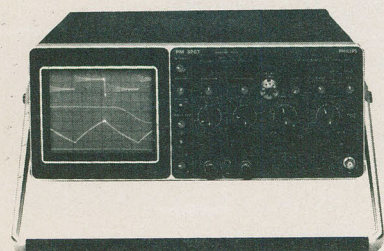Both models utilize to-day's most advanced circuit design and component technology to achieve an excellent, very reliable, all-round performance, for both analog and digital measurements.



**PM 3267 \$2,635.00**

PM 3267 has been designed for a wide range of applications – from the simple to the sophisticated – in workshops, laboratories or tough field conditions. In particular those engineers with non-specialist experience in electronics seeking easy-to-operate test equipment will find the PM 3267 a most useful, uncomplicated tool, well within the scope of their understanding.

ALL PRICES IN CANADIAN DOLLARS AND INCLUDE DUTY AND FEDERAL SALES TAX.

### PM 3207

- 15 MHz/5mV
- 2000V acceleration voltage
- Large 8 × 10 cm screen
- Auto, TV triggering
- Same sensitivity on X and Y channels
- B-invert facility
- Triggering from A or B channel
- Double insulation

### PM 3215 / PM 3217

- High 2mV sensitivity across full 50 MHz bandwidth
- Easy auto-mode triggering plus level control
- Automatic TV triggering on both line and frame
- DC-coupled triggering
- Variable trigger hold-off avoids double-writing
- Full X-Y display facilities including X-X/Y
- Compact size and low weight with battery option

### PM 3267

- 100 MHz
- Wide input voltage range
- Trigger view as third display channel
- Alternate main and delayed time bases
- Automatic triggering
- Robust, fully enclosed cabinet for difficult environments
- Double insulated power supply

**ALL MODELS CARRY 3 YEAR WARRANTY  
FOR MORE INFORMATION ON THESE AND  
OTHER GREAT VALUES IN OSCILLOSCOPES,  
CONTACT YOUR LOCAL PHILIPS OFFICE**

TORONTO (416) 292-5161 MONTREAL (514) 342-9180  
OTTAWA (613) 237-3131 CALGARY (403) 243-2710



**Test & Measuring  
Instruments**

**PHILIPS**

PEL-310



## What's Happening In Shortwave



poration's Northern Service, and a rebroadcast of various privately-owned stations.

The CBC's shortwave service is known as Radio Canada International, and

they broadcast on a wide number of frequencies between 6 and 21 MHz. Programming originates in Montreal and is relayed by microwave to transmitters at Sackville, New Brunswick. The broad-

casts to Northern Canada are in English, French, Eskimo, and Cree; some of the frequencies are (in KHz): 9625, 6065, 6195, and 11720. As you'd expect from the name, there is wide international coverage in many languages. The Montreal signal is sent via undersea cable to transmitters in the UK and Portugal.


There are at least four shortwave rebroadcasts of privately-owned stations: Toronto's CFRB on 6070 KHz, Montreal's CFCF on 6005, Calgary's CFCN on 6030, and Halifax's CHNS on 6130. The transmitting power isn't much by commercial AM standards — 0.5 to 1 kW. However, under good atmospheric conditions, you should be able to tune in to a big-city broadcast as you put up your wilderness tent.

For a comprehensive listing of the world's broadcasters, we recommend the World Radio TV Handbook, available at specialist bookstores, or contact Billboard Publications, One Astor Plaza, New York, NY 10036. **ETI**



**DUNCAN INSTRUMENTS LTD.**  
ELECTRONIC INSTRUMENT SPECIALISTS

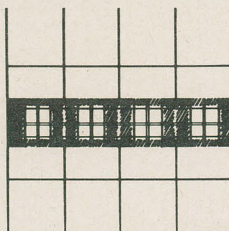121 MILVAN DRIVE,  
TORONTO, ONTARIO M9L 1Z8 TELEX: 065-27271



## TOP LINE OSCILLOSCOPES. BOTTOM LINE PRICES.

FOR FULL DESCRIPTIVE BROCHURES: (416) 742-4448


### MODEL 6022

DUAL TRACE 20MHz OSCILLOSCOPE

- 6" CRT with internal graticule
- 20MHz bandwidth (—3 dB)
- Stabilized power supply
- Trace rotator
- Low power consumption
- X-Y mode; Add/Subtract; 5 trigger modes
- Built-in component tester

**\$575.**

FST and Dual Probes included.

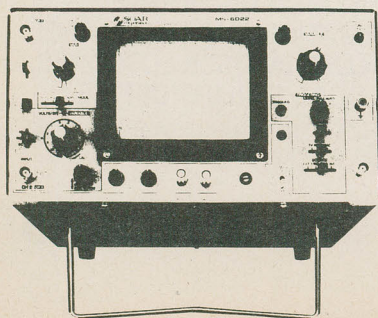


### MODEL 6035

DUAL TRACE 35 MHz OSCILLOSCOPE

- 35MHz bandwidth (—3dB)
- Delayed trigger sweep
- Sensitivity 1mV
- 6" rectangular tube
- 10 ns rise time
- X-Y operation

**\$975.**

FST and Dual Probes included.

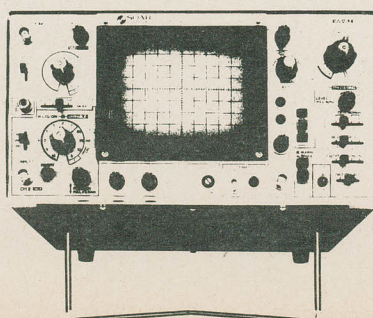


### MODEL 6100

4 TRACE 100MHz OSCILLOSCOPE  
WITH 8 DIGITAL INPUTS

- 100MHz bandwidth (—3dB)
- 3.5 ns rise time
- Delayed time base
- 4 channel inputs plus 8 digital data inputs
- 1mV/div sensitivity

**\$2,450.**

FST and Dual Probes included.

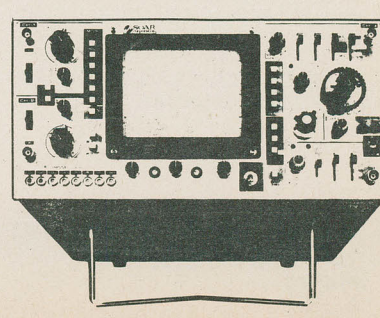



**An Important Announcement  
To Advertisers and Readers of  
Computing Now! and Electronics Today**

The October issue of Computing Now! and Electronics Today will feature the Directory of Microcomputer and Electronic Retailers in Canada.

This semi-annual update will not only supply name, address and telephone listings for a combined total of over 1200 outlets but will inform readers and advertisers of the product line offered by each outlet and whether catalogues are available on request.

For advertisers, these issues offer a special opportunity to display their message to not only the thousands of regular readers of Electronics Today and Computing Now! from coast-to-coast but also the many additional readers and companies who purchase these special issues for permanent record and for distribution to staff. For readers, there is the opportunity to find out about the many new outlets that have surfaced since the last update.

Additional copies of these issues will be available on a bulk copy basis and orders should be forwarded now to the Circulation Manager of each publication. For advertising space reservations contact should be made immediately with Omar Vogt, Rick May, or Claire Zyvitski at (416) 423-3262. Time is of the essence to avoid disappointment.

Moorshead Publications are proud to be able to serve the computer and electronics fields in this fashion. We thank the outlets involved for their help and co-operation.

Sincerely,

*Halvor Moorshead*

Halvor W. Moorshead,  
Publisher

**Moorshead Publications, 25 Overlea Boulevard,  
Suite 601, Toronto, Ontario, M4H 1B1**



# Audio Recording

**Linsley Hood enlightens us on the ins and outs of audio recording.**

ALTHOUGH the tape recorder in its cassette form is almost taken for granted, in reality, recording on magnetic tape is beset with so many problems, and hedged around with so many restrictions and limitations, that it is surprising that it even works at all, let alone that it gives the superb results, which, when all is done well, it can!

Having said that, it is difficult to find any description of this technique which explains these problems and limitations in a way which is easy to follow. So before I proceed to look at the types of circuitry which are needed for tape recording, I propose to try to explain, as simply and lucidly as I can, just what it is that we need to do.

## The Process

If we pull a piece of unmagnetized iron oxide coated tape past a recording head, as in Fig. 1, and we apply an alternating current to the electrical winding on this head, we will leave a series of magnetized regions, as indicated by N-S-N-S-N-S..., produced by the magnetic field at the trailing edge of the record head gap. These will have a 'wavelength' along the tape given by  $\lambda = \text{tape speed (ins/sec)}/\text{frequency (Hz)}$ . If we try to replay this, with a head having a gap length  $X$ , we will have zero output when  $X = \lambda$ , since both ends of the gap will be sitting on parts of the tape which are identically magnetized (i.e., both N or both S). This is **Problem No. 1**: the gap length of the replay head imposes an absolute limit on the upper frequency response.

It is a characteristic of magnetic induction that the voltage induced in a coil of wire is linearly proportional to the speed with which the magnetic flux through that coil is changed. In mathematical terms, this is expressed as  $V = L \cdot dB/dt$ ; where  $L$  is the inductance,  $B$  is the flux density, and  $t$  is time. ( $d/dt$  is the mathematical notation for a rate of change with time).

The result of this is that if we were to record at a constant remanent flux level on the tape, which we will assume will be given by a constant level of (RMS) current through the record head, we will end up

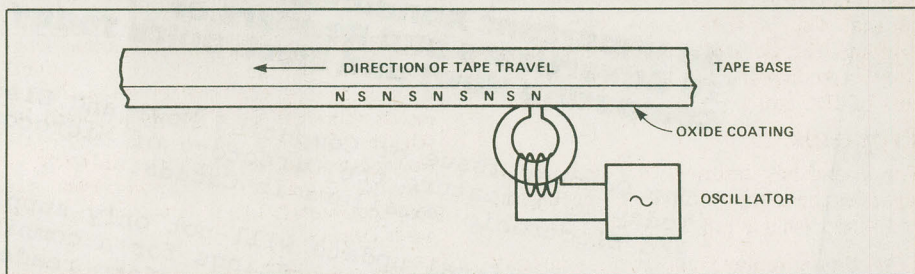


Fig. 1. The basic principle of tape recording.

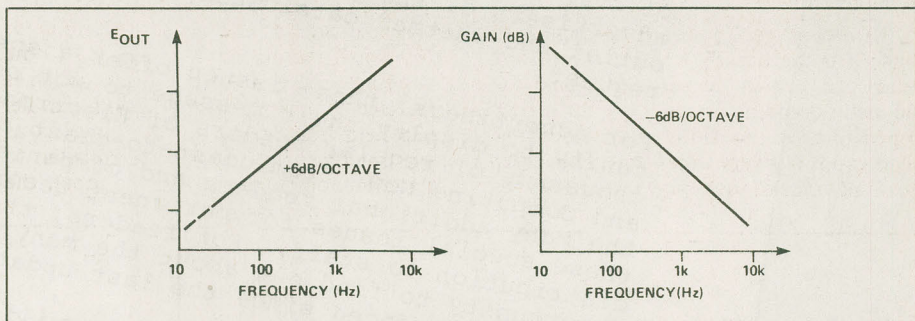


Fig. 2. The theoretical AC output from a tape replay head.

Fig. 3. An idealized replay amplifier characteristic.

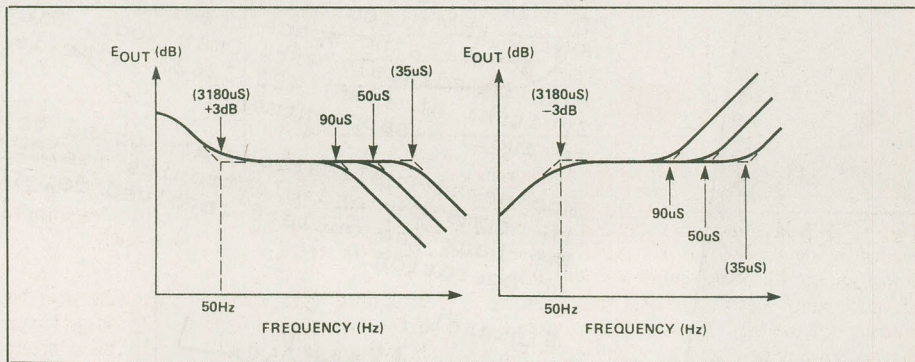


Fig. 4. NAB recommended record characteristics (effective).

Fig. 5. NAB recommended replay response (effective).

with a replay characteristic as shown in Fig. 2, in which the output increases linearly with frequency. This will necessitate a replay characteristic such as in Fig. 3, if we are to get a level final frequency response; this, in itself, would not present any great circuitry difficulty.

In the same way in which an internationally agreed standard is employed in the manufacture and replay equalization used for 33 RPM and 45 RPM records, (the RIAA standard) there is an internationally accepted standard for record and

replay equalization for tape and cassette recording (the NAB standard). This requires effective record and replay characteristics of the type shown, with the appropriate time-constants for the turn-over points on the frequency scale, in Figs. 4 and 5. When the replay equalization curve is superimposed on the curve of Fig. 3, we get the practical replay equalization characteristic of Fig. 6, which is what we will hope to find if we do some measurements on the replay side of a commercial tape or cassette recorder.



To avoid the need for a replay gain characteristic, which continues to rise as frequency decreases, the NAB curve provides for an LF turn-over point of 50 Hz, expressed as a 3180  $\mu$ s time constant, and an HF turnover point that depends on tape speed as listed in Table 1. Turn-over frequency,  $f$ , is given by  $f = 1/2\lambda\pi CR$ ; the value of CR is the time constant, and this is normally expressed in microseconds ( $\mu$ s) so that Cs, in nanofarads and Rs, in kilohms, can be used directly for calculations, avoiding the need to throw in factors of  $10^9$ , etc.

## Problems

The above has assumed an ideal world; however there are a number of problems, as follows (this is not a complete list!).

**1. Maximum replay frequency:** As already mentioned, the size of the replay gap imposes an absolute limit on the upper frequency response.

**2. Effect of replay head gap spacing:** Since it is the trailing edge of the record head gap which leaves the remanent magnetic domains on the tape, to a first approximation the width of the recording head gap is not very important. However, this is not true of the replay head (as we've

Table 1		
15 ins/sec 38 cms/sec	50/3180 NAB/BSI	35 DIN/CCIR
7.5 ins/sec 19 cms/sec	50/3180 NAB/BSI	70 DIN/CCIR
3.75 ins/sec 9.5 cms/sec	90/3180 BSI	140 CCIR
	70 or 120/3180 BSI & DIN/CCIR	(cassette only)

Equalization time constants of various standards; (NAB (or NARTB) — National Association of Radio and Television Broadcasters (USA); BSI — British Standards Institute; DIN — Deutscher Industrie Normenausschuss (W. Germany); and CCIR — Comité Consultatif International des Radiocommunications (International Standards Organizations).

**4. Tape, magnetic non-linearity:** All of the above problems pale into insignificance in comparison with the high degree of non-linearity of the magnetic tape itself. The characteristics of this are shown in Fig. 9. If a small signal current is applied to the windings of the recording head (which is an electro-magnet with a small parallel gap held in contact with the tape, set as accurately as possible, perpendicular to the direction of motion of the tape), the

Fortunately, after a lot of early experimentation with this medium, a trick was found which would solve this snag. This scheme was known as 'HF bias', or in normal tape parlance simply as 'bias'.

**5. Need for bias:** If a suitable high frequency AC signal is simultaneously applied to the recording head with the signal which it is desired to record, and if this HF signal, which will typically be somewhere in the range of 30 kHz to 250 kHz, it is a good bit larger than the recording signal (typically 20 to 100 times) so that it sweeps the BH characteristics of the tape backwards and forwards across the non-linear region of the BH characteristic, one can, surprisingly, end up with a quite linear magnetization of the tape, as shown in Fig. 10a. However, as you will by now expect, there is another snag, and this is that the final recording characteristics of the tape depend on the size of the applied bias waveform. If we apply more, we get the curve shown in Fig. 10b, which is one of reduced recording sensitivity. Also, too much bias tends to 'erase' the higher audio frequencies which we are trying to record. Moreover, the 'correct' level of bias depends a lot on the actual tape being used at the time, and without previous ex-

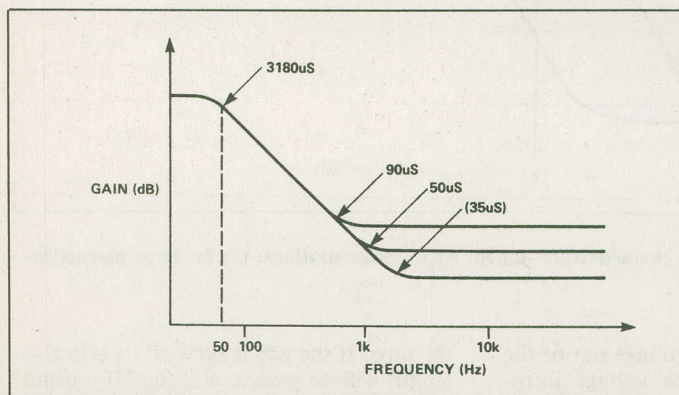


Fig. 6. A practical replay equalization characteristic for reel-to-reel recorders which conform to NAB recommendations (cassette replay to BSI/DIN specifications would use 70/120  $\mu$ s).

already seen). Below the maximum replay frequency, the HF response is very dependent on gap width, as I have shown in Fig. 7. Unfortunately, the output from the head also falls as the head gap-width is reduced, partly because there is less magnetic material in the gap, and partly because of the magnetic shunt effect, due to the proximity of the two sides of the head gap.

**3. Effect of tape speed:** The differing equalization characteristics, quoted above, tacitly recognize that the performance of the recorder, other things being equal, will be very strongly influenced by the speed at which the tape passes under the replay head. Not only will the output signal fall as the speed is reduced, but the HF performance will also be impaired, as I have shown in Fig. 8.

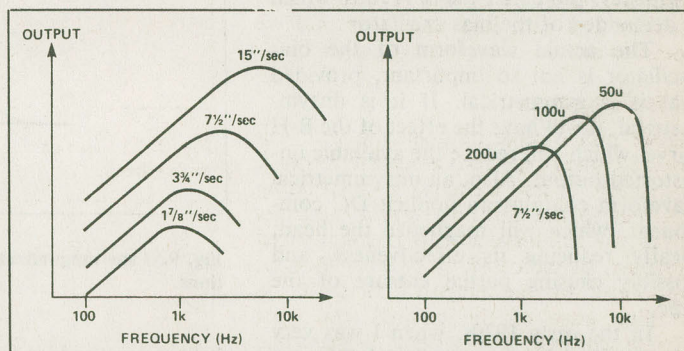


Fig. 7. (left) Output level versus frequency response for different tape speeds.

Fig. 8. (right) Output level versus frequency response for different head gaps.

remaining flux on the tape (B) will be related to the applied magnetizing force (H, which is proportional to the current flow through the winding on the head) in the way shown in Fig. 9a.

Clearly, this would not lend itself to hi-fi reproduction. At small signal levels, the recording would be very inefficient with hardly any remaining magnetism on the tape at all. At higher levels there would be the equivalent of a large amount of 'crossover' distortion, and at greater recording levels still, there would be a lot of 3rd and other high-order harmonics generated as the tape magnetization was pushed into the regions where the curve flattened again. Also, to add to the problems, if the tape is magnetized fully, there is a 'hysteresis' loop in its magnetic characteristic, as shown in 9b.

perience, we cannot know what that will be!

**6. Problems with bias:** The dependence of recording characteristics on bias level is shown in the graph of Fig. 11. This curve (a) shows the relationship between recorded level and bias current at 1 kHz, and (b) the same thing for an input recording signal at 10 kHz. Clearly, the bias setting has a large effect on the flatness of frequency response of the tape recorder. Curve (c) shows the effect on the distortion of the recorded signal of the bias level. Good HF response is not readily compatible with low THD. The effect of bias level on tape 'modulation' noise is shown in Fig. 11, curve (d). Here, happily, low noise levels fit in fairly well with other needs.

The actual frequency of the bias signal is not very important, though there



## Audio Recording Technology

is some evidence that the recorded noise level on the tape, and the distortion at the upper end of the audio spectrum, may both be lessened by the choice of the higher bias oscillator frequency. The snag here is that it is the current through the head which is important, and because the windings have inductance, a higher bias frequency will require a higher applied bias voltage. Also, the head will work progressively less efficiently at higher frequencies, which contributes to this effect.

**7. Design of bias oscillator:** The tape cannot distinguish the source of the signal which is applied to it. It will therefore record small noise voltages present on the bias voltage waveform just as easily as it will record the noise components present on the incoming signal. So, if the bias voltage waveform is 20 times the size of the signal being recorded, its signal-to-noise ratio will need to be a lot more than 20 times better if it is not to degrade the S/N ratio of the incoming signal. You will note that I have referred to bias voltage, not to bias current. This is because the noise signal will be a wide band, and will not be restricted by the inductance of the head to the same extent as the HF bias waveform. Therefore, the higher the bias frequency, the better the S/N ratio which is demanded of the bias oscillator.

The actual waveform of the bias oscillator is not so important, provided that it is symmetrical. If it is unsymmetrical, it will have the effect of the B-H curve, which will reduce the available undistorted output. Also, an unsymmetrical waveform contains an implicit DC component, which will magnetize the head, greatly reducing its effectiveness, and possibly causing partial erasure of the tape.

In the early 1970s, when I was very interested in cassette recording, I did some experiments with both square wave and sawtooth bias waveforms. Both worked, and the square appeared to be quite effective. However, for reasons of practical convenience, it is desirable that the erase oscillator should operate at the same frequency as the bias oscillator, and it is easier to get large voltages at a good S/N ratio from an LC sinewave oscillator. Square wave (RC) generators tend to have fairly poor S/N ratios, due to jitter on the 'flip' times.

**8. Effect of head inductance:** Our aim in recording, is to record all the frequencies in the audio band equally. However, the recording head has inductance, which will restrict the flow of current at higher frequencies. It is necessary, therefore, to find some way around this problem. Of the possible solutions, the simplest is to put a resistor, say 47k, in series with the output from the recording amplifier, to swamp the effect of the changing impedance of the record head with frequency. This also

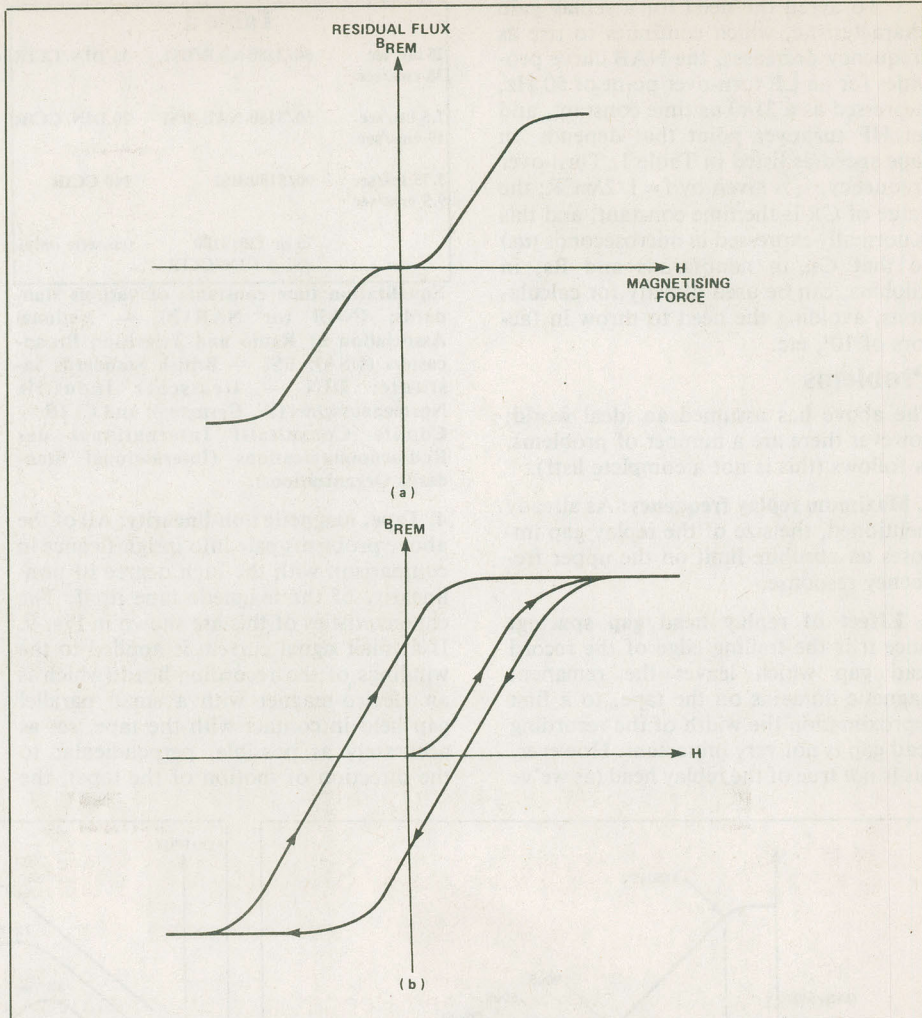


Fig. 9. Tape magnetization characteristics: (a) for small magnetizations; (b) for large magnetizations.

helps keep the bias HF voltage out of the recording amplifier. Bias voltage intrusions would probably do no harm provided that they did not push the record amplifier into a non-linear or overload condition.

Other useful solutions, which make lesser demands on the size of the signal output from the recording amplifier, are to design this amplifier so that it has a high output impedance, or to use a current NFB loop to make the amplifier look like a constant current source. All DC components must be rigorously excluded from the head windings to avoid head magnetization. If a DC blocking capacitor is used, it should be of good quality, and switch-on current surges through this must be prevented.

**Head alignment:** The way in which the width of the replay head affects the HF response of the recorder has been shown above (Fig.7). This presumes that the head is accurately aligned so that its gap is at right-angles to the direction of travel of

the tape. If the gap is skewed, its effective length will be greater and the HF output will be less. The same applies if the record and replay heads do not have the same alignment. This may be less important if one records one's own tapes, but on pre-recorded tapes this is vital. Happily, alignment tapes are fairly easy to buy. On these, though a double-beam oscilloscope makes matters simpler, one can do quite a good job by just adjusting head azimuth for maximum HF output, usually by working upwards through the frequency test bands provided.

**10. Noise and noise reduction:** Because of the granular nature of the oxide coating deposited on the tape, all tape recordings will suffer from some degree of background noise. In addition to this, any parts of the record process which tend to clump or otherwise disturb the uniform random distribution of the magnetic domains, will make this background noise worse. Erase oscillator systems are not perfect in this respect, as can be shown by





## **Electronics Today helped Mike Honing build his business.**

Mike Honing, President of R.H. Nichols Co. Ltd., one of Canada's largest suppliers to industry of Test Measuring and Recording Instrumentation and Process Instrumentation, has used Electronics Today virtually exclusively to market his Metermaster division to the consumer marketplace. There is a reason.

Mr. Honing says, "I have used Electronics Today since its launch in 1977, first on a quarterly basis, and now virtually every month. Although I have tested other media for Metermaster, I have not found any other vehicle to be better. Reader response is measured and we consistently receive enquiries to justify our advertising investment.

"Further, direct sales are substantial and 95-100% can be attributed to Electronics Today. Our corporate aim of supplying quality products for a reasonable price, thus giving value for money is accomplished through Electronics Today and its readership."

This tells you a great deal about Moorshead Publications and its readers, since in addition to Electronics Today, Mr. Honing uses Computers in Education to reach the educational market. As publications, they deliver results that are measurable. Let our Account Executive show you how Electronics Today and its sister publications can deliver for you and your company as it does for Metermaster.

**Electronics Today** INTERNATIONAL **can help build your business as well.**

For Advertising Information Call (416) 423-3262

In Quebec (514) 735-5191



# AM Stereo Update

**ET updates the AM stereo scene with a look at a broadcaster's position and a couple of new stereo receivers for AM.**

**by Edward Zapletal**

FOR SOME time now we have had our ears pampered by the clean, rich sound of FM stereo broadcasts. The early seventies (technological middle-ages) brought us a much improved quality in the various listening media: LP records, home and portable stereo units, and AM/FM cassette car stereos. The shift in listener preference to FM began here, and with a few exceptions, AM radio's decline was signalled. Today, technological advances give us miniaturized home stereos not much bigger than car radios, 'computer controlled' gadgets to keep us amused, and now, AM stereo.

## AM Stereo?

Don't run to your favourite AM/FM stereo sound box to see if you can catch a listen of it; and don't laugh, many unfortunate souls (this author included) diligently tuned their brains out without so much as a dB of separation to be heard. What you do get from your standard AM radio is an improved sound quality from AM stations broadcasting in stereo; this is because of the 'cleaning up' of the transmitted signal, a result of AM stereo stations upgrading their hardware all the way from the station to the transmitter. On a recent visit to CHUM radio's headquarters in Toronto, I was treated to my first real encounter with the new medium, and it was very impressive!

## Industry Happenings

CHUM's Director of Industry Relations, Duff Roman, enlightened me on the goings-on to date, and without repeating too much of what's already been said, here's a recap:

At present there are four different systems available for broadcasters to choose from when they decide to take the big step of conversion to stereo. The manufacturers involved are: Kahn Communications of New York, Harris, Magnavox, and Motorola. On the opposite end of the scale there is the consumer who has a current choice of at least

four known manufactures of AM stereo receivers: Sony, Sansui, Motorola, and Kahn Communications. At a glance there would seem to be no problem. The problem is though, that General Motors and their Delco components division have decided to go with the Motorola design for GM's AM stereo car radio. What's wrong with that? Well, lots. The signal produced by Motorola's AM stereo transmitter can only be decoded by a Motorola AM stereo receiver. The Japanese (Sony and Sansui) however, have developed a chip which will decode the above mentioned transmission systems, including Motorola's. With this in mind, we get into the intertwinings of why AM stereo is in limbo.



**Sansui's CX-990 AM stereo/FM stereo cassette player with a suggested retail price of \$720.**

## Who's On First?

Citing General Motors' share of the North American car market, it becomes clear as to why broadcasters are leery of sinking their fortunes into converting to stereo. With all those GM cars wheeling around with Delco radios (Motorola dedicated receivers) in them, AM stations would have to broadcast with Motorola transmitters if they wanted to be heard (in stereo that is). Freedom of choice in the marketplace becomes the foremost issue here. If a broadcaster feels that one of the four mentioned systems is better than another, he should be able to go with that choice, right? CHUM has taken this stand. After months of testing and comparing the systems, CHUM AM went on-line in September of 1983 with the Kahn system. Several other stations are also evaluating the various systems, but according to Roman, "...broadcasters are being extremely cautious with making a decision as to the system they choose in the event that they may end up with obsolete technology." It would seem that Motorola (and GM) are passively forcing AM broadcasters to adopt an industry standard which clearly benefits only those two players. Unfortunately, the one who is going to suffer the most from all this politicking is the consumer, who in reality is the end user of the radio product.

## Tuning In

Already on the market are a small number of portable AM stereo receivers from Sony, as well as a car radio from Sansui. Duff Roman introduced me to the Sony SRF-A100 FM stereo/AM stereo mini-portable receiver, and it was a very impressive unit. The sound quality of the AM stereo equalled that of any FM stereo signal around. However, while taking the bus home from work, I decided to indulge in some of the new improved AM, and instead was treated to amplified noise from the electrical system onboard the bus. This is a minor point which will hopefully be overcome in the future. The unit sells for around \$159 and is in short supply. Also, Sony has introduced another AM stereo/FM stereo receiver in the form of their popular Walkman radios and it is currently selling for around \$100.

On the advice of Mr. Roman, I contacted the people at W. Carsen Co., distributor of Sansui products, and was introduced to the CX-990 car stereo. The AM stereo sound produced by this unit was excellent and above all, free from any interference. To date, this is Sansui's only entry in the AM Stereo market.

According to a pamphlet published by Kahn Communications, their subsidiary, Kahn Consumer Products, also manufactures an AM stereo receiver.

The important thing to note about the products mentioned above is: they are all capable of receiving signals from any of the four available transmitting systems.

General Motors will be offering the Motorola AM stereo receiver as an option in the 1984 Buick line. Remember, that could be the deciding factor for AM stereo's rise or fall.

## The Future of AM Stereo

At this point in time, there is quite a bit of stagnation in the launching of AM stereo. Broadcasters are holding back, manufacturers of transmitters are vigorously trying to sell their individual systems, and the makers of AM stereo receivers are sitting back waiting to see if there is actually going to be a market for their product. Probably the most distressing point in all this is the lack of awareness of the existence of AM stereo. If the whole AM stereo issue continues to be veiled in secrecy, there is a danger that its fate may go the route of quadraphonic records. With more public awareness there is chance that this won't happen.

**ETI**



# Audio Test Set



IN ORDER to make comprehensive performance checks on audio equipment, a number of expensive pieces of test gear are needed, including such things as an AC millivoltmeter, a high quality signal generator, and filters for distortion measurements. Such an array of test equipment, even if home constructed, is probably not a practical proposition for most amateur electronics enthusiasts. But probably few people require such a sophisticated set-up anyway. For the majority of testing, all that is really needed is some sort of audio signal source, plus an audio signal tracer.

The unit featured in this article has a simple but very useful signal generator, plus an audio power amplifier for signal tracing. The signal generator covers a frequency range of under 10 Hz to over 100 Hz in four ranges: 10 Hz - 100 Hz; 100 Hz - 1 kHz; 1 kHz - 10 kHz; and 10 kHz - 100 kHz. Three output waveforms are available: sinewave, triangular and square. The sinewave output is the one that is required for general purpose testing, such as frequency response measurements. The maximum output voltage with the sinewave signal selected is nominally three volts peak-to-peak, or in terms of RMS voltage, just over one volt.

The squarewave output gives a similar peak-to-peak output voltage level, but the figure for the triangle output is higher, at about five volts peak-to-peak. However, a variable attenuator control enables the output to be continuously adjusted down to zero, and an attenuator switch allows the output to be reduced by 40 dB (a factor of 100). The latter is useful when trying to set very low output levels, and makes accurate adjustments of the variable attenuator much easier.

The output level remains almost constant over the full frequency range of the

---

**An easy to build all-in-one test set designed for fault finding on audio circuits. With the addition of a simple multimeter, this project will cover just about every audio test and measurement situation.**

---

unit, with variations being no more than about 1 dB. The unit has a low output impedance. The total harmonic distortion on the sinewave output is typically under one per cent, which is less than ideal for distortion measurement, but is more than adequate for most other testing, such as gain and frequency response measurements.

The audio amplifier section uses a very simple circuit based on a TBA820M integrated circuit, which is the only active device used in this part of the unit. The amplifier has a maximum output power of about one watt RMS into and eight ohm impedance loudspeaker, an input impedance of about 400k, and an input sensitivity of approximately 20mV RMS for maximum output power. This enables an output at reasonable volume to be obtained from even a low level signal such as the output from a microphone.


## Function Generator

There are two basic systems that can be used in a signal generator. One is to use a high quality sinewave oscillator, such as the popular Wien type, with a clipping circuit normally being used to additionally

provide a squarewave output. This system works well in practice, giving a very high quality sinewave signal, but it has the disadvantage of relatively high cost and complexity. The second method is to use a function generator, which is based on a system along the lines of the block diagram shown in Figure 1. This gives sinewave, triangular and squarewave outputs, but the oscillator at the heart of the system is a relaxation type that produces the triangular signal.

This signal is generated by charging and discharging a capacitor from a constant current source. As the current is constant, so is the rate at which the charge voltage on the capacitor rises and falls so that a triangular waveform of good linearity is generated. In a practical system, an electronic switch is used to control the charge/discharge cycle, and the charge/discharge currents are often controlled by separate circuits. A voltage detector is used to operate the electronic switch, setting it to the discharge mode when the charge voltage reaches a certain level, and then reverting to the charge mode when the voltage falls to a second threshold potential. In other words, a standard relaxation oscillator action.

The signal across the capacitor is at a fairly high impedance, and loading on the output could easily result in both a change in frequency and a degradation of the output waveform. A buffer amplifier is therefore included to ensure that excessive loading of the signal across the capacitor cannot occur. A variable resistor enables the charge/discharge current to be varied, and this acts as the fine frequency control. The operating frequency can also be changed by using different capacitor values, and using several switched capacitors enables several frequency ranges to be covered.

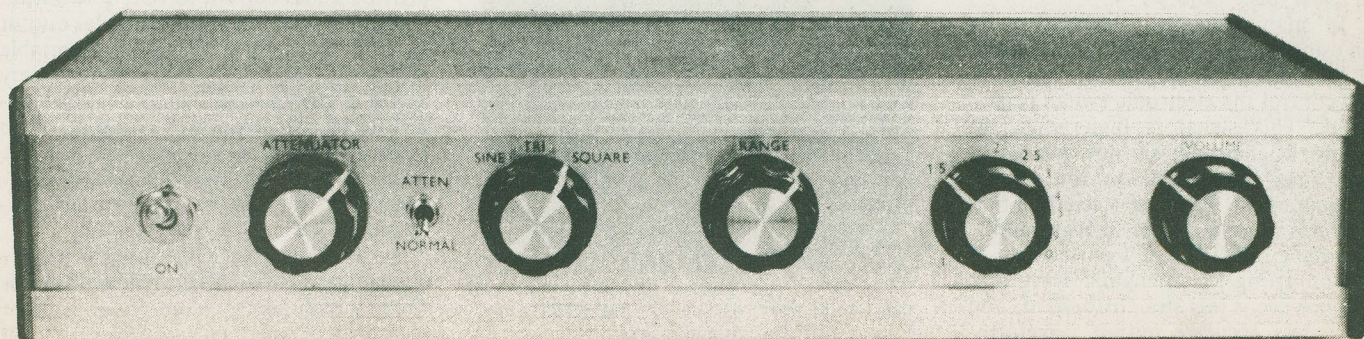



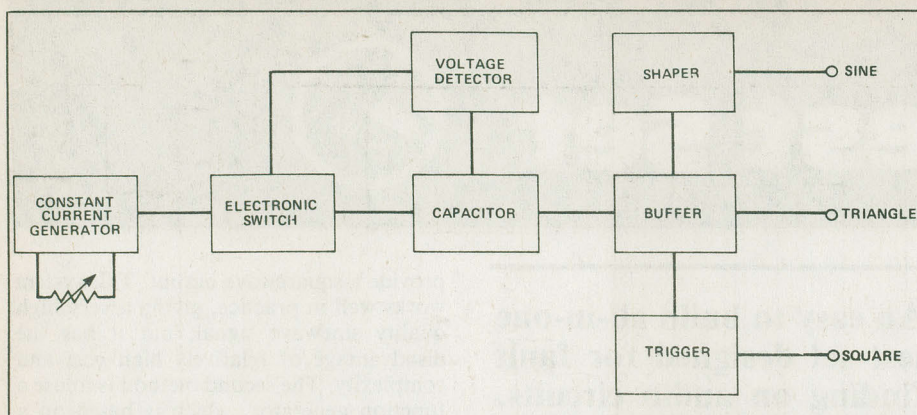


Fig. 1. Block diagram of the function generator — all this on one chip.

## Sine, Triangle and Square

It is quite easy to generate a squarewave signal from a triangular one; and it is just a matter of using a trigger circuit to clip the triangular signal. Figure 2 shows the way in which this system operates. If the triangular input signal goes above a certain threshold voltage, the output of the trigger circuit quickly switches fully positive. If the input signal goes below the threshold level, the output of the trigger almost instantly reverts to the fully negative state. Provided the correct threshold potential is utilized, exactly half way between the maximum and the mini-

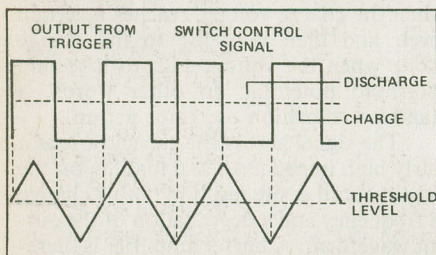


Fig. 2. Generating a square wave from a triangular signal is quite easy. As shown in the block diagram (left), a trigger circuit is used to square the triangle by switching rapidly between full positive and negative voltages whenever the triangle wave passes through a certain threshold voltage.



mum voltages of the triangular signal, the output from the trigger circuit will be a squarewave having an accurate one-to-one mark space ratio.

In many practical designs, rather than using a separate trigger circuit to provide the squarewave output, the signal used to control the electronic switch is used instead. This signal is high while the capacitor is charging, and low when it is discharging, giving an accurate one-to-one squarewave. Whether a separate trigger circuit is used or not, a high quality squarewave signal is easily generated.

Converting the triangular waveform to a sine wave is less straightforward, and gives a less accurate output waveform.

The system normally used is a non-linear amplifier which has a level of voltage gain that reduces as the input voltage on each half cycle rises. This reduction in gain rounds off the sharp peaks of both positive and negative half cycles, to give a reasonable sinewave output signal. Even using a fairly sophisticated shaping circuit, the distortion on the output is far higher than that produced by a high quality sinewave oscillator; but a good shaping circuit will give less than one per cent total harmonic distortion, which is more than good enough for most purposes.

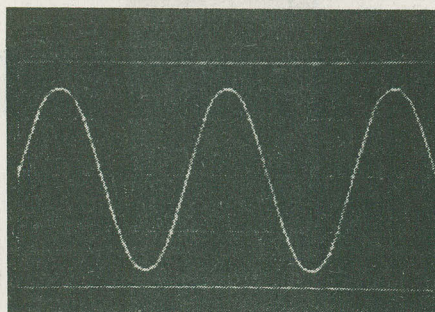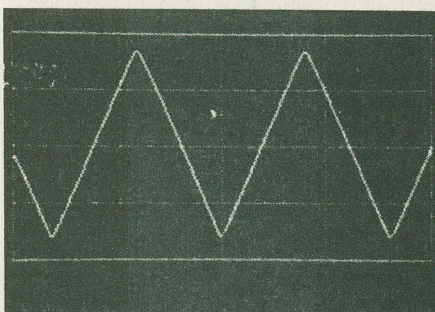The amplifier obtains its non-linearity by the inclusion of diodes (or transistors connected as amplified diodes) in the feedback network. At low output voltages, the diodes fail to conduct and the amplifier exhibits its full closed loop gain. At higher voltages, the forward threshold voltage of one diode will be ex-



The output waveforms, while not perfect, are good enough for most purposes.

ceeded, it will start to conduct, providing additional feedback and a reduction in the voltage gain of the amplifier.

In a practical circuit, a fairly complex diode/resistor or transistor/resistor feedback network is needed in order to give good results, so that the input voltage increases as more diodes are brought into conduction. Furthermore, separate networks are needed to process negative and positive output half cycles.

## The Circuit

From the above description, it will probably be clear that a function generator is a fairly complex piece of electronics. Fortunately, there are several function generator integrated circuits available, and a unit of this type can be constructed using one of these, plus a handful of discrete components. This unit is based on the XR2206 function generator integrated circuit, as can be seen from the circuit diagram of Figure 3.

The charge/discharge capacitor connects between pins 5 and 6 of IC1, and in this case four switched capacitors are used to give the unit its four frequency ranges. Variable resistor RV2 is the fine frequency control and C7 is a bypass capacitor for an internal circuit of IC1. The sinewave/triangular output is taken from pin 2 of IC1, and the output from this is normally the triangular waveform. The sinewave signal is obtained by connecting a resistor (R6) between pins 13 and 14 of IC1.

Rather than having separate amplifiers for the triangular output buffer and the sinewave shaping circuit, the XR2206 uses the same amplifier for both functions, and switching in R6 connects the shaping components into the feedback circuit of the amplifier. This resistor could be replaced with a preset resistor, which would then be adjusted to optimize performance, but results should be more than adequate using the specified (fixed) value.

The squarewave output is available at pin 11 of IC1, and R4 is used as the load resistor, which also reduces the amplitude of the squarewave signal to match that of the sinewave output. Switch SW1b provides the output waveform switching.

The purpose of R1 to R3 plus C2 is to provide a bias current to IC1. The output amplitude from the sine/triangular output can be controlled by using a variable resistor in place of R3, but this is not very useful in this case, as it does not give control over the squarewave output. This facility is therefore left unused, and the output level is adjusted by means of an ordinary volume control type variable attenuator, RV1.

The second IC, IC2, is used as a unity voltage gain buffer stage, which gives the circuit a reasonably low output impedance regardless of which output waveform is in



use. C8 provides DC blocking at the output of the circuit, while R7, R8 and SW3 are the -40 dB attenuators.

Unfortunately, the XR2206 does not work well from a nine volt supply, and a supply potential of about 12 to 15 volts is needed. Power is therefore obtained from two nine volt batteries in series via a 12 volt regulator, IC3. This gives a well stabilized supply and consistent results from the circuit.

## Audio Amplifier

Figure 4 shows the full circuit diagram of the audio amplifier section of the unit. RV3 is the volume control, and this also biases the non-inverting input of IC4 to the negative supply rail. C12 provides DC blocking at the input of the amplifier and prevents any DC component on the input signal from affecting the biasing of IC4.

Apart from RV3, all the biasing is provided by internal components. The additional socket at the input, SK3, is to enable an input signal coupled to the input to be taken out to another item of equipment if desired. This is not a second input and only one input signal should be coupled to the amplifier at one time.

Pin 2 is the inverting input of IC4, and there is an internal 6k2 feedback resistor between this and the output terminal of the device. Resistor R9 is a discrete feedback resistor, and the voltage gain of the amplifier is roughly equal to 6200 divided by the value of R9 (in ohms), or about 132 times with the specified value of 47 ohms. This represents about the highest voltage gain that can be used in practice, since higher gain could easily lead to instability and the audio output quality would probably be significantly reduced.

Capacitors C14, C16, C17, and R10 are all needed to prevent instability. The amplifier is powered from the stabilized 12 volt supply, like the signal generator section. It would be possible to have separate on/off switches for the two circuits, but as each one has a stand-by current consumption of a few milliamps, and most of the time both sections will probably be used together, this was not thought worthwhile and a single on/off switch is used.

## Construction

A metal instrument case, measuring about 300 x 160 x 60mm, is used for the prototype, but this is somewhat larger than is really necessary. However, it would be difficult to make the unit very much smaller than this, since a fair amount of panel space is needed to take all the controls and sockets, and internally there are additionally the component panel and two batteries to be accommodated.

The general layout of the unit can be seen from the photographs, and it is ad-

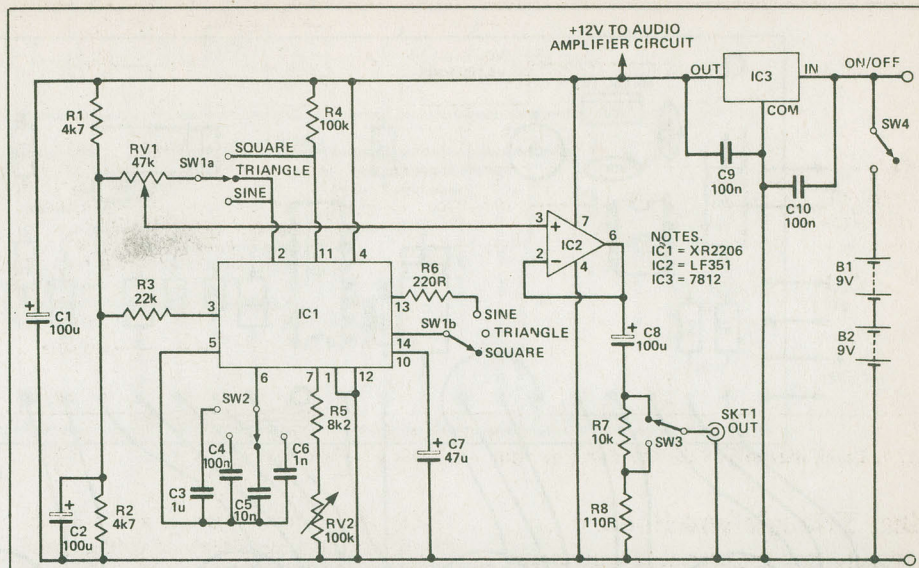


Fig. 3. Circuit diagram of the signal generator section, IC1 does almost all the work, with IC2 included as a buffer to give a low output impedance for all three waveforms.

visible to keep to roughly the same overall layout. The use of a metal case is strongly recommended as this will help to shield the audio amplifier from power hum and other sources of electrical interference. Details of the printed circuit board and component layout and wiring are provided in Figure 5.

Start by fitting the resistors, capacitors, and the single link wire. Close tolerance resistors and capacitors should be used where specified in the components list. Also C3, C4, C5, and C12 should be the specified polycarbonate (or sub-miniature polyester) type, if they are to fit onto the printed circuit board properly. Next, the four integrated circuits are fitted to the board; be careful to get them the right way round. IC1 is a fairly expensive device, and it is probably worthwhile using a 16 pin DIL IC socket for this, even if sockets are not used for IC2 and IC4. The audio amplifier IC3 does not have to dissipate much power and it does not require a heatsink.

Finally, Veropins are fitted to the board at the places where connections to offboard components will eventually be made, and it is then mounted on the base panel of the case. Spacers about 6mm

long are used to keep the underside of the board clear of the metal case so that there is no danger of accidental short circuits here. With the board completed and installed, it then only remains for the point-to-point wiring to be added.

This is shown in Figure 5, and it is completed using ordinary multi-strand hook-up wire or ribbon cable if preferred. The only exceptions are the two leads from the board to SKT2/3 and it is preferable, although not essential, to use shielded cable here to minimize static pick-up by the amplifier.

No ground connection to SK1 is shown, and in most cases this connection will be made via the case and the other sockets. Of course, if insulated sockets or a plastic case is used, it will be necessary to use an insulated lead to connect the ground tag of SK1 to the negative supply rail.

The unit is intended for use with an external loudspeaker, and a small, inexpensive, bookshelf type is ideal. Of course, if preferred, an internal loudspeaker can be fitted, but be careful to use a type which can take up an output of power of at least one watt RMS. Whether an internal or external loud-

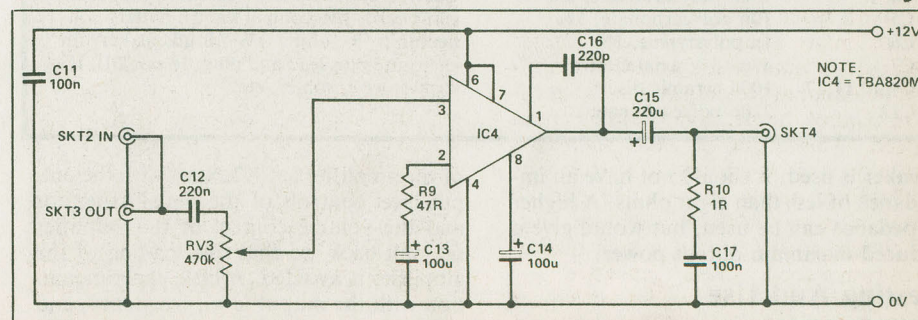


Fig. 4. The audio amplifier circuit. This section will prove useful for tracing signals, or testing small audio generator circuits.



## Audio Test

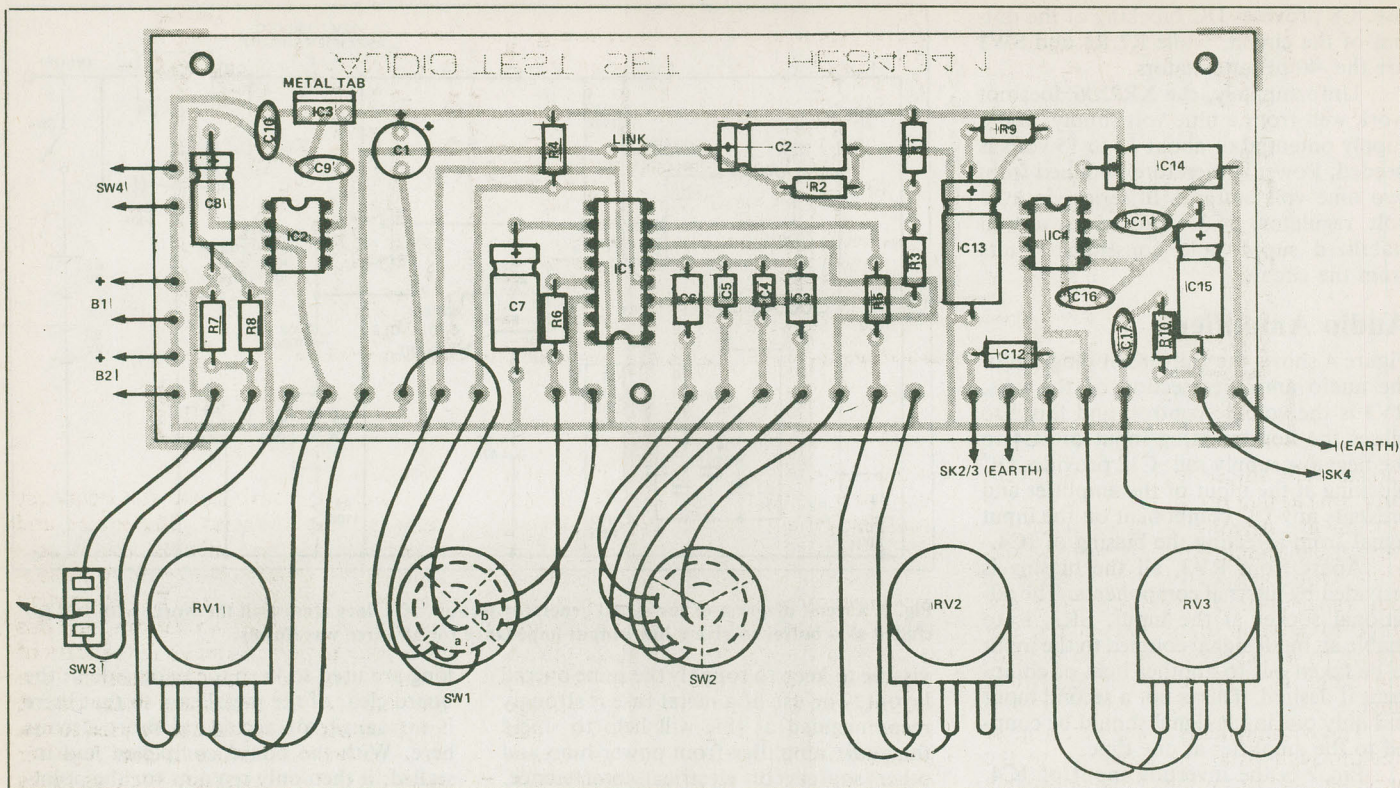


Fig. 5. All components, with the exception of panel mounted controls, fit onto a single small printed circuit board. Details of the connections from the PCB to the controls are also shown in the photographs below, and on the preceding page.

### PARTS LIST

#### Resistors (1/4 W 5% carbon except where noted)

R1,2	4k7
R3	22k
R4	100k
R5	8k2
R6	220R
R7	10k 0.5 watt 1%
R8	110R 0.5 watt 1%
R9	47R
R10	1R

#### Potentiometers

RV1	47k linear carbon
RV2	100k linear carbon
RV3	470k log. carbon

#### Capacitors

C1	100u 16 V radial electro
C2,8,13,14	100u 16 V axial electro
C3	1u polycarbonate, 5%
C4	100n polycarbonate, 5%
C5	10n polycarbonate, 5%
C6	1n polystyrene, 5%
C7	47u 16 V axial electro
C9,10,11,17	100n ceramic disc
C12	220n polycarbonate

C15	220u 16 V axial electro
C16	220p ceramic plate

#### Semiconductors

IC1	XR2206 Exar function generator
IC2	LF351 or TL072 JFET op-amp
IC3	uA7812 12 V 1A regulator
IC4	TBA820M audio power amp, Fairchild or SGS.

#### Miscellaneous

SK1,2,3,4	1/4" jack sockets
SW1	3 way 4 pole
SW2	4 way 3 pole rotary switch
SW3	SPDT miniature toggle switch
SW4	SPST toggle switch
B1,2	9 volt
Case	about 300 x 160 x 60 mm; printed circuit board; five control knobs; battery connectors; 8 ohm 1W loudspeaker in enclosure plus lead and plug; 16 pin DIL IC socket, wire, solder, etc.

speaker is used, it should not have an impedance of less than eight ohms. A higher impedance can be used, but would give a reduced maximum output power.

### Testing And Use

The obvious way of testing the unit is to couple the output from SK1 to the input

of the amplifier at SK2. Start with the output level controls of the signal generator and the volume control of the amplifier set well back, so that overloading of the amplifier is avoided. A little experimentation with the output level, frequency, and volume controls should reveal whether they are all functioning properly.


If an oscilloscope is available, this can be used to check the output waveforms. If not, set the frequency controls to produce a low audio output frequency and set SW1 for sinewave output. A sinewave gives a pure tone which does not contain any harmonics (signals at multiples of the fundamental frequency). This gives a very distinctive sound which should become more harsh when the unit is switched for triangle output. A squarewave has an even stronger harmonic content and consequently an even harsher sound.

For the signal generator to be of maximum use, a simple frequency scale should be marked around the control knob of RV2. If a calibrated signal generator is available, this can be used to provide reference tones against which the unit can be calibrated. Similarly, the unit is easily calibrated if you can gain access to a frequency meter which is suitable for audio frequency use.

In the likely event of neither being available to you, an alternative is to use a musical instrument to provide reference tones. For example, the G below middle C is at a frequency of 196 Hz, which is close enough to 200 Hz for most practical purposes.

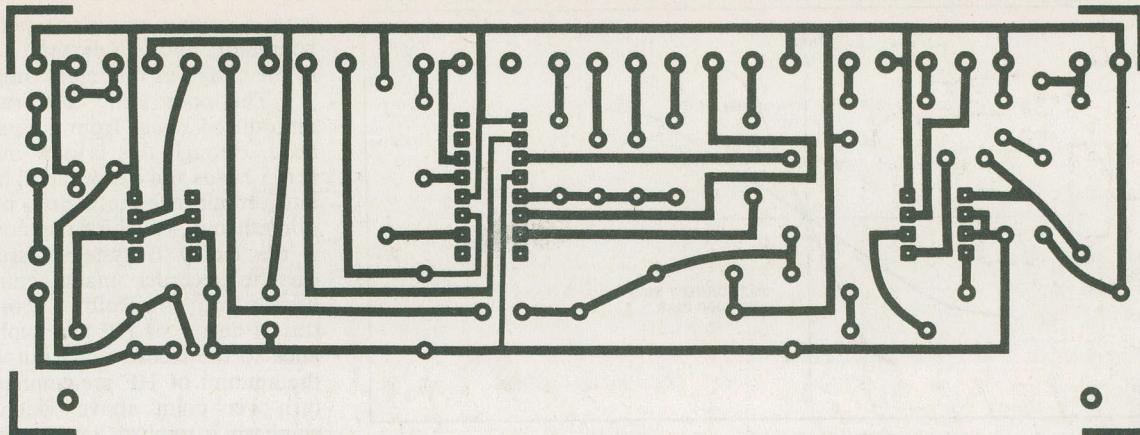The frequency control of the generator is set at the correct frequency by simply listening to the output of the unit





and carefully adjusting the control for the same tone as that produced by the musical instrument. Anyone with a reasonably musical ear should not find this too difficult. Only one scale is required for all four ranges, since switching from one range to another simply alters the frequency by a factor of ten, and a scale of one range is easily used on any other range.

There is inevitably a small amount of breakthrough from the generator to the amplifier, and this will be most noticeable when the generator is set for a middle audio frequency. When the amplifier is connected to a single source, this


breakthrough will almost invariably disappear completely, and it is not something that should be a problem when the equipment is in use.

In order to make frequency response measurements, some form of audio level indicator is required, and an AC millivoltmeter would normally be used for this. A simple alternative is to use an ordinary multimeter switched to a low AC voltage range, as most power amplifiers and preamplifiers can produce a high enough output signal level to drive a multimeter, most of which have a flat response over and beyond the audio frequency range. Beware of some digital instruments,

though.

Use a sinewave signal for frequency response measurements. The square and triangle outputs are of most use in conjunction with an oscilloscope. A square-wave signal can be used to test equipment for instability on fast waveforms, and this instability usually shows up in the form of a high frequency signal modulated onto the output of the equipment under test. A low level triangle signal can be used to test for cross-over distortion in class B power amplifiers. This manifests itself as kinks in what should be the straight lines of the triangular signal.

ETI

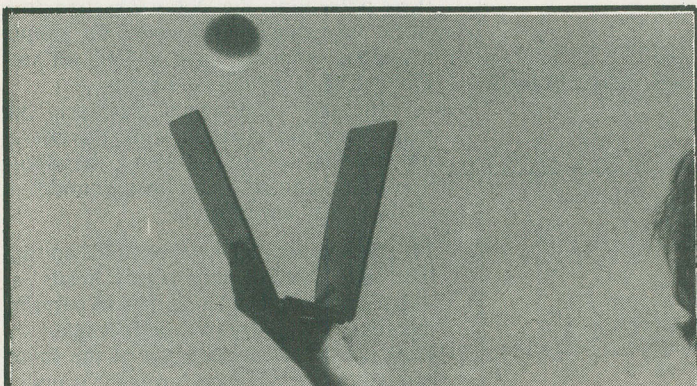

### Catcher's Mitt/Magazine Binder

Ah, summertime. You've worn out the old mitt already with heavy duty service down at the sandlot, and it's time for a replacement. With just such a predicament in mind, we offer the ETI Catcher's Mitt.


Sturdily made from vinyl and chromed metal, it has been field-tested and is guaranteed to catch at least three out of ten balls if they're thrown into it slowly and carefully.

Rained out? Cold weather coming? We're ready for that, too. They also will hold 12 issues of Electronics Today; a diabolically clever spring arrangement holds the magazines without cutting or punching. In addition, for no extra charge, we print on the spine: Electronics Today, Computing Now!, or Moorshead Publications.

They're available postpaid for \$9.25 — don't forget to specify the one you want — and Ontario residents are required on pain of death to add 7% provincial sales tax. Send to:

Moorshead Publications Binders  
Suite 601, 25 Overlea Blvd.  
Toronto, Ontario M4H 1B1

## ETI NEXT MONTH

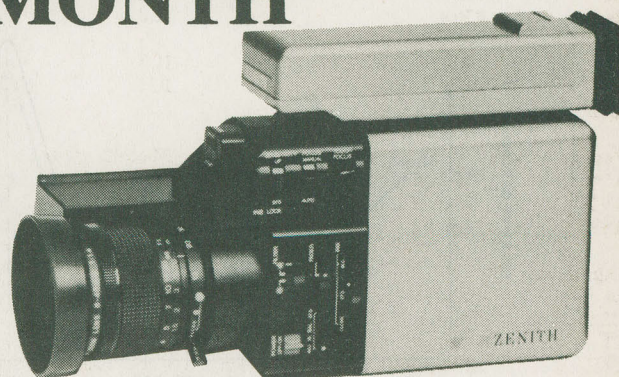

### A Look At Video

An update of some of the new miniaturized video equipment.

### Video Distribution Amplifier Project

Hook up to five video units together without interference.

### Project Bonanza

Ten short projects to keep you busy.

### Getting the Best From Your Oscilloscope

Operating hints and tips.



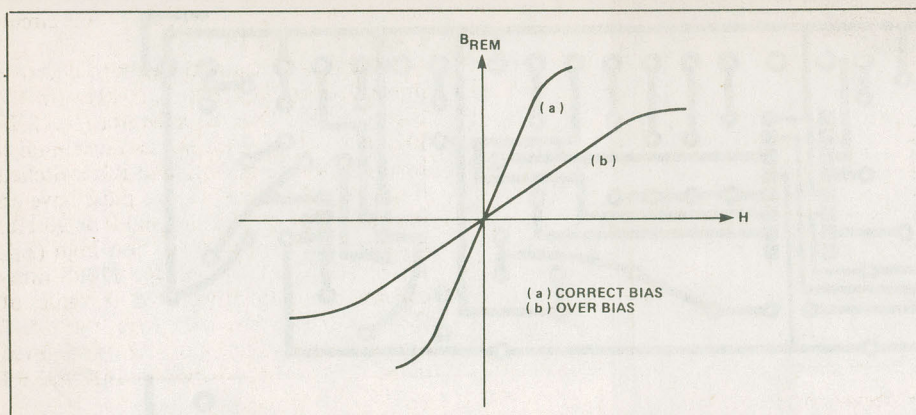


Fig. 10. The effect of HF bias on tape magnetization linearity.

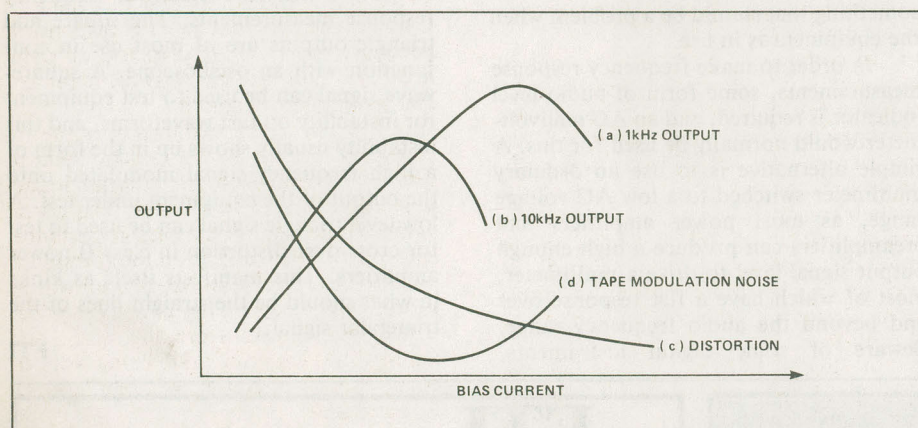


Fig. 11. How recording characteristics vary with bias current; note that only curves a) and b) are to the same scale.

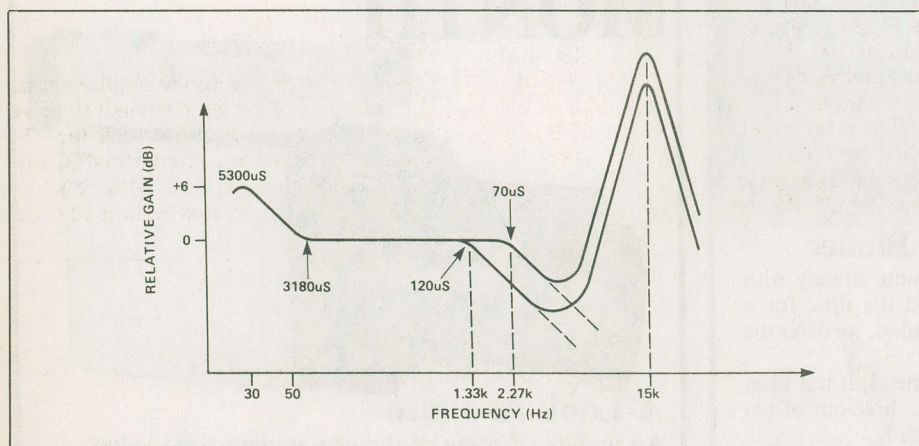


Fig. 12. Record pre-emphasis and de-emphasis for cassettes, showing additional compensation for head losses.

listening to the background noise on a bulk erased tape, as bought, and after it has been 'erased' by one's own recorder following the recorder of a zero signal.

The output from the tape recorder will depend on the tape speed and (although not discussed so far, this is a fairly logical extension of the arguments

above) on the tape width at the head. So, the the lower the tape speed and the narrower the tape head width, the worse the signal to noise ratio will be. This becomes a particular problem with cassette recorders, where the tape creeps past the head at 1.875"/sec., and the track width is only 30 thou. or so anyway. The signal output

from a cassette recorder replay head will be minute, and will demand a lot of skill in the design of the replay amplifier.

The poor basic S/N ratio of the reproduced signal from a cassette replay head, (though this is now improved by better heads and better tapes) has brought into prominence the various noise reduction schemes, of which the most common is the Dolby B system, used by most cassette recorder manufacturers under license from the Dolby Laboratories. In this, a degree of HF pre-emphasis is applied to the record signal, in which both the amount of HF pre-emphasis and the turn-over point above which this pre-emphasis is applied, is automatically adjusted in response to the measured level of the incoming signal. The reverse compensation is applied on replay to restore a flat frequency response.

There is a snag of course. This is that unless some means is provided for monitoring the tape output, which is only possible on relatively expensive three-head cassette machines, some assumptions must be made by the cassette recorder manufacturer, in setting up the Dolby B replay operating levels, about the actual signal level which his recorder will give on replay for a given input recording level. This will depend on the actual tape chosen by the user, and on the appropriateness of the bias setting. Nevertheless, in spite of these objections, the Dolby B system does work surprisingly well, even on simple machines, and can give a 6-10 dB improvement in overall S/N ratio.

In many commercial machines, the replay amplifier is muted while the tape is not moving, to avoid drawing the attention of the listener to the background hiss of the replay amplifier.

**11. Head losses:** We have assumed so far, that the recording and replay heads — which are often the same unit in cassette recorders — behave in a perfect manner. They don't. Mainly because of the finite gap width, their HF performance is poor. This means that some form of HF pre-emphasis has to be applied, during recording, to assist in achieving a satisfactory HF output. This recording pre-emphasis, of 15-25 dB magnitude, will be applied, as shown in Fig. 12, at the point where it is expected that the replay HF response will start to fall. This is not a good thing, since it will tend to cause HF overload, and increased distortion and intermodulation effects, but is feasible because signal amplitudes at HF are generally low.

## Practical Circuit Design

We have seen from the above what some of the problems are in tape recording. Since these are exaggerated in cassette recorders because of the narrow low-speed tape tracks, a look at the design of the electronics in a cassette recorder — ex-



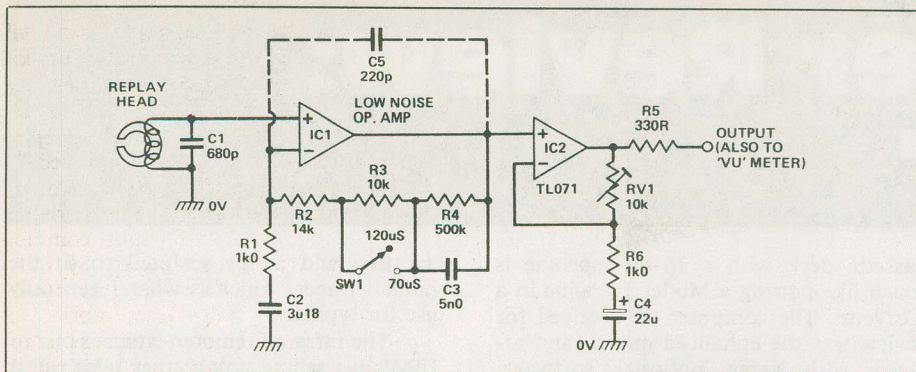


Fig. 13. A typical cassette replay amplifier giving the frequency response shown in Fig. 6.

cluding the Dolby processing — will show the types of circuit layout which will be needed in all these systems.

## Replay Amplifier

The overriding consideration here is of low noise in the amplifier, since the input signal will only be about 0.5 mV, and a 60 dB S/N ratio will demand an effective input noise of 0.5 μV, from the amplifier and input circuitry. Fortunately, the effective bandwidth of the replay amplifier, because of its downward slope with frequency, is only 1 to 2 kHz. Nevertheless, this necessitates an effective input resistance of only some few thousand of ohms. We must be careful therefore, that we do not needlessly include input resistive components, to add to the 300-600 ohms of the head winding resistance. The required equivalent input noise resistance required by the desired S/N ratio does put most of the audio ICs out of consideration; however, there are a few, such as the Signetics/Mullard NE5533/5534, the Precision Monolithic/Raytheon OP27, and the Hitachi 12017, which would be satisfactory electrically. Of these, the latter has a non-standard base connection, which would make it awkward to substitute,

whereas the ICs with the standard 741 type connections could be upgraded as better devices appear.

In commercial units, for reasons of economy, it is customary to use the same amplifier for both record and replay, with appropriate component changes accomplished by multiple switching. However, from the point of view of the amateur constructor, and certainly for the ease of explanation, it makes life easier to show the record and relay circuits as separate entities. I have shown a suitable circuit design, based on a low-noise op-amp, in Fig. 13.

In this circuit, the output of the replay head (through suitable switching if it is combined with the record head) is taken directly to the input of IC1. The gain-frequency characteristics of this stage are determined by the RC network in its negative feedback loop. Referring back to Fig. 6, we see that the LF gain is rolled off at 50 Hz (a 3180 μS time constant), at a gain of 500. From this we can infer that the total resistance in the feedback path, from output to -ve in, must be 500K, if R1 is 1kΩ. Also, the time constant of R1C2 must be 3180 μS. If R1 is 1kΩ, then C2 must be 3180 nF or 3.18 μF. This shows how simple the use of 'time constants'

makes the task of working out circuit component values.

Now, we require the gain to decrease linearly from 50 Hz to 1.33 kHz (in the case of the 120 μS equalization) or 2.27 kHz (for 70 μS). This we can accomplish by means of C3 and R2 and R3, switched by S1. If C3 is 5nF — this must have an impedance greater than 500 k at 50 Hz, but we can't afford to go too high ( $Z_{C50}$  for 5nF is 636k) — then the 120 μS time-constant will be given for a value of R2 + R3 of  $120/5 = 24k$ . Also, the 70 μS time constant will require R2 on its own, to be  $70/5 = 14k$ . So R2 = 14K and R3 = 10K.

IC2 is a simple output buffer stage, to give an adjustable gain of 1 to 11, depending on the setting of RV1. R5 gives some output isolation, and the value of C4 is chosen so that the LF response is adequate. Since 3.18 μF gives a -3 dB point at 50 Hz, 22 μF will give a -3 dB point at 7 Hz, which is low enough.

A small circuit refinement is the inclusion of C1 across the cassette head to tune the head, with its internal inductance, to some 15 to 18 kHz. The actual value will depend on the head inductance, and can be calculated from the formula  $f^0 = \frac{1}{2} LC$ . A value of 680-820 pF will be in the right order. This limits the wide-band noise output from the head, and reduces the chance of noise being worsened by cross-modulation within the input IC amplifier.

C5 across the first amplifier stage performs a similar bandwidth limiting function. This may not be acceptable for the NE5533 or 5534, so regard it as an option.

## Record Amplifier

This has to meet five design requirements. The output must be large enough to drive the cassette record head through the 47k swamp series resistance. A normal IC op-amp will do this quite well, with very low distortion, when operated from ± 12 or 15

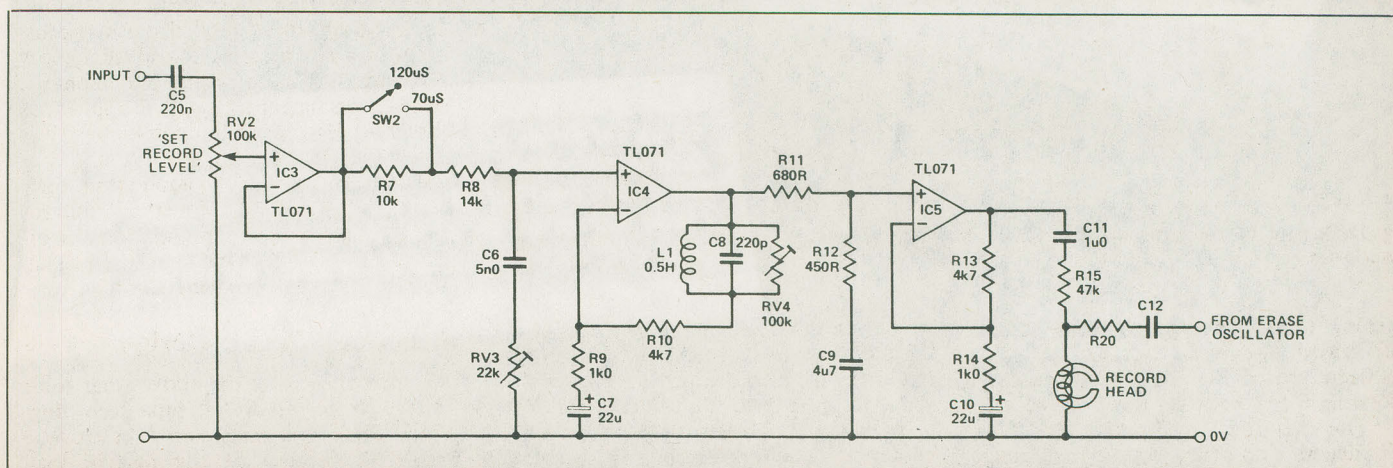


Fig. 14. A typical cassette record amplifier giving the frequency response shown in Fig. 12.

continued on page 52



# Computer Review: IBM PCjr

The PCjr is being offered as a low-cost way to get into the world of 16-bit PC-DOS. ETI looks at the advantages and disadvantages.

---

By Bill Markwick

---

SEPTEMBER already? But summer just got here... Ah, well, in the fall your fancy may lightly turn to thoughts of buying a computer, particularly one for the back-to-school bunch, and you can't have missed the ads for the PCjr now that its price has been reduced. At the time of writing, you can get the enhanced version with 128K and a single disk drive for \$1549; the basic model with 64K and cassette ports is \$998, though using a

cassette deck with a 16-bit machine is much like putting a Model T engine in a Corvette. The computer we received for review was the enhanced model, and arrived with some optional software: PC-DOS, Cartridge BASIC, and the Writing Assistant word processor. We also tried out the PCjr Compact Printer.

## Unwrapping

The first thing you'll notice as it emerges into the light is the keyboard. It has no cable, being linked to the console with infrared beams, and it has keys that are only one step above the eraser types you find on bottom-of-the-line home computers. You may have read elsewhere that the keyboard is a real turkey, so let's get the pessimism over with right away: it's a real turkey. The key spacing is that of a full-sized keyboard, but the keys themselves

are tiny and aren't sculpted to fit the human finger, which is what I generally use for typing.

The infrared remote feature is one of IBM's big selling points; they even call it the 'Freeboard'. It worked flawlessly and wasn't too fussy about angles, but the keyboard cable is last on my list of computer annoyances that need fixing up. Besides, you'll eventually have to buy four 'AA' cells or eliminate them by buying IBM's optional cable.

Another economy measure which may annoy some people is the use of various shift functions to minimise the number of keys required; for instance, many of the keys have three functions as selected by the Shift, Alternate, Control, or Function keys. If you're a slow typist, you'll find that these various combinations delay you even more.



August 1 — as we went to press, IBM Canada has announced changes to the PCjr: a proper keyboard, an "electronic disk" program, a speech synthesizer, and others. The enhanced version lists at \$1569.



There. That's the nasties over with. Now for the good stuff:

## Powering Up

The console is small and light; on the front is the 5 1/4 inch 360-kilobyte single-sided drive and two cartridge slots, along with a small hole for the infrared receptor. On the back are connectors for two joysticks, a lightpen, a keyboard cable (if used), an RF output, a video output, an audio output, a direct graphics output, and the power socket. There are also ports for a cassette deck, an optional modem, and a printer.

The power supply is a separate black box that sits on the floor and provides enough current for one disk drive; it has to be upgraded if you add another (IBM has no second drive available at the moment, but there are independent suppliers who do). When you power up, the start-up ROM looks for a disk or cartridge; if there isn't one, it boots up with the internal BASIC and announces that there are about 63 kilobytes free. The rest is used up by BASIC itself and by a comprehensive ROM; we'll get back to some of the built-in features. The RAM is expandable to 640K.

If the first key you press after booting is Escape, the PCjr's ROM starts a program called the 'Keyboard Adventure', a tutorial for children that lets them get used to operating the keys. Otherwise, you are now in cassette BASIC, written for IBM by Microsoft. Its syntax is similar to other Microsoft versions, except that it has wonderful full-screen editing; just cursor up and correct. There's even an 'Insert' key on the keyboard to eliminate the EDIT-I-ESC format beloved by Microsoft.

The cassette BASIC lacks many of the audio features and extended graphics available on the cartridge version. It's more than adequate for most programming needs, but for the real bells and whistles, you'll need to buy the optional plug-in.

## Cartridge BASIC

Most computer makers caution you not to fool around with any cartridges if the power is on because dire things are said to happen. On the PCjr, they even encourage it; nothing happens but a system reset. The extended BASIC that comes on is comprehensive indeed. It has all the familiar commands, plus a graphics package of amazing flexibility. The sound functions include the usual PLAY and SOUND commands, but the notes generated can be held in separate buffers, allowing multiple voicings. Both the graphics and the sound functions are difficult to learn, but the payoff is in the remarkable quality of the programs you can produce.

The manual which comes with the cartridge is hard to understand and contains some typographical errors just to add to the fun; the typos got in because they have had the example listings typeset instead of photographing a computer printout.

## Exploring

A demonstrator disk is included, called 'Your IBM PCjr Sampler'. It's a collection of twelve simple programs, such as an alarm clock, a typewriter, a monthly expense account, and so forth. You'll get to see some of the remarkable graphics capabilities of a 16-bit machine. Some of the games are fun, too.

Another included disk is 'Exploring the IBM PCjr'. This one should go a long way toward discouraging people about computers; it's basically a case of the computer programming the operator. The keyboard demonstrator, for instance, invites you to try changing the display via the cursor keys; nothing happens until the computer feels that it's good and ready. The graphics in the DOS explanation may appeal to some.

## DOS

The Disk Operating System is like the steering wheel and foot pedals of a car: it gives you complete control over your disk files. Using simple commands, you can view, load, save, and delete files; these can be languages such as BASIC, games, text, or anything that fits on a disk. Using more complex commands, the experienced computer fan can rearrange parts of the computer's memory or disk files, write programs, shuffle files around, and more. The PCjr uses the same operating system as its larger cousin: PC-DOS, one of the implementations of MS-DOS. It's very similar to the workhorse CP/M, and most of the commands will look the same to the operator, but it's considerably enhanced over the 8-bit version.

The next obvious question will be: how compatible is the PCjr with IBM-PC software? It's difficult to pin anyone down on this, but the general answer is that any PC software will run within the limits of the installed RAM, assuming that it doesn't insist on dual drives. Much MS-DOS software is compatible as well. Keep in mind that you must purchase the DOS package before you can run a lot of software; many programs do not have DOS tracks on their disks. The DOS disk is run first, loading its commands into memory; the disk is then removed and replaced with the software program. IBM has a PCjr brochure which lists software compatibility and whether or not DOS is required.

The PCjr solves the problem of having only one drive by faking a dual system: if you type B: for the second

drive, the B: actually appears on the screen. This is your cue to remove the first disk and replace it with another. CP/M users note: you can swap PCjr disks back and forth to your heart's content with nary a read-only message.

One of the great advantages to both CP/M and PC-DOS is ease of use for beginners. File handling becomes a breeze compared to the low-end micro systems. This isn't true as you delve deeper into the mysteries of programming, but you only need go as far as you want to; first-time users should get along fine with PC-DOS.

Computer hackers upgrading to 16-bit will be pleased to know that most of the Debug utility is virtually identical to CP/M's DDT (and you can write corrections to the disk!). Unfortunately, there was no assembler program included with the DOS package, though you can do a sort of mini-assembling using Debug in a way similar to the DDT 'A' command.

## Back to BASICS

Before continuing with the operation of the software, let's have a look at some of the keyboard functions waiting for you in ROM. Lots of things are hiding in that 64K worth of chips. The first thing you'll notice when you boot either version of BASIC is five commonly used commands at the bottom of the screen (LIST, RUN, etc.). These, and five others, are selected with the function keys; to save on the number of buttons, IBM has used the numerical keys and the Function button to implement this feature. The screen listing of the functions can be suppressed with F9 and the word 'OFF'.

Some of the alphabetical keys have been assigned functions as well: PAUSE replaces the usual Control-S, BREAK replaces Control-C, and the Control-P printer toggle is now ECHO. There's also a key function to print the screen display. The cursor keys can be turned into end-of-file and page-at-a-time scrolling. All function keys can be user-defined using the KEY command; each key will hold a 15-character string.

There's yet another: the ALT key. Its only purpose seems to be adding four punctuation marks, aside from its involvement in implementing a fail-safe RESET: this requires the Control-ALT-Delete keys to be pressed simultaneously; you really have to have your heart set on rebooting.

WIDTH 80 will give you an 80-column screen in BASIC. If there's a way to call this font with other software, such as the word processor, I couldn't find it.

Without kicking this poor keyboard while it's down, I'll point out once again that the rubbery action, the tiny keys, and the multiple functions make this a prize pain for typing. It's also designed for



## Computer Review

overlay sheets to suit various software, and therefore the legends are printed above the keys rather than on them; this makes for much peering over the edge.

### DOCs

The PCjr comes with a reference manual and BASIC tutorial; all other software is extensively documented via three-ring binders crammed full to the brim with all sorts of information. Unfortunately, the value of documentation is not measured by the kilogram, and most users are likely to find themselves on quite a wild goose chase if they need to find a specific instruction. IBM's documentation style is to start off with the painstaking tediousness as you whip over page after page looking for something else. Then the complicated points are crammed in to the last few pages; see the printer description below as an example.


### Software

One of the best selling points of the PCjr is the ability it gives you to buy into the vast quantity of software that's been generated both by IBM and others. Our review model came with cartridge BASIC, the Writing Assistant word processor, and sampler disks for the Graphing and Filing Assistants.

The Writing Assistant requires you to load DOS first, and then the program disk. This takes about 60 seconds; the 8088 16-bit system is not particularly fast in either disk loading or screen refresh time. Once into the editing mode, you'll find a 40-column display with auto word-wrap. You can reset the margins to a maximum of 78 using the Define Page function, but only 40 characters display at once; horizontal scrolling is required.

The program certainly contains all the features required for fancy word-fiddling; the function (and shift/function) keys are reset to the commonly-used commands such as tabs, erase word, erase line, copy, append a file, and 13 others. There's the usual Search and Replace, and a spiffy Spelling Checker with a huge vocabulary and an unusual ability: on finding an unknown word, it can offer the possible spellings that it thinks might be correct. When it came to 'Plork', for instance, it offered the possibility that it might be 'Polar', 'Polka', or 'Porkers'. It can then replace the word in the text, or if you prefer, write your peculiar word into the dictionary for future reference. Lots of fun, if a bit slow.

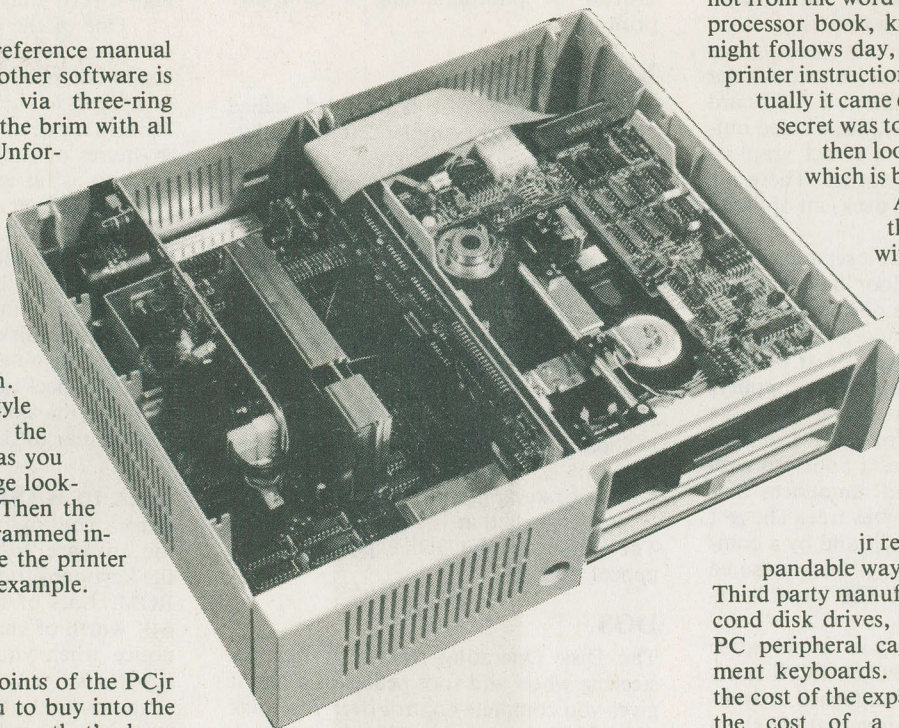The other software was on a par; the Graphing Assistant only required a list of



categories and numbers to turn them into bar charts, graphs, or pie charts. Easy as, ah, pie. Filing Assistant is a database suitable for keeping track of information and generating reports.

### The Printer

The IBM Compact printer is a suitable peripheral for the PCjr, being a 50 character per second unit that sells for \$259. It prints with a dot-matrix on thermal paper; this eliminates the need for ribbons, and IBM's paper produces a nice high-contrast image with no problems caused by photocopier heat, although it's only coated on one side.

The printer had no controls other than Paper Feed, not so much as a roller knob; paper is poked into it, the Paper Feed is held down, and the paper trundles around the roller. There are four modes available: standard text, compressed text, double-width text, and underlining. How we found this out was a good example of IBM's frustrating documentation.

There were no instructions with the printer, so we dug through the computer's Guide to Operations, which contains the instructions for all sorts of optional equipment. Getting the paper in, seemed self evident, so the search was on for the procedure to make the Writing Assistant print in the various modes. However,

IBM sees fit to use no less than 16 pages of text and diagrams on how to insert the paper. Then the control code explanation begins: it contains some garbled hints on how to change modes from BASIC, but not from the word processor. I opened the processor book, knowing that as sure as night follows day, it would say 'See your printer instructions,' and so it did. Eventually it came down to guesswork; the secret was to type an asterisk/P and then look up an ASCII number which is buried in the text.

Aside from these gripes, the printer works silently with sharply defined characters, though it does leave a high-gloss sheen on the paper where the printhead touches it.

### Finally

With exception of the keyboard and the poor manuals, the PCjr represents a powerful, expandable way to get into PC software. Third party manufacturers are offering second disk drives, expansion slots to hold PC peripheral cards, and even replacement keyboards. You'll have to tote up the cost of the expansions you want versus the cost of a full-size PC or PC-compatible.


### Quick Reference IBM PCjr, enhanced version

**Price:** \$1595  
**CPU:** 8088  
**RAM:** 128K, expandable to 640K  
**ROM:** 64K  
**Screen:** 40 x 24 (80 x 24 in BASIC)  
**Graphics:** 6 modes up to 640 x 200  
**Colour:** 16 in low or medium resolution  
4 in high resolution  
**Sound:** internal speaker, external jack  
**Printer I/O:** 1 serial port  
**Display Outputs:** RF and video

ETI


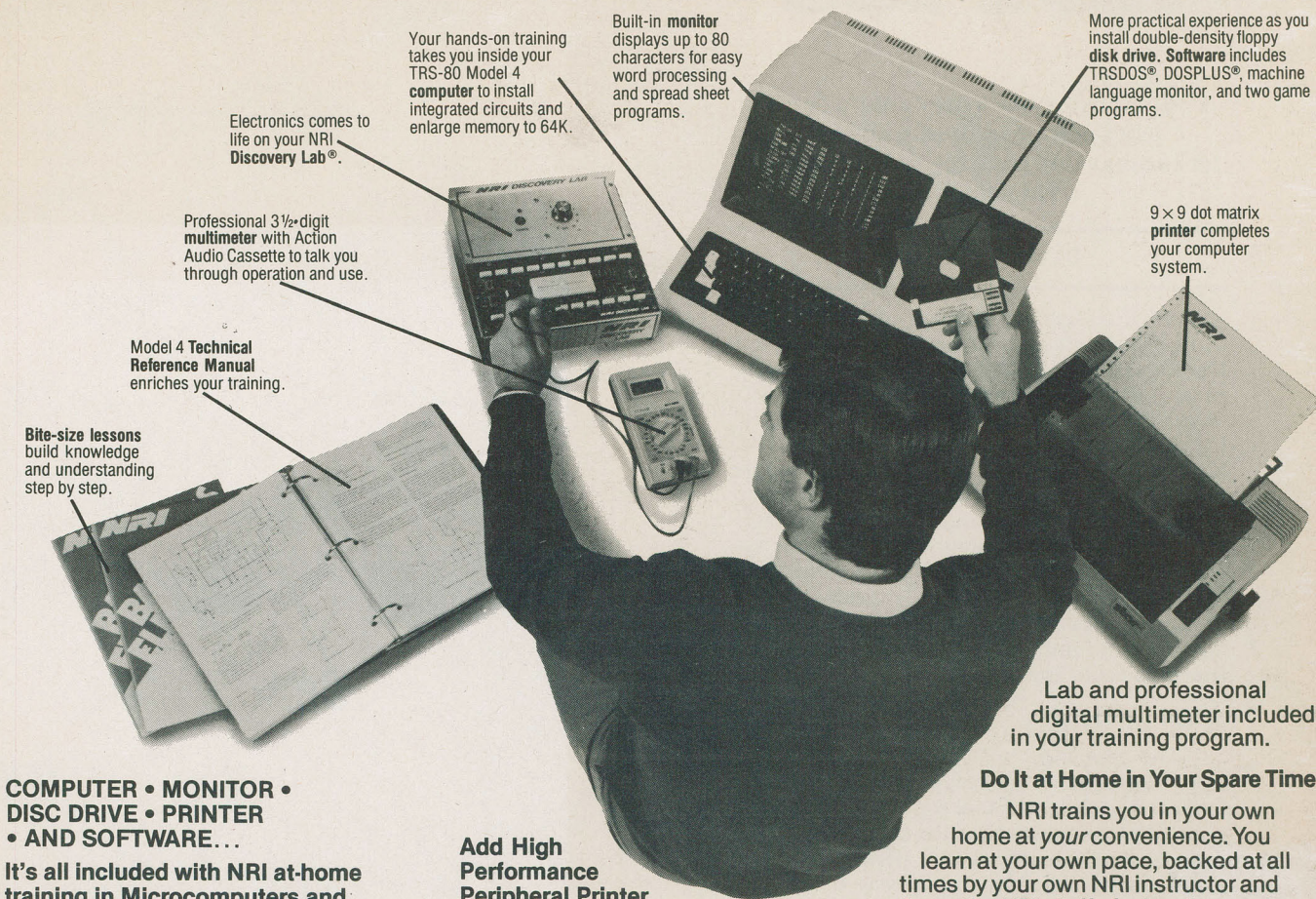
# ONLY NRI GIVES YOU TOTAL COMPUTER SYSTEM TRAINING



## COMPUTER • MONITOR • DISC DRIVE • PRINTER • AND SOFTWARE...

It's all included with NRI at-home training in Microcomputers and Microprocessors. And *only* with NRI training.

If you really want to learn how to work on computers, you have to learn how to work on computer systems. Only NRI includes a complete system with your training...total training that gives you hands-on experience with computers, peripherals, and software. Training that builds the knowledge, skill and confidence you need to become a computer professional.

### Get Inside the Famous TRS-80 Model 4 Computer

Learn programming techniques for troubleshooting...go inside to expand its RAM to a powerful 64K...even install a double density floppy disc drive.

You'll become familiar with computer languages...BASIC, the most popular microcomputer programming language, and machine language for diagnosis and repair work. You'll run software that demonstrates computer operation, even learn to do your own programming. You'll become proficient at modifying programs to fit your business or family computing needs.

### Add High Performance Peripheral Printer

Only NRI gives you a total system training by including the flexible Gemini 10X printer as part of your hands-on learning. Working with it, you'll get practical experience in adding peripherals, learn maintenance and servicing operations. And you'll use it for hard copies of important programs, business records, and word processing.

### Understanding Built On Experience

You start with the basics, rapidly build on the fundamentals of electronics with bite-size lessons to master advanced concepts like digital logic, microprocessors, and computer memories.

You'll reinforce this new understanding with hands-on, practical demonstrations and experiments that give you real-world experience and build almost intuitive skills. You'll use the exclusive NRI Discovery Lab® to see what makes transistors tick, build and test working electronic circuits that duplicate key computer circuitry, construct digital logic circuits that demonstrate computer performance. And, you'll probe into the very heart of your computer using the Discovery

### Do It at Home in Your Spare Time

NRI trains you in your own home at *your* convenience. You learn at your own pace, backed at all times by your own NRI instructor and the entire NRI staff of educators and engineers. They're always ready to answer questions and help you over the rough spots to keep you moving toward your goal.

### Free Catalog Tells Much More... Send Today

See all the interactive training equipment you get in this state-of-the-art course in today's technology. Look over the lesson outlines and descriptions of the exciting experiments you'll perform. And look at other high-tech career fields like Robotics, TV/Video/Audio Servicing and Data Communications.

Mail the postage-paid card today to see how NRI can give you the skills and confidence you need to start a good-paying career as a microcomputer technician. If the card has been used, please write.

**NRI SCHOOLS**  
McGraw-Hill Continuing Education Center  
330 Progress Avenue  
Scarborough, Ontario M1P 2Z5  
or telephone 416-293-8787

**We'll give you tomorrow.**

TRS-80 is a trademark of the Radio Shack division of Tandy Corp.





# Hot Ice

**A short history of remote data sensing leads into a look at Canada's technology for tracking ice movements via satellites.**

**by Roger Allan**

REMOTE sensing is customarily argued by those of us in the west to be traceable back to Signior Galileo Galilei's attempt to snow the Venetian Senate into granting him research money (for 'research' read 'grocery') by falsely presenting the Dutch discovery of the telescope as a product of his own fertile mind. While he intended to use the funds to subsidize his own work in astronomy (permitting him to make one of the most wonderful statements to an assistant ever: 'Do you know what the Milky Way is made of? I do.'), the Venetian Senators took a far more pragmatic view of the device, for it would permit them to spy the mast heads of unfriendly shipping before the unfriendlies could spy them.

## A Bit of History

The permanent recording of remotely sensed data, however, has a far more ancient lineage. The classical Chinese developed an earthquake detector which took the shape of a bronze frog. Carefully balanced in a necklace arrangement around the frog's neck was a series of bronze balls, each about the size of a cherry. Located directly underneath these balls was a series of bronze cups, and the entire device was mounted on a heavy stone pedestal several feet off the ground. When an earthquake occurred, the frog would 'shudder' or 'sway' in a line parallel to the movement of the earth, knocking two balls on opposite sides of the frog off into the cups. By having two such devices some miles apart connected by Imperial despatch riders, the local governor could use triangulation to determine if the earthquake's epicentre was within his jurisdiction, and if so, rescue attempts could be sent to the afflicted area.

More recently, the development of the camera in 1822 provides a Modern Era start to the history of remote sensing with permanent data acquisition, though it was not until 1856 with the coupling of a camera and the hot air balloon that real remote sensing producing a permanent record can be said to have begun. The first such instance of balloon aerial photography occurred over the city of Paris. Nine years later, such methods became increasingly used, particularly by the Union Forces during the American Civil War.

The next milestone came when Wilbur Wright photographed Rome from an airplane, predating by five years such a technique's widespread use by the military during the Great War.

A portion of a plot depicting the Labrador coastline with pertinent "hot ice" data in the form of isobars.



The intervening decades between the Great War and the 39-45 War saw a rise in the use of remoting sensing abilities, primarily based on the ever-increasing knowledge of the intricacies of electronics: radio direction finding, improved seismic detectors, and acoustic detection.

The German Kriegsmarine used a submarine to place a series of battery-operated wind, rain, temperature and barometric pressure devices on the coast of Labrador, automatically connected to Germany by radio. It marked the first major effort in remotely obtained and transmitted meteorological data over a prolonged period; it lasted for eight months until the batteries ran out. The Axis war effort also saw the first use of rockets in a remote sensing capacity, specifically for ground photography.

### Remote Meets Hi-Tech

In the decades subsequent to the war, remote sensing has increased both in volume, quality and type. Its name, in fact, came from Evelyn L. Puitt of the US Office of Naval Research; she was one of the major forces behind the development of computers, work which was rewarded by her becoming the first woman admiral in any national navy. The development of satellites permitted large scale studies over prolonged periods, and just as importantly, there was the decrease in electrical requirements of components used to drive and control remote sensing devices (such as transistors, IC's, improved batteries and solar cells). While the vast majority of such efforts have been predicated on military requirements (see *Spy Satellites*, Electronics Today, April '83), civilian requirements such as logic processing and pure research have all played a role in this field's expansion.

### Canada's Frontier

Canada is in an odd sort of position. We have the second largest national geographical mass (the Soviets beat us by a little bit, as in hockey), with by far the longest coastline of any nation. Vast areas are either underpopulated or not populated at all. Yet information derived from these frontier areas has enormous personal and economic use for those of us who live in more populated areas. Storm fronts in the Arctic will determine whether farmers should or should not seed their fields this week or next, ocean currents determine where our fishing fleets should steam, and snow fall in the mountains determines whether contingency plans should be formulated in cities and towns hundreds of miles down stream preparatory to the spring thaw.

Add to this the fact that Canada has enacted legislation to implement a 200-mile resource protection zone off our coasts; it has been named the "resource ribbon" by Dr. F. Bunn of York University, and encompasses an area half as large

as Canada itself. We thus find ourselves in the unenviable position of requiring phenomenally vast amounts of remotely-sensored processed data, but lacking the financial or infrastructural capability to provide it. Not that Canadian scientists are unable to provide the processing ability, presupposing they can obtain the raw data in the first place, but rather there just isn't the money, either to put the remote sensors in place on a space platform, buoy, etc., or to pay for the processing of the collected data.

### Solutions

There are, seemingly, ways around this problem, specifically via international co-operative efforts. But this is not always as clear cut as it seems. For example, it is not particularly secret that the United States maintains two enormous anti-submarine monitoring networks, CEASAR and SOSUS. Collectively, they and monitor millions upon millions of square miles of ocean, providing enormous quantities of data. From this information avalanche, the military only requires some ten percent of the volume. Within the ninety percent excess capacity is found vast quantities of information which could, relatively easily, be applied to the tracking of ice bergs, fish school migrations, etc. The US is quite prepared to let anyone have access to this data, providing that one pays 90% of the cost of data acquisition (since they use only 10% of it); this includes capital costs for putting the systems in place initially. Suffice to say, the costs of building and maintaining such a vast network of underwater listening devices is simply horrendous, so much so that no one can afford it.

But the need remains. One interesting element concerns marine navigation in Arctic waters, and in those areas such as off the east coast and the Hibernia oil field that are directly affected by icebergs. It has been calculated by Dr. Bunn, that by 1990 the value of being able to predict ice conditions will be worth several hundreds of millions of dollars a year to industry; knowing ice conditions could aid in the removal of iron ore concentrates from Arctic mines, the transportation of oil and liquified natural gas from frontier regions and the protection of oil rig platforms from the vagaries of errant icebergs.

Currently, such information is produced by Ice Central, a department in the Atmospheric Environment Service (AES). They are dependent for their information for producing their daily ice reports on data received from aircraft reconnaissance, history, and some meteorological work from satellites such as LANDSAT or GEOS (both of which operate effectively only in daylight and clear weather). Some information is received from passing ships, either merchant marine, which provide low quality data, or 'ships of con-

venience' such as military vessels, which provide data that is high quality but intermittent. Of the total Canadian coastline, only some 5% can be covered using these techniques within the restraints of the \$10 million per year budget.

### Hot Ice

There is, however, another way that this data can be obtained, processed and passed on to interested parties either in real time or a close approximation of it. It is dependent on the realities of physics, realities which result in 'hot ice'.

Until one reaches absolute zero, when all molecular motion ceases, there is no such thing as a 'cold' object. Everything radiates energy in one form or another. A hot stove element, for instance, glows red due to its radiating energy in the visible red wavelength region. As one passes further down the temperature scale, the wavelength of the radiation increases until it passes out of visible light's frequency range. By the time one reaches 'cold' levels, such as ice, the radiation is in the microwave region. The important point is that as long as radiation is emitted, it can be detected. Hence the concept of 'hot ice'.

In Canada, the idea of utilizing the microwave emissions of ice to determine its concentration, position and age, was first proposed by Drs. Rene Ramseier and Steven Peteherych, currently at Ice Central AES in Ottawa, and the Atmospheric Environment Service in Downsview, respectively. The trick was to get the raw data without bankrupting Environment Canada.

### To The Rescue

Fortunately, the US Navy has a branch known as 'Fleet Numerical Oceanographic Service' in Monterey, Calif. It is here that data from US Navy Fleet satellites is decoded and processed. A deal was struck whereby the Navy, after processing the data for their own purposes, would produce as a side product semi-processed data which could be utilized in Canada for the determination of ice formations, including their ages (first year or multi-year), and movements. It was a simple situation; the Navy had the numbers, while Canada had the ice. With the exception of Goddard/NASA, Canada is the only recipient of this information.

The data is received in Canada at a company known as PhD Associates Inc., located at York University. Run by Dr. Frank E. Bunn and Dr. Frank W. Thirkettle, the company currently numbers about 22 persons: faculty, support staff, and students ranging from undergraduates to Ph.D candidates. This company is typical of York's increasingly successful attempt to provide an interdisciplinary approach to scientific problems that involve academia, government and industry.



## Crunching the Numbers

The hot ice determination process is relatively straightforward, once the software to do the number crunching had been developed, a process that took some three years. The US maintains the NIMBUS-7 satellite in a near-polar orbit. On board are sensors tuned to the 18 and 37 GHz frequencies which detect the microwave emissions of the ice, technically known as the temperature brightness. Every second day (due to power constraints) the recorded data is transmitted down at high speed to the tracking station at Gilmore Creek in Alaska. Gilmore then bounces the signals off a COMSAT to Monterey, where Fleet Numeric does the initial processing and the 'ice useable' by-product is roughly fleshed out. Ph.D Associates obtains the data over land lines, storing it on their Super Pet's disks. The major processing then involves sending the data to the university's IBM mainframe, which also produces large mylar pictures denoting the coastline and the relevant numerical data; this data is read as the temperature brightnesses at the two frequencies, the first year ice concentration and the multi-year ice concentrations. The data is then dumped back into the Super Pets, connected to an 8x11 plotter and re-plotted into smaller paper maps, four of which are equivalent to one mylar map.

Any one of a number of representations can be made: isobars between similar concentrations producing lines similar to height gradations, color representations, whatever. These maps are then sent to Ice Central in Ottawa over a data fax (facsimile) system and used to help determine the daily ice forecasts. Similarly, these smaller maps can be sent to individual ships via a radio facsimile system. This means that ship navigators and owners of oil rigs can receive ice information on a bi-daily basis. Its use in saving time and reducing hazards is therefore enormous.

## Through Difficulty...

There are, however, some difficulties. The smallest pixel of information is some 30 square km, covering an area far larger than any iceberg. Some calculations are only arrived at with difficulty due to winds whipping up the water patches within expanses of ice (technically known as 'polynyas') which lowers the water's perceived temperature. Getting the information to the ships (due to their being out of range of a COMSAT) requires radio faxing, which in turn is derived from a data fax transmission, resulting in an overall degradation of signal quality. The passive system used is not as good as an active system which would send down a microwave beam and read the reflections.

## ...To Success

But nonetheless, while still on something of a shoe string (Ph.D has only spent about \$1 million over the past three years), the operation does work and work very well. And matters seemingly will improve. In 1986 the US Defense Meteorological Satellite Platform (DMSP) will be launched, and will contain an SSM/I, a Special Sensor Microwave instrument. This will permit reception not only on the 18 and 37 GHz frequencies that are currently available, but also on the 85 GHz band. The 85 GHz is expected to produce interesting results; the pixel resolution will be 12.5 km, which while still not showing individual icebergs, is better than the 30 km currently available.

And finally, Ice Central itself. On their current budget of \$10 million per year they can only cover some 5% of our coastline. Due to the off-shore work that is increasingly being done, they are being asked to provide data that they simply don't have the money to generate. Using this system would only cost about \$2 million per year and would provide coverage for all of Canada's coastline.

All in all, Ph.D's efforts seemingly give credence to a remark made by Dr. Bunn at a Space Science symposium held at York last fall, that "there's money in hot ice."

ETI

## MEMORY SPECIAL

4116 150NS NEC	\$ 1.99
4116 200NS	\$1.49
4864 1x64K Hitachi 150NS	\$ 7.75
4164 C-3 150NS NEC	\$ 8.50
2716 2Kx8 HITACHI, NEC	\$ 4.99
2732A 4Kx8 TI	\$ 9.00
2732 NEC	\$8.25
<b>2764 8Kx8</b>	
Mitsubishi 250NS	\$12.25
2764 8Kx8	
Mitsubishi 300NS	\$11.75
2532 Hitachi	\$ 7.65
2114 200nS (Hitachi)	\$ 2.25
2128-2, 2116, 4016, 2016	\$ 8.25
6116LP 150NS Hitachi	\$10.50
TMS 4416 120NS 4Kx16	\$ 9.50
Mc3470	\$ 5.99
2003A	\$ 1.59

Call for quantity price  
OEM Enquiries Invited.


## Japanese Parts Specialists PARTS 100% GUARANTEED

### CPU

Z80	\$ 5.99
Z80A NEC	\$ 6.75
6502A 2MHz	6.99
6502	\$ 6.50
6845 CRT Controller (Hitachi)	\$10.99
6522	\$ 6.99
6850	\$ 4.99
8035	\$11.00
8039	\$12.50
8279	\$ 9.00
8155	\$11.50

### 800 Series for IBM

8088D NEC	\$29.50
8237A-5 NEC	\$29.95
8253A-5	\$16.00
8259A-2	\$10.99
8255A-5	\$15.95
8284A	\$13.50
8288D	\$19.00
UPD 765A	\$45.00
82C43C	\$11.00
82C53-5	\$10.75
8243C	\$12.00

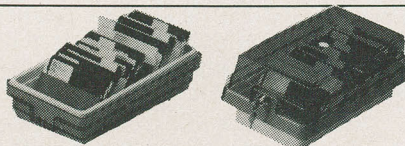

5-1/4 Floppy Disk Case (storage up to 150 diskettes) Lock included	\$ 29.95
5A Hydro approved Switching Power Supply (for Apple)	\$85.00
15A, 130W Switching Power Supply for IBM PCB's	\$169.00
52 function numeric keyboard (electronic touch) upper/lower case)	\$ 99.00

## Diskettes

Maxell MDI	\$ 33.50
Verbatim	\$ 33.50
SKC S/D	\$ 27.00

## Disk Drive

IBM Compatible	
5-1/4 Slimline double sided double density disk drive.	
MODEL: Matsushita	
JA551-2 (same as Shugart SA455)	\$249.00
Mounting Hardware	\$ 6.99
Full Height Front Panel (to above drive)	\$ 12.50
5-1/4 dd for Apple TM	\$299.00
Model JA550-2 Panasonic	

1. 40-80 Column Switch	\$ 5.00
2. Colour R.F. Modulator	\$15.00
3. Joystick (Self-centering) two adjustable controls	\$39.00

a) 128K RAM Card	\$225.00
b) 16K RAM Card	\$ 59.00
c) 80 Column Card	\$ 79.00
d) Disk Controller Card	\$ 59.00
e) Z80 Card	\$ 60.00
f) Communication Card	\$ 79.00
g) 40/80 Col. soft switch	\$ 19.95

Service Centre and Retail Outlet, 4051 Sheppard Avenue East (at Kennedy), Agincourt, Ontario M1S 1S8 (416) 298-3280

# Kitstronic

INTERNATIONAL LTD.

(416) 298-3280  
Telex - 065-26150

Mail Orders: Send a certified cheque or money order plus \$3.00 for shipping and handling. For Special Delivery, please add \$1.00 extra. Ontario residents add 7% P.S.T. Visa & Mastercard accepted.




# DXing: The Dying Hobby

**C.M. Stanbury II explains what you can find on the standard AM broadcast band if you're patient.**

FOR OVER 60 years, almost every radio listener has on occasion stumbled across distant signals on the standard AM broadcast band. In 1983, how many Expo fans kept track of the rival Phillies on WCAU 1210, the Pirates on KDKA 1020, and the Cardinals on KMOX 1120? Some radiomen, like myself, have even spent years collecting cards and letters ('QSLs') from stations verifying distant ('DX') reception of their signals. However, in a few years all of this may be over: the FCC and CRTC plan to squeeze in so many new stations that DX reception will require the most sophisticated of communications gear. Even following the baseball pennant races via an ordinary AM receiver might then be a thing of the past.

For those with an eye, or should we say ear, for memorabilia, now is the time to hunt down these far-off Medium Wave

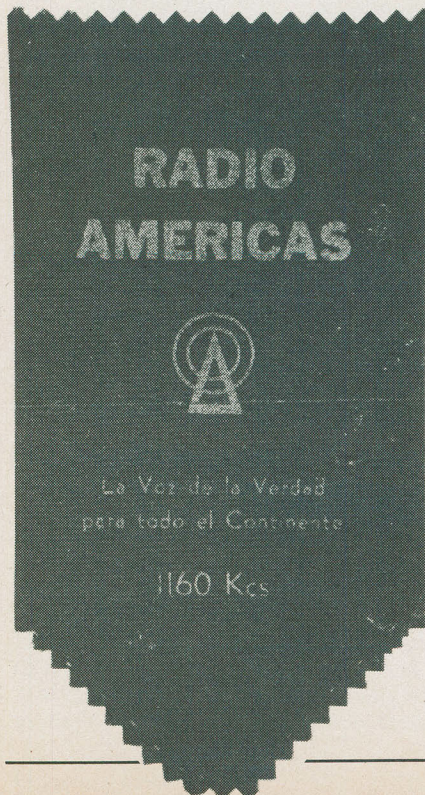A souvenir pennant from Radio Americas, also known as Radio Swan, received by the author to confirm reception.



broadcasters. Here is a brief summary of what's still available.

## Split Frequencies

There continue to be a few BCB transmitters in Latin America operating on frequencies between the regular 10-kHz-spaced channels assigned in Canada and the US. The most often heard of these are Radio Paradise at 825 kHz on new independent St. Kitts, Radio Belize at 834 kHz, 'Amiga' at 1125 kHz from San Jose, Costa Rica, Caribbean Lighthouse at 1165 kHz from Antigua, and Radio Cayman at 1555 kHz.

## Clear Channels

There are still a few spots on the dial where no Canadians transmit at night and only one or two American 50 kilowatts (though not for much longer). Under certain conditions, primarily but not exclusively ionospheric disturbances, Latin American signals will top the US signals. Although they're mostly in Spanish, a little practice will allow the listener to pick out the station name and location, e.g., Radio Tiempo, 1200 kHz, Caracas, Venezuela. Other frequencies upon which similar reception can be expected include 650, 660, 670, 700, 720, 750, 760, 770, 780, 820, 830, 840, 870, 880, 890, 1020, 1030, 1040, 1100, 1120 and 1210 kHz.

## Cuba

Although the Cuba-US radio war set off by the Reagan Administration's Radio Marti will be a major source of increased interference, Cuban signals continue to be the most widely heard of all the distant signals; for instance, the high-powered Radio Progreso outlets on 640 and 1160 kHz. Prior to Radio Marti's appearance on 1180, a low-powered Progreso transmitter was on that frequency, as well as another relaying Radio Reloj Nacional. Both of these, to give readers an idea how well Cubans reach into Canada, had been heard in Southern Ontario despite the presence of the 50 kW WHAM in Rochester. With the debut of Radio Marti on 1180 kHz, it is anybody's guess what Castro may throw on the frequency. Other channels to watch in the Cuban-US spectrum war include 590, 600 and 1040 kHz.

## Coast to Coast

After Radio Progreso on 640 kHz signs off about midnight (assuming that they

still do sign off by the time you read this), listeners in Eastern Canada should watch for KFI in Los Angeles. Listeners in the West will find east coast logging now almost impossible, although WHN at 1050 kHz, New York City, might make it. WWL at 870 kHz from New Orleans on the Gulf of Mexico is not too difficult.

## Beyond the Edge

As noted in Spectrum Wars (ETI, Sept., 1983), plans are afoot to expand the broadcast band up to 1700 kHz, and already stations are broadcasting on 1610 kHz. By far the most widely heard of these is the English language religious Caribbean Beacon on tiny Anguilla in the eastern Antilles. Caribbean Beacon's US owners have persistently indicated an interest in becoming involved with the Radio Marti; thus 1610 kHz is a frequency which should be watched. **ETI**

## Teachers! Students! Engineers! Technicians!

We offer a Z80 based  
MICRO COMPUTER KIT  
starting at \$159.95

Also, we offer a  
**MULTILAB CARD**

**This card features 6 interfaces, including Analog to Digital and Digital to Analog Converter, HEX Keyboard, Mini Led screen display, 7 segment Digit display, etc.**

**\$239.00 Kit \$289.00 Assembled**

**FREE!**

Call or write for your free catalogue featuring the products we manufacture.

Add 3% shipping and handling. Quebec residents: add 9% P.S.T. Cheque, money order, visa accepted. Please print your name, visa no, expiration date & signature.

**PROTEC MICROSYSTEMS INC**


725 Decarie Suite 202, St. Laurent, Que. H4L 3L4

**(514) 744-3363**

Circle No. 13 on Reader Service Card



# Direct Broadcast Satellites

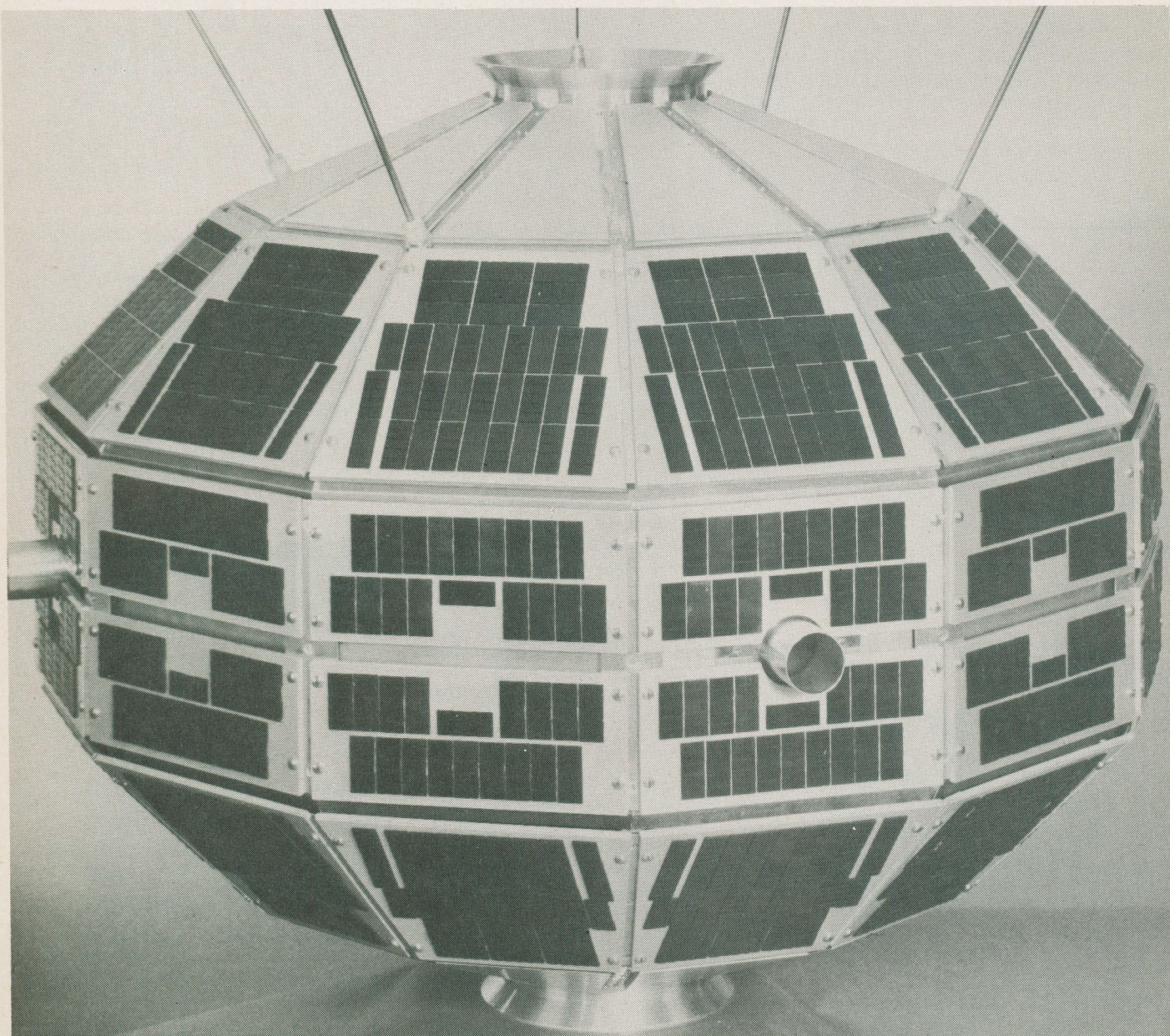

**Roger Allan looks into the politics of DBS and its possible impact on the broadcast industry.**

IN CANADA, government and broadcast interests have a distinct sense of déjà-vu on the subject of direct-to-home or direct broadcast satellite (DBS) transmissions. This is due to the parallels that exist bet-

ween current perceptions of television and radio transmissions and those that existed in the pre-TV days, to wit: the perceived need to offset the rapid encroachment of U.S. television services into Canada and to provide new opportunities to the domestic electronic equipment industry.

This perception has been heightened in recent years by the governmental policy steps taken to help negate the penetration of U.S. broadcasting signals (and

therefore cultural mores) into the country. The matter has most recently come to a head due to over a dozen U.S. companies requesting authorization to proceed with 6/12 GHz DBS services, many of which will have spill-over in that geographic ribbon along our southern border which contains almost two-thirds of our population. While many of these applicants intend to use scrambling devices so that they can charge subscribers for their services, a



# Software Now!

FIRST  
ISSUE  
OCTOBER 1984

Canada's Microcomputing Software Magazine

\$2.95

- Up to the Minute Reviews
- News of Games, Business, Home, Professional and Education Packages
- Exciting New Applications
- Soft for IBM, Apple, CP/M, Commodore, Radio Shack, Macintosh and more
- Canadian Sources



Announcing a very special offer for  
charter subscribers to  
Canada's Microcomputer  
Software Magazine!



### From The Editor,

Not knowing about software is a multiple edged sword. Not only don't you know what you need; you don't even know what you're missing. It's terribly easy to leap upon the first package that comes within waving distance of your application and then bend your application to suit it.


This is not the way it should be.

There is software for every use, perfect software for any conceivable purpose . . . but finding what you want can be a drag, if for no other reason than the constant repetition of the tune from Mission: Impossible playing inside your head.

The fabulous thing about editing a magazine like this is that you get to play with every package in the cosmos. However, this is extremely tiring . . . the fabulous thing about reading a magazine like this is that you get the benefit of being able to play with every package in the cosmos without actually having to do all that typing.

**Software Now!** will keep you abreast of what exists, tell you what probably shouldn't exist and inform you about where to get it so you can make it all exist for your needs.

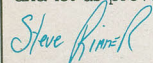We know that **Software Now!** is going to become one of the most essential accessories any computer user can own. Subscribe . . . Now! . . . and let us prove it to you.



**Steve Rimmer**  
Editor,  
**Software Now!**

# Software Now

## First Issue October

### A New Canadian Publication for the Ultimate Medium

The difference between we humans and the other inhabitants of the planet is our capacity for making tools. Civilization is often measured by its grasp of technology . . . it's through his use of tools that man has come to be able to manipulate his environment.

The computer is the ultimate tool . . . it is, like man himself, unspecific, and thus adaptable to virtually any task. The same computer can be a bookkeeper, a game, an artist's palette, a composer's amanuensis, a word processor or a programmer's development station.

The computer itself is simply a box full of chips. The power of computers lies in the software that runs on them.

**Software Now!** is the new magazine for people harnessing the power of the microcomputer. In its pages you will find the information which you will need to choose and apply the software that will dedicate your computer to your tasks. It will help you make sense of the myriad of similar software packages, translate the intricate complexities of software claims, understand the watershed breakthroughs in software development . . . and even have a bit of time left over to dematerialize a few aliens.

Perhaps most exciting, however, is that the pages of **Software Now!** will contain news about software for applications you've never even considered running on your computer. Imagine having an overview of the work of the world's most gifted program developers . . . and you'll have a good idea as to what this new publication is about.

**Software Now!** will be dealing with a broad range of systems and applications, encompassing eight, sixteen and thirty-two bit machines and software as diverse as video games, drafting systems and spreadsheets.

We've reached a level of development in microcomputer software wherein one needn't be a computer genius to apply a computer. In fact, one can operate a computer with only a bit more expertise than one needs to successfully make toast. The key that will unlock the power of your computer is the software you plug into it.

**The key to that software is understanding.**

**The key to understanding software is Software Now!**

### The Pedigree

**Software Now!** is published by Moorshead Publications, which also brings you Computing Now!, Electronics Today, Computers in Education and the Printout newsletter. It has been producing successful magazines in Canada since 1977.

Moorshead Publications is unique in the way it produces magazines. The expertise in applying microcomputers has allowed us to make virtually the entire process of publishing electronic. The editorial in the publications is created on word processing terminals and computer type set. All the financial planning is handled by computer, as is filing and list management. The company also

maintains an on line telecommunications computer to communicate with its readers.

The Editor of **Software Now!** is Steve Rimmer, who also edits Computing Now! In the first year of its existence Computing Now! went from a standing start to having over twenty two thousand subscribers, making it Canada's largest consumer microcomputer publication.

Steve has had experience with a wide range of software, from word processors to sophisticated music and graphics packages. He uses a number of computers, including several CPM based machines, an IBM, an Apple II+, a Commodore and a MacIntosh.



are  
W!  
ber 1984

## Features In The Queue

This is some of the editorial we have lined up for the first few issues of Software Now! You can expect it to change a bit... new software springs up almost daily, and Software Now! will always feature the most important developments in this dynamic field. Articles being developed during the preparation for the magazine include:

Computer Aided Drafting On a Micro • Techniques in MacPaint • How to choose a Spreadsheet • Apple Software Crate • Getting to the Root of UNIX • The Digital Research Pantry • A Thousand and One Word Processors • IBM's Productivity Family • Can Mac Write? • Professional Software Roundup • Power Programs for the 64 • Approaching the C • Word Processing Support Programs • dBase II Enhancements • Will it Run Multiuser? • Concurrent CP/M •

**Reviews:** 10 Base • Mighty Mail • WORD-BASE • Easy Script • Computer Chef • Electronic Circuit Analysis Program • Superex Retailer • MAI Basic Four • The Print Shop • TK!Solver • Microsoft BASIC for the Macintosh • Sundog • Turbo PASCAL for the IBM • AutoCAD • MultiMate • Lexicheck and Word Juggler • Dataflex • Symphony • OmniTerm 2 • DB Master • Paint Magic.

In addition to this look for these regular features:

**The Library** (Our monthly survey of books)  
**By The Boards** (Public domain software)  
**Arcade** (A blast at the latest games)  
**Short File** (A short overview of new releases)

# The Amazing Software Now! Software Disk Free to Charter Subscribers

At Moorshead Publications, we have always managed to launch new magazines with a flying start; this time we want our previous records to be smashed. We believe we have come up with "an offer you can't refuse".

The **Amazing Software Now! Program Disk** is, we believe, the best offer ever made to Charter Subscribers to a new magazine. A charter subscriber is one who helps provide the initial circulation base and we feel they deserve something special — what we are offering is just that.

The disk contains some fairly amazing custom written material:

**CalcNow:** A real spreadsheet program with many as the new features of programmes costing a small fortune. CalcNow is perfect for those who want to experiment with a spreadsheet and are dying to see how they work. It is far from a toy.

**DataBox:** A flexible data base manager and is a version of a program we developed for our own company use.

**Poker:** Life is not complete without a video game.

**Phone Jack:** A telecommunications terminal.

The contents of the disks vary depending on the system and additional programs come for some systems: see overleaf for a more complete description.

The **Software Now! Disk** is available in a huge number of different formats but we haven't forgotten you if you haven't got a disk drive or a system that we can accommodate: everyone will also receive a hard copy listing of those programs written in BASIC (listed for Microsoft Basic for you to modify yourself).

This disk will be sent to you **FREE** if we get your subscription order **before September 30th, 1984**. Early orders will get their disks as soon as processing and shipping time allow, later orders will receive them with the first copy of the magazine.

The **Software Now! Disk** is not available at this time **EXCEPT** to **Software Now! Charter Subscribers**. The software is currently in the final stages of development but we must reserve the right to modify the content.

Software Now! is available at a charter rate of **\$19.95** for a one year subscription, **\$34.95** for two years. This rate is valid until September 30th, 1984. This rate includes your choice of a free software disk... please specify the machine operating system and format you want the disk to run with: check those available.


**Software Now! Subscriptions**  
25 Overlea Boulevard Suite 601  
Toronto, Ontario  
M4H 1B1

## YOUR GUARANTEE

If you do decide that Software Now! is not the magazine you expected or want, or if you decide to cancel your subscription for any reason or no reason, you may do so and receive a refund on the unexpired portion at any time.

If, however, you cancel before receiving your THIRD issue, we will issue a complete refund. Charter Subscribers receiving the Software Disk as part of their subscription will have just \$3.00 deducted for the raw cost of the disk.

This guarantee is backed by the full resources of Moorshead Publications. Any refund will be made promptly and cheerfully.

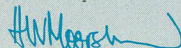  
H.W. Moorshead  
President

**Be a Charter Subscriber:  
Save up to 50% and get your Free  
Software Now! Disk**

## Advertising

For details on advertising in Software Now!,  
Call our Advertising  
Department: (416) 423-3262.



# The Amazing Software Now! Bonus Disk

The programs available on the disks are as follows:

Product	(yr)	Resin	(1979)	PLA/Phn	PLA/Pl	U-Tr	az	U-HLS
31:PS TOTUS/GAMES	1.40							
31:PS INJ HOLD MISC	9.00							
32: (Prof) 27.5 Inj Hold Misc		27.50				137	1.26	63
33:PS/STAN EGG CARTONS	7.50					137	1.50	75
34:								44
35:PS/STAN ROOFING	6.70							
36:PS/STAN SHEATHING	5.50							
37:PS/STAN EXTR MISC	5.00							
38: (Prof) 18.8 Extr Foam		18.00						
39:EPS INSULATION	16.00							
40:EPS HOT-DRAWN CUPS	5.70							
41:EPS PACK SHAPES	3.30							
42: (Prof) 25.0 EPS Foam		25.00						
43:PS/STAN FLOOR WAXES	2.00							
44:								
45: Total PS	126.30							
46: Resin exports	13.20							
47: Actual net totals	126.20							
48:								
49:								
50:								
51:								
52:								
53:								
54:								
55:								
56:								
57:								
58:								
59:								
60:								
61:								
62:								
63:								
64:								
65:								
66:								
67:								
68:								
69:								
70:								
71:								
72:								
73:								
74:								
75:								
76:								
77:								
78:								
79:								
80:								
81:								
82:								
83:								
84:								
85:								
86:								
87:								
88:								
89:								
90:								
91:								
92:								
93:								
94:								
95:								
96:								
97:								
98:								
99:								
100:								

Item Entry Page
Record number [ 2 ]
Name of Item: (VIC 20 PROGRAMMER'S REFERENCE GUIDE )
Supplier's Code: (WH110 )
Internal Code: (C081 )
Retail Price: (23.50 )
Our Cost: (20.00 )
Profit Per Item: (3.50 )
Maximum Inventory: (25 )
Current Inventory: (19 )
Minimum Inventory: (15 )
Enter, New page or Abort: [E]

Poker!
I'll see you and raise \$100.

## CalcNow

CalcNow is a fully capable spreadsheet package. It can manage a sheet sixteen columns across by twenty six rows deep. It allows for automatic and manual recalculation, full cursor movement, formulae, constants and labels, disk storage of your sheets and a full hard copy reporting function. Its syntax and behavior is very much like that of the popular packages and for models of the size usually used in small business and personal financial planning it's equivalent to professional... and very much more expensive... spreadsheet packages.

## Phone Jack

Most computers have telecommunications hardware built into them... it's a shame that they don't all have software available to drive it. This program does basic telecommunications and, while its features do vary a bit from system to system... based on what the operating systems allowed us to implement... it does provide for the basic requirements of calling computer bulletin boards and dial up mainframes.

## Utility Pack

Most revisions of the disk will also have a choice selection of utility programs. These vary a lot from system to system so it's a bit difficult to describe them all here. However, these are the little routines that make life so much easier when you sit down at the keyboard and switch on.

## DataBox

Many commercial data base managers are extremely powerful, extremely expensive and, in fact, grossly over qualified for most tasks. DataBox can handle most of their routine tasks that data base managers are bought for. It is efficient of disk space, reasonably fast and very, very flexible. It can keep track of your files, your stock... or even your record collection. It features variable fields, hard copy reporting and flexible search parameters.

These programs will vary a bit from system to system... the following outlines the formats in which we can supply this software. You will need your own Microsoft compatible suitable BASIC Interpreter (e.g. GWBASIC, BASIC-80, MBASIC, APPLESOFT, RS BASIC, PET BASIC, Microsoft Macintosh BASIC etc.)

**For CP/M\* users:** CalcNow, DataBox, Poker!, Utility Pack, Phone Jack

**For Apple II+DOS Users:** CalcNow, DataBox, Poker!, Phone Jack, Utility Pack plus Clef Hanger (An Apple Music Box), Skyhook (a teletype converter) and Fruit Crate (a BBS).

**For IBM Users:** CalcNow, DataBox, Poker!, Utility Pack, Phone Jack plus Bandit (A slot machine simulator)

**For Macintosh Users:** CalcNow, DataBox, Poker, Phone Jack and Letterhead (a stationary generator).

**For Commodore Users:** CalcNow, DataBox, Poker, Utility Pack and Phone Jack.

**For TRS-80 Model III and 4:** CalcNow, DataBox, Poker

## Poker!

We wanted to include a game on the disk and, after some deliberation decided that a good dimly lit, smokey card game would fill the bill best. This one simulates five card draw poker in the proper cowboy style. It can deal, draw, call, bet... do everything but cheat and pull its six gun on a really bad hand. POKER! features a graphic display of the cards being played.

This software is available as a free gift to charter subscribers to Software Now! magazine. To be eligible to receive this disk your subscription order must be at our offices no later than September 30th, 1984.

\*Available for Apple CP/M, Osborne single and double densities, Access Matrix, Kaypro II, Lobo max 80, Morrow Micro Decision, Olympia single and double, Superbrain, Systel/Olympia, DEC VT-180, Nelma Persona, Xerox/Cromemco, 3R Avatar, Casio FP-1000, Epson QX-10VD, Attache, Micromate, if800, Sanyo MBC 1000, Televideo, Zorba and on eight inch single sided single density disk.

I'd like to become a Charter Subscriber to Software Now! and receive my Amazing Software Now! program disk.

☐ One year (12 issues) for \$19.95

☐ Two years (24 issues) for \$34.95

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

Province \_\_\_\_\_

Post Code \_\_\_\_\_

☐ Cheque enclosed

☐ Bill my Credit Card (Visa, Mastercard, American Express)

No. \_\_\_\_\_

Expiry Date \_\_\_\_\_

☐ Bill me (we are happy to bill you but you will NOT qualify for a Software Now! program disk).

Please specify the format you want for your disk

Offer expires September 30th, 1984.

--	--	--

Mail to: Software Now! Subscriptions,

Moorshead Publications, 25 Overlea Blvd., Suite 601, Toronto, Ontario M4H 1B1.

## Please Specify Your Disk Code as follows:

APP	Apple II+ DOS
IBM	IBM PC
MAC	Macintosh
TRS	Radio Shack Models 3 & 4
CBM	Commodore Disk formats
ACP	Apple CP/M
OS1	Osborne Single Sided
OS2	Osborne Double Sided
AMT	Access Matrix
KAY	Kaypro
LOB	Lobo max 80
MOR	Morrow Micro Decision
OLI	Olympia Single sided
OL2	Olympia Double sided
SBR	Superbrain
SYS	Systel/Olympia
DEC	DEC VT-180
NEL	Nelma Persona
XER	Xerox/Cromemco
3RA	3R Avatar
CAS	Casio FP-1000
EPS	Epson QX-10VD
ATT	Attache
MIC	Micromate
SAN	Sanyo MBC 1000
TEL	Televideo
ZOR	Zorba
IF8	if800
8"	8" Disk Single Sided, Single Density



number of them do not; they intend to let the signals land where they may and be picked up by anyone, income being derived from the sale of advertisements on the various channels.

As such, both Canadian broadcasters and the federal government have been quietly agitating to get something in the works other than the policy statements and recommendations that have been propounded (and until recently, largely gathering dust) by the Department of Communications and the Canadian Association of Broadcasters. Of the two, the broadcasters are particularly concerned; while about 45% of Canadian homes have direct off-air access to current U.S. signals (rising to 57% for those that have cable), U.S. DBS signals could penetrate as much as 85% of the available Canadian market. Recognizing that they are having enough difficulty with U.S. TV competition as it is, the thought of even more is not greeted with glee in the broadcasters' boardrooms.

### Technical Equivalence

One of the prime considerations espoused by the broadcasting community is that the government not implement a system that is incompatible with that used by the Americans. They learned in the 1930s, when the government ordered all private AM radio broadcasting stations to

operate at much lower power levels than was permitted in the U.S., that this can only result in a major erosion in the market, an erosion which is difficult to overcome when the government finally wakes up (in this instance, in the early 1940's) and permits technical equivalence between the two national structures. Specifically, as far as the Canadian Association of Broadcasters (CAB) is concerned, the question lies in the power strength of the transmission down-links from the satellites; make it any less than the U.S. DBS system and larger receiving dishes are required, along with a concomitant increase in cost to the consumer, and less likelihood of viewer acceptance.

This is borne out in the conclusions of a government-commissioned study by the Woods Gordon Company, which indicated that a reception system costing \$600 in 1981 dollars (representing the cost of a 1.2 metre receiving dish) would only include about one-third of the market of a \$400 dish (0.8 metres) and that the market would virtually cease to exist if the dish alone cost \$1,200 (1.8 metres).

The initial question that must be asked, of course, is why one should bother. After all, as government studies indicate, the cost of implementing such a system is rather high (so high in fact, that CAB insists that it cannot be done without government financial intervention) and

would require large portions of the consumer market to purchase new equipment.

### Why?

The usual answer is twofold: the Americans are going to do it, so we had better do it as well; and secondly, we want to reach the 'underserved' consumers. While I wouldn't suggest that anyone in Canada should receive less mass media input than anyone else, the government's description of 'underserved' would make most of the world's population sit down and giggle. According to one government report, more than 16% of the Canadian population still has 'relatively limited' access to broadcast services, either television or radio, and this despite the use of relay satellites. While urban dwellers have on average access to twelve television channels (either picked up from antennas or piped through cable systems) there are some four million Canadians in rural or northern areas that receive an average of only three television channels. It is to serve this market that the DBS system would be created.

A further consideration is that High Definition television is on the horizon as a new technology. It requires improved television tubes and less transmission interference than current models. Should HDTV become a market reality (at the

## EVERYTHING FOR IBM-PC

AMDEK - AST - COMREX - CONTROL DATA - EPSON - EVEREX  
HITACHI - IBM - KEYTRONIC - MAYNARD - NEC - NETRONIC  
PANASONIC - PGS - QUADRAM - ROLAND DG - SHUGART - TECHMAR

- IBM-PC, 128K, 2-360K full size drive, kboard \$3,395
- IBM-PC, 128K, 1-360K drive, 1-10Mb hrd disk 4,595
- 10Mb Hard disk subsystem (with controller) 1,350
- CONTROL DATA CDC9409 full size Drive-360K 349
- SHUGART SA-455 slim Drive-360K 239
- IBM - certified full size 360K floppy Drive 599
- AST SixPak Plus (OK, serial, parallel, clock) 429
- AST I/O Plus (serial, parallel, clock) 279
- AST Monograph Plus (serial, parallel, clock) 839
- MAYNARD floppy controller 259
- opt: parallel or serial port 69
- NETRONICS floppy controller with parallel 299
- opt: real-time clock 69
- SASI hard disk interface 69
- IBM color / graphic card 365
- IBM monochrome / printer card 399
- TECHMAR Graphic Master card 799
- KEYTRONIC 5150 keyboard 299
- KEYTRONIC 5151 De Luxe Keyboard 399
- AMDEK V310A amber, TTL input monitor 269
- PRINCETON HX-12 RGB color monitor 849
- QUADRAM Quadchrome RGB color monitor 869
- EPSON FX-80 matrix printer 749
- EPSON FX-100 matrix printer 1,199
- EPSON LQ-1500 letter quality printer 1,999
- 64K memory add-on (set of 9-4164) 69

Prices apply to mail order ONLY. Certified check, money order, VISA  
Quebec residents add 9% P.S.T. Add 3% for shipping & handling

Special prices available for corporations

We warranty 3 days shipping or we pay the shipping charges



**SWEET  
ELECTRONICS inc.**

6767 Cote Des Neiges, suite 405, Montreal, Quebec H3S 2T6  
(514) 340-1895 Circle No. 24 on Reader Service Card

## WHY SPEND A FORTUNE ON A DIGITAL CAPACITANCE METER?

The MC100A comes completely assembled and calibrated and at \$89.95 is an outstanding value. The extensive range of 1 pF to 9,999 uF (no external meters required) and true hand held portable size (only 4 1/2" x 2 1/2" x 1 1/2") make the MC100A an extremely practical and easy to use instrument for the hobbyist technician or engineer.


### CHECK THESE OTHER FEATURES

- \* Basic accuracy 1% (± one count) on pF, nF ranges, 3% (± one count) on uF range.
- \* Uses single 9V battery (not included).
- \* Decimal points light up when battery is low or when capacitor is overrange.
- \* Full 4 digit high efficiency LED display uses special circuitry to save on batteries.
- \* Constructed with a tough impact resistant plastic case.

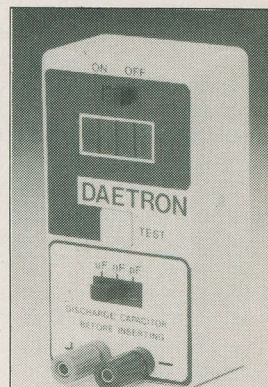**ONE YEAR PARTS & LABOUR WARRANTY**



**DAETRON**  
935 THE QUEENSWAY  
BOX 641  
TORONTO ONTARIO M8Z 5Y9  
(416) 255-9701  
DEALER ENQUIRIES INVITED



1 pF to 9,999 uF

**\$89.95**

### PLEASE SEND ME

(Quantity) MC100A(s) @ \$89.95 \$  
Ontario residents add 7% PST \$  
Postage — \$1.85 (per instrument) (C.O.D. orders add \$1.59) \$

☐ I ENCLOSE CHEQUE ☐ MONEY ORDER ☐ BILL MY VISA TOTAL \$

☐ VISA CARD NO. \_\_\_\_\_

EXPIRY DATE \_\_\_\_\_ SIGNATURE \_\_\_\_\_

Immediate shipping on orders with money orders, VISA or certified cheque.

Personal cheques please allow 2 to 3 weeks for clearance.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ PROV. \_\_\_\_\_ POSTAL CODE \_\_\_\_\_

MAIL TO DAETRON 935 THE QUEENSWAY BOX 641 TORONTO ONTARIO M8Z 5Y9

Circle No. 14 on Reader Service Card



## Direct Broadcasting Satellites

moment it is similar to the way laser-read audio disks were ten years ago), then a DBS system would be the most cost-effective way of reaching the market. Further, there is some thought that an entirely new signal processing and transmission system might be used, such as the Multiplexed Angular Component (MAC) system developed and currently being field tested by the Independent Broadcasting Authority in Great Britain. Such an introduction would follow the historical developments in domestic television receivers. Initially they were equipped with front end tuners for the VHF channels (2-13), later designs included UHF tuners, and current models are cable compatible. The next logical step is a television set containing the additional circuitry necessary for satellite reception, and it may as well be based on a new broadcasting system such as MAC as any other.

### Europe

Canada and the U.S. are not alone in actively considering DBS systems. France and the Federal Republic of Germany are planning to introduce DBS around 1985/6. Their considerations are similar to those of Canada and the U.S., with the added point that they each want to improve their respective audio-visual presence in the European market. In other words, rather than complaining about other nations affecting their culture, they are actively counterattacking by exporting their life styles via the media. This has not been mentioned either in Canadian government or CAB submissions as a reason for Canada developing a DBS system, though it is just as valid.

Surprisingly, one of the earliest and most ambitious undertakings in the realm of DBS was undertaken by the Scandinavian countries. Based on a satellite designated NORSAT, the system was to provide programming for all the countries. The initial discussions were predicated not on commercial considerations, but rather on the recognition that no single Scandinavian country could afford DBS by itself, and that any system would result in signal spillage over several countries, analogous to Canada's concern over cultural sovereignty. It was felt that any disputes over spillage and cultural transpositions should be dealt with first. The discussions are currently progressing slowly, with Sweden threatening to go it alone despite the enormously high cost per viewer reached.

### Elsewhere

Britain announced in 1982 that it will compose a two satellite DBS system to commence operation in 1986. Operated by the British Broadcasting Corporation, it will provide either direct-to-home broadcasting or community reception. The two

channels will consist of an amalgamation of BBC-1 and BBC-2 programming and a subscription-type channel.

According to Dominic Kelly, an officer from the Australian Broadcasting Corporation on secondment to the Canadian Department of Communications, Australia has many of the same time-zone, geographic and demographic difficulties with DBS as Canada does, and next year will be accepting delivery of two satellites known as AUSSAT 1 and 2. Their system will go into effect in October or November 1985, and will require 1.2 to 1.4 meter dishes for reception.

### Techniques

The modelling of a proposed DBS system is dependent upon receiving dish sizes, the power of the satellite's Travelling Wave Tubes (see *The Potent Helix*, ETI, February/84), the satellite position, and the uplinks/downlinks.

While early satellites and a few contemporary ones utilized for specialized purposes fly within a couple of hundred kilometres of the earth's surface (see *Spy Satellites*, ETI, April/83), most communication satellites have a much higher circular orbit, some 36,000 kilometres, permitting them to have an orbital period of 24 hours. This makes them appear stationary with respect to the ground, simplifying tracking and reception. However, since these geostationary orbits lie only along the equatorial plane with a unique radius, the number of satellite slots available is not limitless. The number of slots is not dependent upon the physical volume to be filled, but rather the radio interference between neighbouring satellites. In the realm of DBS broadcasting, where high power satellites are required, there are only a very limited number of available slots, and hence DBS modelers have to start carefully juggling their system's technical parameters. The optimum arrangement would be for a very large number of satellites whose beams, or footprints, would only cover a small area, and being high powered, would require only small dishes for good reception. However, the limited number of slots would mean that high-powered TWTs would interfere with each other.

In Canada's case, covering a vast amount of area and a number of time zones as it does, there are really only two models which might work: the four-footprint and the six-footprint versions. While not optimum, they do take into account such mundane considerations as time zones, the need for regional/national programming, market characteristics and political considerations as well as costs. While a one-beam model covering all of Canada is technically feasible, it would not adequately address the above considerations, while a system with more than

six beams would be prohibitively expensive.

### The Four-Beam Model

In the four-beam model, two satellites (and one back-up) would send eight channels per beam and use circular polarization of the signal, decreasing interference with neighbouring satellites. It would produce an effective isotropic radiated power (EIRP is the signal's ground strength) of either 50 dBW or 54 dBW depending on the strength of the TWTAs on board (47dBW is considered the minimum for any such a system). The higher the EIRP, the more powerful the TWTs have to be and the higher the cost and difficulty of providing both the maneuvering engines and the electrical power from solar cells. Further, the actual physical size of the satellite becomes a consideration. A 57dBW system would need 20 super-high-powered TWTs, necessitating higher launching costs.

This four-beam model would result in the time zone coverage being split into four segments; one covering British Columbia and most of Alberta, one covering Manitoba, Saskatchewan and part of western Ontario, one covering most of Ontario and part of Quebec and one covering the rest of the country. While seemingly adequate in itself, it lessens the broadcasters' ability to introduce regional programming, and would provide scheduling problems for national broadcasts — the ten o'clock news coming in at nine o'clock, for instance. It is, however, relatively cheap, weighing in at some \$652 million 1982 dollars for a 50 dBW version and \$832 million 1982 dollars for the 54 dBW version.

The six-beam model would require three satellites (plus one back-up) and would allow ten channels per beam. As such, it would be more compatible with the country's time zones, as well as permitting increased regional and specialized broadcasting.

At present it appears to be the most likely candidate for acceptance by the powers that be, though its cost rings in at 920 million 1982 dollars for the 50 dBW version and 1,280 million 1982 dollars for the 54 dBW version. Polarization would likewise be circular.

### Modulation

The modulation system for either version is favoured to be FM. While it would seemingly be more appropriate to use the AM system as is currently utilized by terrestrial carriers, the power of the TWTs required to transmit via this method are several orders of magnitude greater than for FM. Since bus space (that is, the volume and weight that can be orbited, either by the Space Shuttle or the European launchers) is limited, and the radiative power of the TWTs would in-



terfere with neighbouring satellites, the situation really calls for a new satellite design. It also has the added benefit of providing far higher quality of audio reception, a factor in viewer acceptance for the system.

## The Links

The determination of uplinks and downlinks is inextricably entwined with the seemingly endless discussion as to frequencies, along with considerations as to EIRP. Currently, the major Canadian communications satellites are the ANIK series, which operate on the 6/4 and 14/12 GHz bands. Since the 6/4 band is also used for microwave transmissions among terrestrial users, the TWTs used must have their power constrained within reasonably tight limits so that interference does not occur. When DBS experiments were conducted in 1979, receiving dishes of 3 metres or larger were required. While the experiments were considered a success, the initial cost of such large parabolic reflectors was considered far in excess of what the consumer market would be prepared to bear.

The 14/12 GHz frequency band has no such problem. It is not used by terrestrial information carriers, and the TWT power can be substantially increased, resulting in dishes of only 0.8 metres in diameter.

The difficulty arises in which frequency to use. A dedicated satellite for DBS operating on 14/12, while under active consideration by the Department of Communications, is well in the future and very expensive. If one waits, then the U.S. will get the jump on Canada, analogous to the reception power considerations in the 1930s mentioned above. If one doesn't wait, it means utilizing the 6/4 band, necessitating the large expensive antennae. Industry proposals are to use the 6/4 band as a stop-gap measure, but to have the reception undertaken by community groups or companies such as the cable systems, who would then feed the signals through their cables to subscribers. This is termed MATV, or Multiple Antenna system for Television.

The difficulty with this proposal is that one of the major features of a DBS system is to provide service to underserved areas. The underserved areas don't have cable, and hence any such DBS system would in the eyes of the government be virtually redundant from the start.

There is some thought that the ANIK C's currently in orbit could be used as a makeshift alternative, since they operate on the 14/12 GHz frequency. However, home viewers would require an antenna dish of 1.2 metres or larger. Nonetheless, both government and industry are of the view that cable companies, community groups and apartment dwellers would be

prepared to share in the purchase of an adequate-sized dish. The single farmer out on the back forty would probably not be able to afford such a large dish, which rather negates the government's reasoning, but in industry's view, better something than nothing.

## The Future?

As for the future, it appears as if Canada is destined to have a DBS system whether the consumer wants it or not. The government is increasingly firm in its stance that such a system should be put in place for

political and cultural reasons, and to provide Canadian manufacturers with another product to sell. Broadcasters likewise are in favour of the system, though they are reticent in bearing the cost, have doubts as to its feasibility for anything other than providing downlinks to cable, and really aren't sure of its overall utility. While you might expect broadcasters to be anti-DBS because of their large investment in cable, and because they've been stung by the poor performance of another innovation (Pay TV), they may indeed have a point.

ETI



## The One Stop Shop For All Your Electronic Needs!

### Conveniently located across Canada

**Montréal**  
5651 Rue Ferrier  
Montréal, Québec  
H4P 1N1  
(514) 731-7441

**Ottawa**  
1023 Merivale Road  
Ottawa, Ontario  
K1Z 6A6  
(613) 728-7900

**Toronto**  
14 Carlton Street  
Toronto, Ontario  
M5B 1K5  
(416) 977-7692

**Calgary**  
3220-5th Ave. N.E.  
Bay 2  
Calgary, Alberta  
T2A 5N1  
(403) 235-5300

**Downsview**  
86 St. Regis Cr. N.  
Downsview, Ontario  
M3J 1Y8  
(416) 630-0400

**Vancouver**  
3070 Kingsway  
Vancouver, B.C.  
V5R 5J7  
(604) 438-3321

\* Mail Orders to Montreal Address.

Visit your nearest Active store, call, write or circle the Reader Service Card for your copy of Active's new catalog.

Circle No. 4 on Reader Service Card





# Electronics In Action

**Two amazing video cameras, a camera that photographs heat, and an intelligent phone.**

**by Roger Allan**

ONE OF THE engineering problems faced in industrial and robotics applications is the difficulty of seeing around corners or obtaining crystal-clear video images from hostile environments. The thumping and crunching of machinery, the whiplash effects of a robot's arm movements, the rapid increase and decrease of pressures and the effects of radiation all make the utilization of video tube cameras less than optimal. They break down regularly, and with particular note in industrial robotics, often times end up as a box full of junk.


In an attempt to deal with this problem, the Fairchild Company has developed a series of what they term 'automation cameras', designed for usage in industrial facilities where video tubes have difficulty operating. Their basic structure is based on the use of charge coupled devices (CCDs) permitting them to overcome the video tube type camera problems while still maintaining optical imagery quality close to that of commercial television.

Their top-of-the-line model is called the CCD4001. It can operate as a single unit or be separated into a camera control unit and a sense head connected by a twelve foot cable. This permits the sense head to be mounted, for instance, at the end of an industrial robot's arm and flung about with wild abandon without effecting the video quality.

Weighing in at a total of 1 kg (with the sense head a mere 227 g) its internal architecture is complicated but compact. The image detector used is a selected, monolithic 256 x 256 element CCD. The buried channel CCD minimizes noise and allows for high frame rates without sacrificing the charge transfer efficiency. It is designed with sufficient 'robustness' to withstand fairly severe hostile environments. The sense head contains the image sensor and the circuitry for generating the high frequency horizontal raster and sample pulse clock signals for the CCD control as well as providing a

buffer for the sensor video. Light reaching the sensor is filtered through a 2.0 mm thick Schott glass lens in order to eliminate infrared content. This results in a near photopic spectral sensitivity.

The camera control unit (housed at the other end of the cable) contains three PC cards performing the functions of camera and sensor timing control, CCD drives and video processing. This unit receives the sensor video from the CCD in the sense head, clamps it, amplifies the signal and blanks it with composite blanketing from the logic boards. This rectifies the image to NTSC standards, thereby permitting its display on standard monitors or digital analysis by computer.

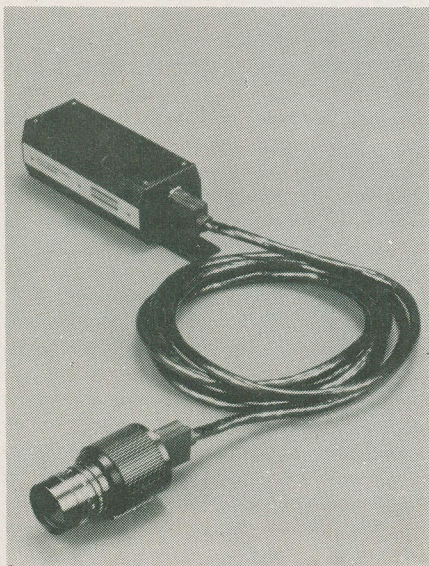

## Command Dialer

One of the more intriguing possibilities presented by the memory storage and number crunching abilities of computers is the ability to recognize human speech, either for data entry or data retrieval. There are a number of devices on the market which utilize voice recognition to a

greater or lesser extent; talking clocks come most quickly to mind. They customarily operate on the recognition of phonemes, the set of the smallest unit of speech that serves to distinguish one utterance from another in a language or dialect. The difficulty with a phoneme-based speech recognition system is that they are really only word recognizers; that is, they can only recognize words in isolation with a pause in between. In order to achieve reasonable recognition ability, words must be spoken distinctly one at a time. As such, before such a system can perform recognition the person has to train the system to recognize the words that are to be used.

In an attempt to overcome this problem, the Audec Corporation has investigated the use of a system that they term 'Rikphones'. It is similar to a phoneme-based system in that it recognizes vocal elements. However, it differs from the phoneme system in that the Rikphones are larger, require a smaller memory storage capacity and hence can be processed faster than phonemes, raising the eventuality of real time data entry capabilities.

In contrast to the other speech recognition processes which utilize frequency spectrum separation of the incoming audio signals via filter banks, this process employs all-digital time-domain waveform analysis, extracting the essential features of the incoming audio signal and comparing them to templates preparatory to processing.

Utilizing this voice recognition process, the Audec Corporation now manufactures several devices for the home and business market, the most interesting of which is the Command Dialer VRT-1200, a voice activated telephone dialing system. This phone has the capability to recognize spoken words and to match them with preprogrammed words and numbers. Its memory can store up to 16 frequently-called phone



numbers, up to 30 digits each (permitting the automatic entry to the MCI or Sprint telephone systems in the United States). For each of the 16 numbers one assigns a code word, such as fire, police, John, whatever. To place a call one merely lifts the receiver (which contains the memory activation switch) speaks the code word and the device automatically dials the call.

Up to four telephone calls can be placed simultaneously in this fashion, with the device automatically calling them in sequence. If the line is busy, the device will continue to dial the numbers in ten minute cycles for an hour. When the connection is completed, this phone advises the user of the connection via an LED display. Upon conclusion of the call, the device will pick up the phoning sequence where it left off until the next call is completed.

There are a number of extra features built into the device: an Instant Notebook which enables one to enter numbers or other short pieces of alphabetical information through the keyboard for latter recall via the LED display during the phone call itself, a security lock to prevent unauthorized entry, and a battery-back up to eliminate re-programming after a power outage or a disconnection. There's also a built in digital alarm clock with snooze control (perfect for the harried business executive during office hours).

The unit is primarily designed for the business market; it can be connected to Audec's MLC-1200 multi-line console, converting it into a five line system, and has a two-way speakerphone for hands-free or conference calling. However, a similar device, the VRT-1100, is available for the home market; it possesses most of the above capabilities, with the exception of having only 16 pre-programmed 30-digit numbers. It was selected for inclusion in the CES Design and Engineering Exhibition in Chicago this June, and in the view of the selection committee represented 'one of the most innovative consumer products introduced in 1984'.

## Heat Auditor

When Sheik Yamani and his OPEC cohorts decided to throw a spanner into the world's economy ten years ago by raising the price of oil, rightly or wrongly, they certainly didn't imagine that their decision's ripple effect would result in a small company in Massachusetts teaming up with the Polaroid company to produce a device capable of helping companies and individuals to reduce their dependence on off-shore energy supplies by reducing heat loss. But such is the case.

The device in question is the Ex-egram 120 Heat Flux Auditor. It is designed to provide a fast, quantitative heat auditing analysis with a permanent record of the readings.



Handheld and weighing in at about 5 lbs, the workings of the system are relatively straightforward. According to the company's president, Frank Pompei, a function thermopile measures the total radiation from a building, room, steam pipe or whatever, converts the signal into digital form, averages it over a specified time period, and then uses the averaged signal to drive an internal LED display. The optical energy produced by the LED then registers on Polaroid 600 Instant Film, giving an instant permanent photographic record of the heat transfer. From such a picture one can determine U and R values of insulations, solar loading, heat losses from equipment and buildings and heat transfer through surfaces, both radiative and convectional.

The number crunching involved in doing the arithmetic is via a number of methods. There are preprogrammed cards for the TI-59 calculator, as well as software listings for use on other mini and micro computers.

Among a number of peripheral devices to help the device calculate the radiation transfer rates are an ultrasonic transducer and rangefinder (Polaroid design), a flash attachment, a digital heat display system for non-photo scanning, and a digital mechanism for recording the

time, date, surface temperature, net heat radiation, air temperature and scale factors on the bottom of the photograph itself.

With a field of view of 30 degrees, a radiation gain/loss range of -400 to 1999.9 BTU/HR/sq. ft., a radiation accuracy of 1%, and a speed of 1.5 photographic records per second, the device will find primary application in industry and among companies catering to the home insulation market.

## JVC Video Camera


One of the major difficulties facing home video film makers arising from the video revolution, if revolution there be, is the inadequacy of most currently available equipment for use on location shoots. You only need to remember the last time you were in the park or at the beach and saw some poor dad desperately trying to film his kids' antics while bestrewn with paraphernalia reminiscent of a Royal Marine traversing East Falkland Island.

In an attempt to overcome the weight and size problem, the JVC company is now marketing a lightweight (less than 2 kg) video camera, recorder and tuner. Known as the GR-C1U, its innards involve the utilization of a smaller cassette (the VHS-C) which despite being one-third the size of a standard cassette (about the size of a pack of playing cards) is capable of recording 20 minutes of footage, and includes a newly designed pickup head. The head drum cylinder of this device, representing the largest single component of any video recorder, has been reduced by about 1/3 of the customary diameter. To maintain a signal recording pattern consistent with standard VHS specifications, a new parallel loading system was developed in which the tape is loaded around 270 degrees of the drum, which rotates 50% faster than is customary. Four video heads are used to produce tracks of the same length as those recorded by standard VHS recorders. This allows the tape to be viewed through a





## Electronics in Action

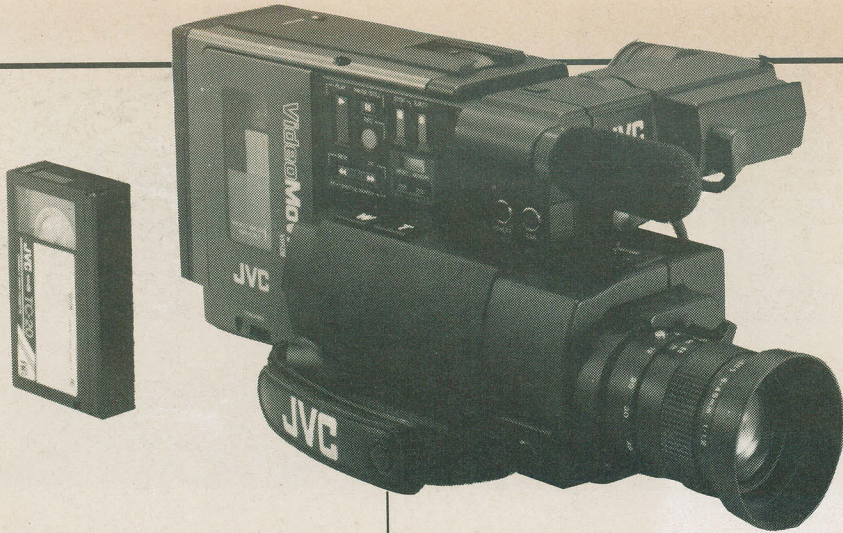

half-inch built-in electronic viewfinder, or alternatively, by fitting the VHS-C into a special cartridge (analogous to the cartridges which permit cassette tapes to be played on 8-track units) the footage can be viewed via standard VHS playback units and a television set. The tape can also be played back through an A/V monitor or (via a built-in RF unit) directly through any television.

The pick up tube utilizes a half-inch Saticon design single-carrier frequency separation design with a reverse filter similar to those used in three-tube broadcast cameras. Its optics are an f/1.2 lens

with 6:1 zoom, while comprehensive color temperature adjustment, employing a combination of filters and electronic circuitry, permits accurate reproduction of the full color spectrum; this can range from the indoors (subdued restaurant lighting) to full direct sunlight. Artificial lighting, either incandescent or fluorescent, is automatically compensated for. Audio recording is via FM. The viewfinder is reminiscent of something from the Space Shuttle, incorporating a surprisingly comprehensive warning system which includes an exposure meter, low battery power, tape-end alarm and

five other indicators. It is through this viewfinder that one can view playbacks of newly-recorded footage for on-the-spot checks of 'program content'.

There are many standard features to this device, such as audio and video dubbing capability, automatic backspace editing, shuttle searching in both directions and still playback. However, it is the external add-ons that really expand this device, such as a plug-on 3-inch color video monitor, and most intriguingly, the CG-P50U character generator which permits the automatic superimposition of titles, dates and lap times on any recorded scene. Further, this character generator incorporates a 14-page memory and can create titles in four character sizes with scrolling and zoom effects. **ETI**

### Addresses

*Fairchild Camera and Instrument Corp., 3440 Hillview Ave., Palo Alto, Calif., 94304, USA*

*Exergen Corporation, 307 West Central Street, Natick, Massachusetts, 01760, USA*

*JVC Canada Limited, 21 Finchdene Square, Scarborough, Ontario, M1X 1A7*

*Audec Corporation, 299 Market Street, Saddle Brook, New Jersey, 07662, USA*

### Complete System +



for  
**\$875.00**

- 6502 Micro processor • 48K memory
- Disk drive • Disk controller card • Upper/lower case • Hi-res Amber monitor
- Colour graphics • 90 days warranty.


### Complete System Model 2200

for  
**\$999.00**



- dual processor 6502 and Z80 • 64K RAM • 80 or 40 column soft switch • controller card • disk drive • Hi-res amber monitor • colour graphics • detachable keyboard • 90 days warranty.

### I.B.M. Compatible

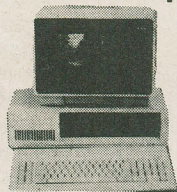

**ECS1**  
**\$1895.00**

- 8088 processor • optional Intel 8087 numeric coprocessor • 64K memory exp. to 256K on board • double sided double density disk drive • detachable keyboard • colour-graphic board • support IBM® software • 90 day warranty

### ECS2 Systems



**\$1195.00**

- dual processor 6502 and Z80 • 64K RAM • controller card • disk drive • Hi-res amber monitor • colour graphics • detachable keyboard with special function • 90 days warranty.

### IBM™ Compatible Main Board

**RX 6600**  
**For**  
**\$479.00**

- 64K Ram
- Z80 (CP/M)
- Special Function Keys
- User's Defined Keys
- Apple II + compatible

### DISK DRIVE

**For \$235.00**

- Apple II Compatible Shugart 390L
- Slim Line Teac \$249.00
- IBM Slim Line Double Side DD \$249.00


### CARDS & PERIPHERALS

- Z80 \$49.00
- 16K Ram \$55.00
- Disk Controller \$45.00
- 80 Column \$69.00
- Light Pen \$199.00
- Joy Stick \$38.00
- 5 Amps Power Supply \$79.00
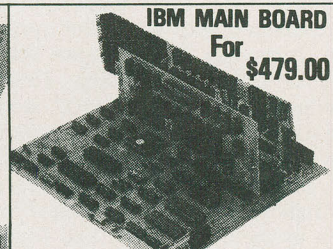
### PRINTERS

- Mannesmantally Sprit 80 \$425.00
- TTX Daisy Wheel \$550.00

**IBM MAIN BOARD**  
**For**  
**\$479.00**



- IBM Compatible bare Board \$39.00
- Multi function card \$225.00
- IBM Compt. Case \$79.00
- IBM Compt. Power Supply 10 amps 100 watts \$119.00
- IBM Compt. Drive DSDD \$249.00

### IBM™ PC COMPATIBLE

**KEYBOARD**  
**\$179.00**



Enhance your IBM PC™ Compatible Computer System with K150 Keyboard.

Use Cherry TS-M0001 switch with life time 20 million operations.

\* IBM is Trade Mark of IBM Canada.

\* Apple is a registered trade mark of Apple Canada Inc.

**Opening  
August 15**

## ELECTRONIC CONTROL SYSTEMS

1590 Matheson Boulevard, Suite 1 & 2 Mississauga, Ontario L4W 1J1 (416) 673-1302  
1890 Meyerside Drive, Mississauga, Ontario L5T 1B4 (416) 673-1302  
Hours — Mon. to Fri. 10-7, Sat. 10-2



# Offbeat Metronome



**A very basic rhythm box for musical practice and improvisation, with a tuning device built in.**

**by Andrew Armstrong**

THIS IS a metronome with a difference. The initial requirement was for a simple metronome which would enable the musician or musicians to practise playing to an even rhythm, instead of succumbing to the inevitable temptation to play faster and faster until collapse from exhaustion ensues. The project became more ambitious when we decided to add a rhythm accent or offbeat to give a variety of rhythm 'feels' to play against. What was wanted, obviously, was a very simple substitute for a drummer.

The other primary motive was to devise an electronic rhythm device which costs less than the \$100 or so demanded for even the cheapest commercial device.

The required variable offbeat was achieved by inserting another note between the regular beats, which can be adjusted to fall anywhere between the two beats, or in unison with one beat to give a stronger accent on that beat, or not to occur at all.

The final embellishment was the addition of a pure "A" tone for tuning purposes.

## Offbeat Circuits

Figure 1 shows the basic functional blocks of the circuit. The oscillator on the top left is one that may be used in any simple metronome project. Next to it is drawn an offbeat comparator block. This is specially designed to add an extra beat between the *tock* and *tick*, so that with the offbeat, the sound is something like *tick-bok-tock, tick-bok-tock*.

In order to have a tuning aid available, an accurate sine wave oscillator is included, with the aid of the mode switch the oscillator can be stopped from oscillating and instead used to provide a slightly resonant sound on the signal from the offbeat comparator.

## Pull And Twist

The controls (see photograph) are a pot governing the speed of the main rhythm, a small switch which pulls to turn the unit on, and rotates to control the volume; the pot which alters the relative position of the offbeat, and a two position switch which selects either the metronome or the "A" tone. The pull switch for on/off was chosen on the basis that pull switches don't wear out as fast as rotary switches with continual use, but an ordinary rotary on/off pot will do just as well.

First of all, the detailed functioning of the tuning oscillator: in order for a circuit to oscillate, it must receive feedback to its input with a phase shift on it, such that the phase change around the entire loop is 360 degrees. In this circuit, the

360° phase shift is achieved by one inversion and two 90° phase shifts. The integrator provides both the inversion and 90° phase shift over a wide range of frequencies. The low pass filter has a phase shift which depends on frequency, so it will only provide a 90° phase shift at one specific frequency.

So that the filter and the integrator can function without clipping, the feedback is taken via a clipper. The distortion produced by the clipper is filtered out by both the filter and the integrator, so that as long as neither the filter nor the integrator themselves clip, the output sine wave is very pure. Similarly, because the circuit is working in a linear mode, the frequency is stable and little affected by battery voltage.

IC1a (see Fig. 2) forms the filter, which is an ordinary low pass design, and IC1b forms the integrator. The clipping action is performed by a pair of back-to-back diodes, D2 and D3, with capacitor C4 preventing DC current through the diodes from upsetting the bias point of the op-amps.


The gain of the integrator is switched by switch SW1b. In the low gain position, where some signal is fed into the integrator from the offbeat comparator, the loop gain of the oscillator is insufficient to permit oscillation. However, when the circuit is excited by a sharp pulse, it will ring slightly, producing a somewhat hollow and resonant sound rather like striking a guitar body. In the metronome mode, this resonant sound is mixed with the basic metronome tone. Resistors R7 and R8 determine the proportion of signals used.

## Time Constant

The metronome oscillator itself uses IC1d. Positive feedback is applied to the op-amp; negative feedback is also applied, delayed by the time constant of C1 and the resistance of RV2 in series with R3.

The time per half cycle of the oscillator is set by the time required for C1 to charge between the voltages, which can be obtained on the positive terminal of IC1d, with the output in either of its two states.

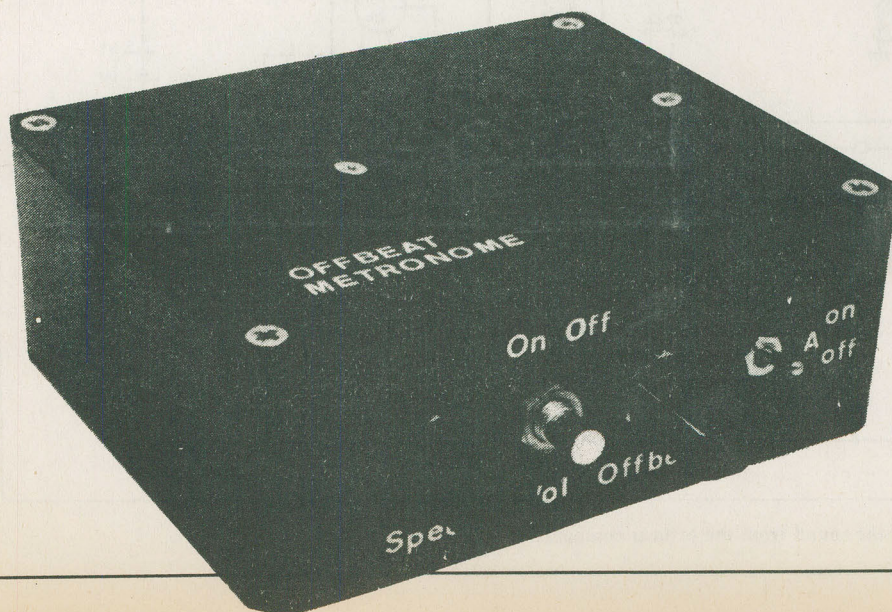This is shown on the waveform diagram, Figure 3. Also illustrated on the waveform diagram is the fact that the output stage of the IC used, an LM324, cannot pull equally as close to its positive power supply as to its negative power sup-





## Offbeat Metronome

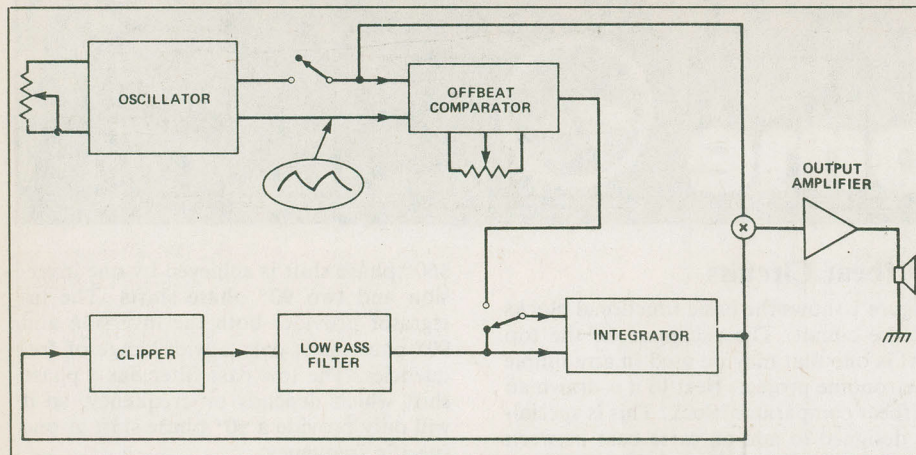


Fig. 1. The block diagram of the Offbeat Metronome.

ply. Thus, in order to maintain symmetry, to keep each half cycle of the oscillator the same length, a symmetry adjustment pot has been incorporated.

The waveform on C1 is also fed to IC1c's positive input. This part of the IC works as a comparator to insert the off-beat. When the output of IC1d is high, and C1 is therefore charging towards a positive voltage, and when the voltage on C1 crosses over the voltage set by the off-set pot, the output of IC1c switches in a positive direction.

If the offbeat pot is set to a high voltage so that this switching does not occur before the output of IC1d switches

low, then the output of IC1c will switch high at this moment. If the output of IC1c has switched high at all, it will switch low at the same moment that the output of IC1d switches high. Thus the return stroke of this comparator does not insert an extra offbeat, it merely modifies the sound of tick slightly. If the offbeat comparator is set at a lower voltage than that attained by C1, then the offbeat comparator will not switch at all, and in this mode an unaccented metronome sound is produced.

### Output Amplifier

The only part of the circuit not yet

described is the output amplifier. This very simple circuit uses a complimentary pair of transistors as emitter followers, to increase the output drive available from a 741 op-amp. These transistors are not biased into class A/B, so a certain amount of distortion is produced on the output. This distortion is not significant for the use to which the circuit is put. However, it does give rise to an interesting waveform on the output of the 741 itself, as the output voltage frantically attempts to compensate for the distortion being introduced by the transistors (see Fig. 4). As a result of this, the distortion produced is not very severe.

The volume control is of a linear type, and the way in which it is used produces an acceptable control law. Resistors R9 and capacitor C8 are included to prevent the possibility of self-oscillation of the circuit due to stray capacitance of the output stage, causing pickup on the wire from the wiper of RV4.

### Construction

First of all, build up the PCB as shown in Figure 5, inserting the ICs last. Connect the controls to the PCB using suitable lengths of wire. Take great care to make sure that both halves of the mode switch are wired up in the correct sense. Failure to do so could result in the metronome and the tuning note to be heard simultaneously! Note that the speed control of the

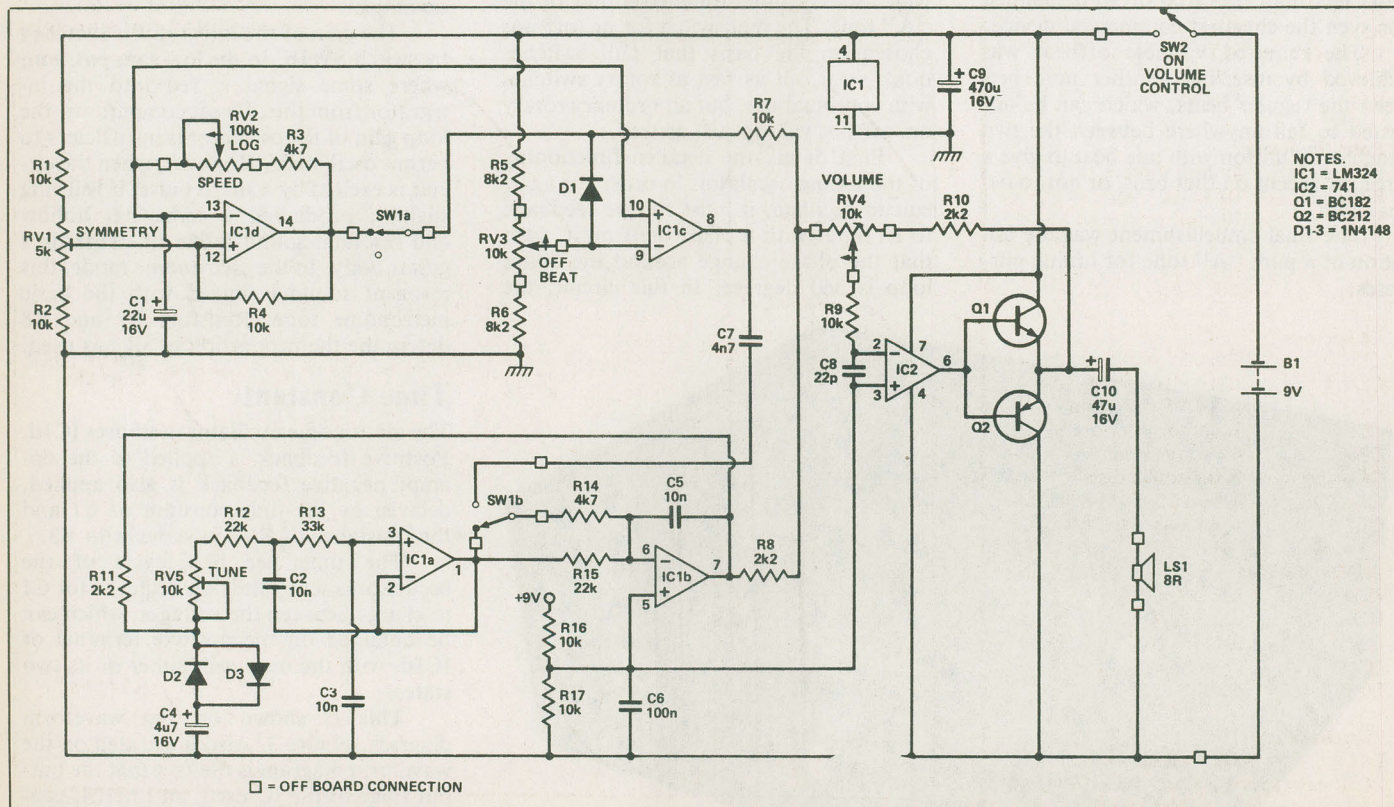


Fig. 2. The circuit. The tuning oscillator also modifies the sound from the offbeat comparator.



metronome is a logarithmic pot, wired up so that counter-clockwise rotation increases the speed. This is done in order to give finer control at the higher speeds.

Once all the controls are connected, the battery should be attached. Care should be taken to ensure that the polarity is correct! The unit should then be switched on, and then either a metronome beat or a tuning note should be heard. If the unit does not work properly, first check for badly soldered joints or solder bridges. If no such problems are found and the unit still does not work correctly, then try this list of remedies for likely problems:

1. Metronome does not work at all: check connections to RV2; check that C1 is in the board the right way around; check that the wiring to switch SW1a is correct.
2. Metronome works but offbeat function does not: check connections to RV3; check polarity of D1; check wiring to switch SW1b.
3. Tuning note will not work: check connections to switch SW1c; check polarity of C4; also check polarity of D2 and D3; check that half the battery voltage can be measured with an ordinary multimeter on IC1 pin 5; if not, check the *bias voltage* track for short circuits.

#### PARTS LIST

##### Resistors (All 1/4 watt 5% carbon)

R1,2,4,7,9,	
16,17	10k
R3,14	4k7
R5,6	8k2
R8,10,11	2k2
R12,15	22k
R13	33k

##### Potentiometers

RV1	5k horiz. preset
RV2	100k log pot.
RV3	10k lin. pot.
RV4	10k lin. pot. with SPST switch
RV5	10k horiz. preset

##### Capacitors

C1	22u 16V radial electro.
C2,3,5	10n polyester
C4	4u7 16 V tantalum
C6	100n polyester
C7	4n7 ceramic disc
C8	22p ceramic disc
C9	470u 16 V radial electro
C10	47u 16 V radial electro

##### Semiconductors

IC1	LM324
IC2	741
Q1	2N5825 etc.
Q2	2N6015 etc.
D1-3	1N4148

##### Miscellaneous

LS1	3 1/2" 8R speaker
PCB; case	approximately 120x100x45 mm;
nuts & bolts; wire, solder, etc.	

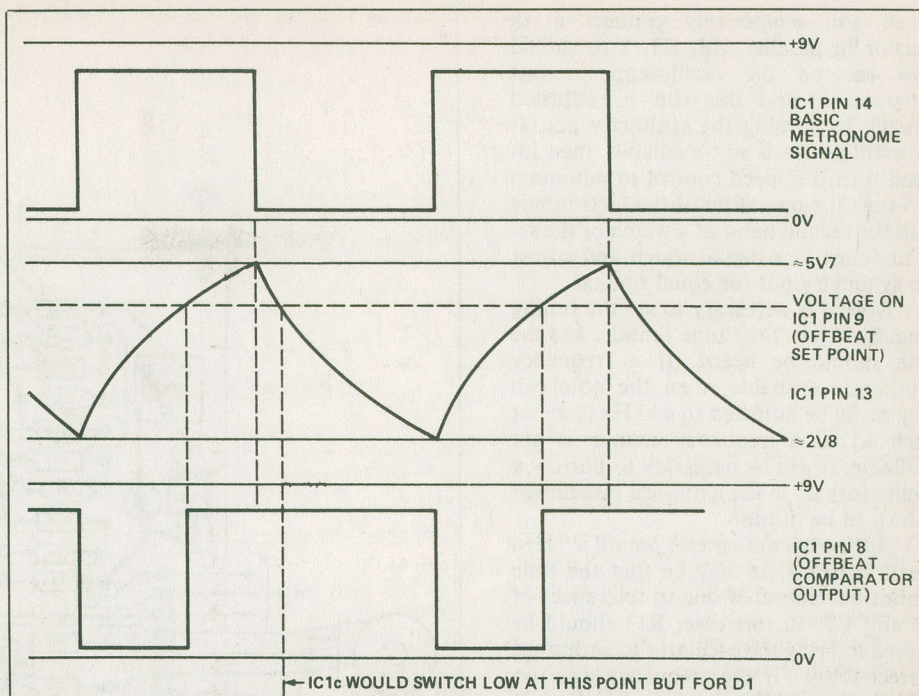


Fig. 3. The waveform diagram. The symmetry pot is included to compensate for the unequal positive/negative swing of the metronome signal.

4. No sound is heard at all: check wiring to battery and switch SW2; check wiring to RV4; check wiring to loudspeaker.

Hopefully, having carried out the checks, any fault will be identified, and you will now be faced with a working unit. The next job is to adjust the symmetry control to make sure that the time

between the *tick* and the *tock* and the *tock* and the *tick* on the metronome is the same.

First, set the offbeat control fully clockwise or fully counter-clockwise, so that the offbeat is not heard. If you have an oscilloscope, then connect the probe to IC1 pin 14, advance RV2 to maximum

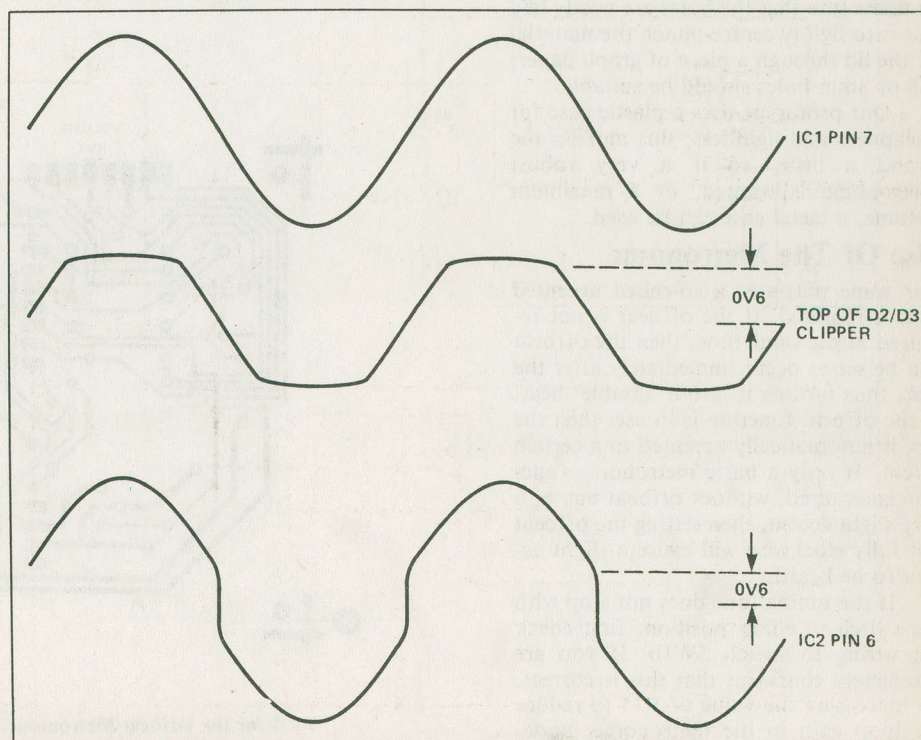


Fig. 4. The waveform at the output of IC2 (a 741) as it compensates for distortion produced by the transistors Q1 and 2.



## Offbeat Metronome

speed and temporarily connect a 1k resistor in parallel with R3. You should now see on the oscilloscope a fast squarewave, and this can be adjusted visually by turning the symmetry pot. If an oscilloscope is not available, then instead turn the speed control to minimum and time the operation of the metronome with the second hand of a watch or the second count of a digital watch and adjust the symmetry pot for equal timings.

Now it is necessary to set the tuning tone. Switch to the "tune" mode, and the tone should be heard. If a frequency counter is available, then the note can very easily be adjusted to 440 Hz (concert pitch A). If a frequency counter is not available, it will be necessary to borrow a tuning fork or to use a musical instrument known to be in tune.

Adjust the tune preset pot till a "zero beat" is heard. It may be that the tone cannot be calibrated due to tolerances of C2 and C3. In this case, R13 should be altered to bring the oscillator to within the correct range. If the frequency was too low, decrease R13 one step at a time. If the frequency was too high, increase R13, again one E12 step at a time.

The unit is now calibrated, and final assembly can be carried out. A row of four holes needs to be drilled in the front of the case to fit the potentiometers. Four holes should also be drilled in the base of the unit to fit the mounting bolts of the PC board. The loudspeaker should be mounted on the lid behind a grid of holes, drilled to let the sound out. The best way to make sure that the holes are neatly laid out is to lightly centre-punch the material of the lid through a piece of graph paper; 2.5 or 3mm holes should be suitable.

Our prototype uses a plastic case for cheapness and lightness; this muffles the sound a little, so if a very robust metronome is wanted, or a maximum volume, a metal case can be used.

### Use Of The Metronome

For some purposes a so-called accented beat is required. If the offbeat is not required at the same time, then the offbeat can be set to occur immediately after the *tick*, thus turning it into a 'double' beat. If the offbeat function is in use, then the *tick* is automatically accented to a certain extent. If only a basic metronome function is required, without offbeat but with very slight accent, then setting the offbeat pot fully clockwise will cause a slight accent to be heard.

If the tuning tone does not stop with the switch in either position, first check the wiring to switch SW1b. If you are completely confident that this is correct, try increasing the value of R15 to reduce the loop gain in the metronome mode. This should cure the problem.


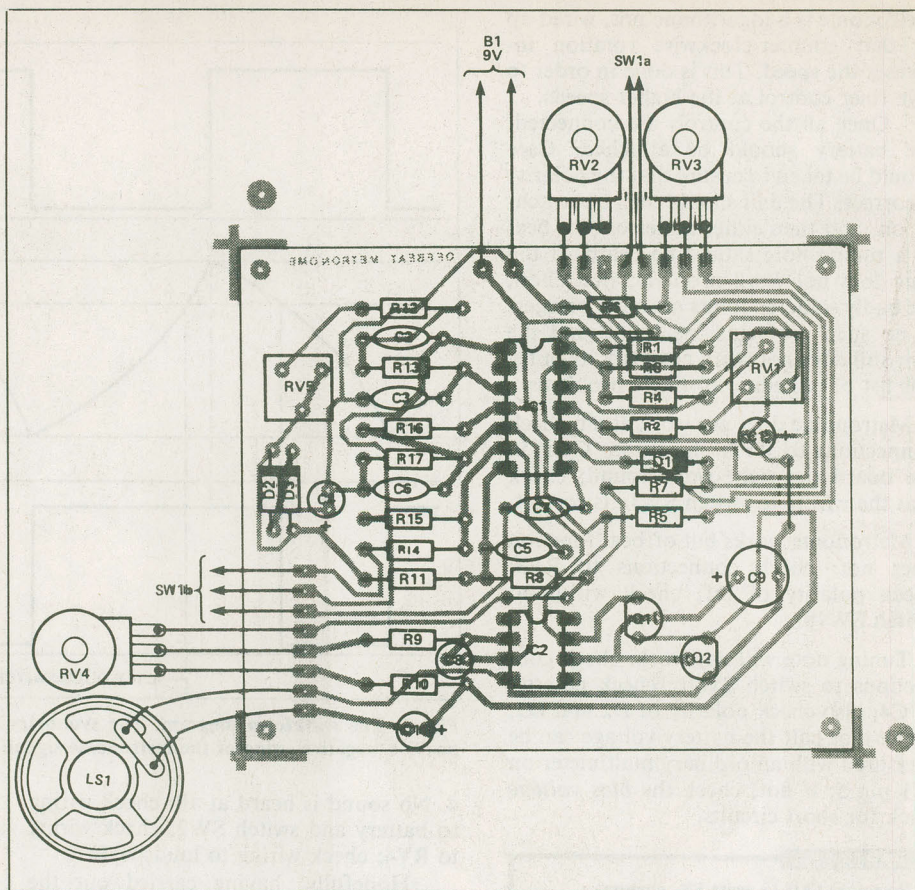


Fig. 5. The PCB overlay. The longer lengths of wire used to connect the switches make the mounting less fiddly, while not being so long as to be untidy.

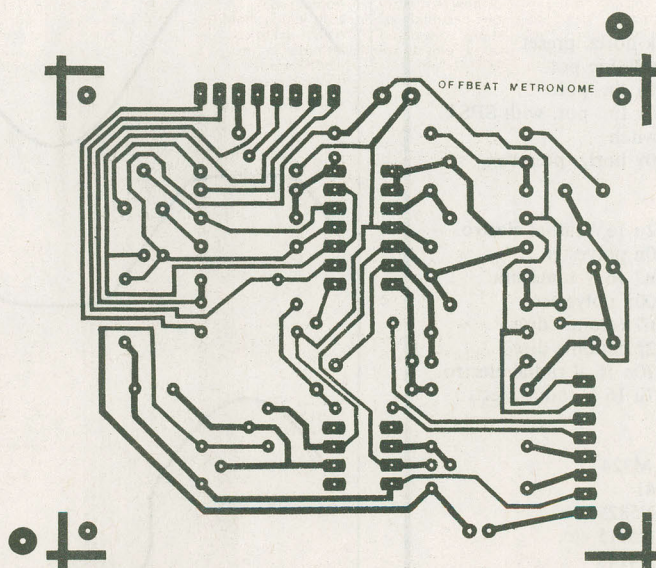

PCB for the Offbeat Metronome.





# Electronics Today Bookshelf

## Top 10 Electronic Books

Based on sales  
from  
**Moorshead  
Publications  
Book Service**

- 1 **BP73: REMOTE CONTROL PROJECTS** \$8.10  
**OWEN BISHOP**  
This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes, depending on personal requirements. Not only are radio control systems considered but also infra-red, visible light and ultrasonic systems as are the use of Logic ICs and Pulse position modulation etc.
- 2 **BP90: AUDIO PROJECTS** \$7.60  
**F.G. RAYER**  
Covers in detail the construction of a wide range of audio projects. The text has been divided into preamplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.
- 3 **The GIANT HANDBOOK OF ELECTRONIC CIRCUITS** \$27.95  
**TAB No.1300**  
About as twice as thick as the Webster's dictionary, and having many more circuit diagrams, this book is ideal for any experimenter who wants to keep amused for several centuries. If there isn't a circuit for it in here, you should have no difficulty convincing yourself you don't really want to build it.
- 4 **ELECTRONIC TROUBLESHOOTING HANDBOOK** \$11.95  
**AB019**  
This workbench guide can show you how to pinpoint circuit troubles in minutes, how to test anything electronic, and how to get the most out of low cost test equipment. You can use any and all of the time-saving shortcuts to rapidly locate and repair all types of electronic equipment malfunctions.
- 5 **BP74: ELECTRONIC MUSIC PROJECTS** \$7.20  
**R.A. PENFOLD**  
Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser-Units, Tremelo Generator etc.
- 6 **BP44: IC 555 PROJECTS** \$7.75  
**E.A. PARR, B.Sc., C.Eng., M.I.E.E.**  
Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

- 7 **BP37: 50 PROJECTS USING RELAYS, SCR's & TRIACS** \$7.75  
**F.G. RAYER, T.Eng.(CEI), Assoc.IERE**  
Relays, silicon controlled rectifiers (SCR's) and bi-directional triodes (TRIACS) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification of circuits or ready adaptation of them to individual needs.
- 8 **BP79: RADIO CONTROL FOR BEGINNERS** \$6.80  
**F.G. RAYER, T.Eng.(CEI), Assoc.IERE**  
The aim of this book is to act as an introduction to Radio Control for beginners to the hobby. The book will commence by dealing with the conditions that are allowable for such things as frequency and power of transmission. This is followed by a "block" explanation of how control-device and transmitter operate and receiver and actuator(s) produce motion in a model.  
Details are then given of actual solid state transmitting equipment which the reader can build. Plain and loaded aerials are then discussed and so is the field-strength meter to help with proper setting up.  
The radio receiving equipment is then dealt with which includes a simple receiver and also a crystal controlled superhet. The book ends with the electro-mechanical means of obtaining movement of the controls of the model.
- 9 **99 TEST EQUIPMENT PROJECTS YOU CAN BUILD** \$15.95  
**TAB No.805**  
An excellent source book for the hobbyist who wants to build up his work bench inexpensively. Projects range from a simple signal tracer to a 50MHz frequency counter. There are circuits to measure just about any electrical quantity: voltage, current, capacitance, impedance and more. The variety is endless and includes just about anything you could wish for!
- 10 **BP76: POWER SUPPLY PROJECTS** \$7.75  
**R.A. PENFOLD**  
Line power supplies are an essential part of many electronics projects. The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed voltage regulated types, and variable voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low voltage types for semiconductor circuits.  
There are other types of power supply and a number of these are dealt with in the final chapter, including a cassette power supply, Ni-Cad battery charger, voltage step up circuit and a simple inverter.

See order form in this issue.

## ELECTRONIC THEORY

ELEMENTS OF ELECTRONICS — AN ON-GOING SERIES	
F.A. WILSON, C.G.I.A., C.Eng.	
BP62: BOOK 1. The Simple Electronic Circuit and Components	1.70
BP63: BOOK 2. Alternating Current Theory	\$ 8.55
BP64: BOOK 3. Semiconductor Technology	\$ 8.55
BP77: BOOK 4. Microprocessing Systems And Circuits	\$11.70
BP89: BOOK 5. Communication	\$11.70

The aim of this series of books can be stated quite simply — it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

BOOK 1: This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

BOOK 2: This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.

BOOK 3: Follows on semiconductor technology, leading up to transistors and integrated circuits.

BOOK 4: A complete description of the internal workings of microprocessor.

BOOK 5: A book covering the whole communication scene.

**PH247: DIGITAL TECHNIQUES** \$29.00  
Covers logic circuits, Boolean Algebra, flip-flops, registers, combinational logic circuitry, and digital design.

## PROJECTS

- BP48: ELECTRONIC PROJECTS FOR BEGINNERS** \$7.75  
**F.G. RAYER, T.Eng.(CEI), Assoc.IERE**  
Another book written by the very experienced author — Mr. F.G. Rayer — and in it the newcomer to electronics, will find a wide range of easily made projects. Also, there are a considerable number of actual component and wiring layouts, to aid the beginner.  
Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and, thus, avoid the need for a soldering iron.  
Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.
- 221: 28 TESTED TRANSISTOR PROJECTS** \$5.00  
**R.TORRENS**  
Mr. Richard Torrens is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks, which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.
- BP71: ELECTRONIC HOUSEHOLD PROJECTS** \$7.20  
**R. A. PENFOLD**  
Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as '2 Tone Door Buzzer', Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.



# Electronics Today Bookshelf

## BP49: POPULAR ELECTRONIC PROJECTS \$7.75 R.A. PENFOLD

Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types: Radio Projects, Audio Projects, Household Projects and Test Equipment.

## BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$7.60 R.A. PENFOLD

Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Inverter.

## BP95: MODEL RAILWAY PROJECTS \$7.60

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects; stripboard layouts are provided for each project.

## BP93: ELECTRONIC TIMER PROJECTS \$7.60 F.G. RAYER

Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually.

## BP113: 30 Solderless Breadboard Projects-Book 2 \$8.85 R.A. Penfold

A companion to BP107. Describes a variety of projects that can be built on plug-in breadboards using CMOS logic IC's. Each project contains a schematic, parts list and operational notes.

## BP104: Electronic Science Projects \$8.85 Owen Bishop

Contains 12 electronic projects with a strong scientific flavour. Includes Simple Colour Temperature Meter, Infra-Red Laser, Electronic clock regulated by a resonating spring, a 'Scope with a solid state display, pH meter and electro-cardiograph.

## BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$7.60 R.A. PENFOLD

We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

## BP84: DIGITAL IC PROJECTS \$7.60 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike.

## BP67: COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS \$7.05 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Numeral indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits.

In this book many applications and projects using various types of numeral displays, popular counter and driver IC's etc. are considered.

## BP99: MINI-MATRIX BOARD PROJECTS \$7.60 R.A. PENFOLD

Twenty useful projects which can all be built on a 24 x 10 hole matrix board with copper strips. Includes Doorbuzzer, Low-voltage Alarm, AM Radio, Signal Generator, Projector Timer, Guitar Headphone Amp, Transistor Checker and more.

## BP103: MULTI-CIRCUIT BOARD PROJECTS \$7.60 R.A. PENFOLD

This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects.

## BP107: 30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1 \$8.85 R.A. PENFOLD

A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown.

## BP106: MODERN OP-AMP PROJECTS \$7.60 R.A. PENFOLD

Features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra-high input impedance, high slew-rate and high output current types.

## CIRCUITS

### How to Design Electronic Projects

#### BP127 \$8.95

Although information on standard circuit blocks is available, there is less information on combining these circuit parts together. This title does just that. Practical examples are used and each is analysed to show what each does and how to apply this to other designs.

### Audio Amplifier Construction

#### BP122 \$8.95

A wide circuits is given, from low noise microphone and tape head preamps to a 100W MOSFET type. There is also the circuit for 12V bridge amp giving 18W. Circuit board or strip-board layout are included. Most of the circuits are well within the capabilities for even those with limited experience.

### Electronic Circuits for Model Railways

#### BP213 \$4.50

Lots of circuits including three types of controllers including one with simulated inertia and one with high power. Signalling and lighting systems are discussed at length and the suppression of RF interference. There are also 4 "steam whistle" and "chuffer" circuits.

## BP80: POPULAR ELECTRONIC CIRCUITS - BOOK 1 \$7.75 R.A. PENFOLD

Another book by the very popular author, Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings: Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits.

## BP98: POPULAR ELECTRONIC CIRCUITS, BOOK 2 \$8.85 R.A. PENFOLD

70 plus circuits based on modern components aimed at those with some experience.

## BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$6.75 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Field effect transistors (FETs), find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home.

This book contains something of particular interest for every class of enthusiast - short wave listener, radio amateur, experimenter or audio devotee.

## BP87: SIMPLE L.E.D. CIRCUITS \$5.40 R.N. SOAR

Since it first appeared in 1977, Mr. R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on.

## BP42: 50 SIMPLE L.E.D. CIRCUITS \$5.75 R.N. SOAR

The author of this book, Mr. R.N. Soar, has compiled 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components - the Light Emitting Diode (L.E.D.). A useful book for the library of both beginner and more advanced enthusiast alike.

## THE ACTIVE FILTER HANDBOOK \$13.95 TAB No.1133

Whatever your field - computing, communications, audio, electronic music or whatever - you will find this book the ideal reference for active filter design.

The book introduces filters and their uses. The basic math is discussed so that the reader can tell where all design equations come from. The book also presents many practical circuits including a graphic equalizer, computer tape interface and more.

## MASTER HANDBOOK OF 1001 PRACTICAL CIRCUITS \$26.50 TAB No.800

## MASTER HANDBOOK OF 1001 MORE PRACTICAL CIRCUITS \$23.95 TAB No.804

Here are transistor and IC circuits for just about any application you might have. An ideal source book for the engineer, technician or hobbyist. Circuits are classified according to function, and all sections appear in alphabetical order.

## BP88: HOW TO USE OP AMPS \$8.85 E.A. PARR

A designer's guide covering several op amps, serving as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

## BP65: SINGLE IC PROJECTS \$6.05 R.A. PENFOLD

There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used.

## BP117: PRACTICAL ELECTRONIC BUILDING BLOCKS BOOK 1 \$7.60

Virtually any electronic circuit will be found to consist of a number of distinct stages when analysed. Some circuits inevitably have unusual stages using specialised circuitry, but in most cases circuits are built up from building blocks of standard types.

This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects rather than simply follow published project designs.

The circuits for a number of useful building blocks are included in this book. Where relevant, details of how to change the parameters of each circuit are given so that they can easily be modified to suit individual requirements.

## 223: 50 PROJECTS USING IC CA3130 \$5.00 R.A. PENFOLD

In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories: I - Audio Projects II - R.F. Projects III - Test Equipment IV - Household Projects V - Miscellaneous Projects.

## 224: 50 CMOS IC PROJECTS \$5.25 R.A. PENFOLD

CMOS IC's are probably the most versatile range of digital devices for use by the amateur enthusiast. They are suitable for an extraordinary wide range of applications and are also some of the most inexpensive and easily available types of IC.

Mr. R.A. Penfold has designed and developed a number of interesting and useful projects which are divided into four general categories: I - Multivibrators II - Amplifiers and Oscillators III - Trigger Devices IV - Special Devices.

## THE MASTER IC COOKBOOK \$17.95 TAB No.1199

If you've ever tried to find specs for a so called 'standard' chip, then you'll appreciate this book. C.L. Hallmark has compiled specs and pinout for most types of ICs that you'd ever want to use.

## BP118: PRACTICAL ELECTRONIC BUILDING BLOCKS - Book 2 \$7.60 R.A. PENFOLD

This sequel to BP117 is written to help the reader create and experiment with his own circuits by combining standard type circuit building blocks. Circuits concerned with generating signals were covered in Book 1, this one deals with processing signals. Amplifiers and filters account for most of the book but comparators, Schmitt triggers and other circuits are covered.

## BP24: 50 PROJECTS USING IC741 \$6.75 RUDI & UWE REDMER

This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics.

## BP83: VMOS PROJECTS \$7.70 R.A. PENFOLD

Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with VMOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits.

## BP50: IC LM3900 PROJECTS \$5.40 H. KYBETT, B.Sc., C.Eng.

The purpose of this book is to introduce the LM3900 to the Technician, Experimenter and the Hobbyist. It provides the groundwork for both simple and more advanced uses, and is more than just a collection of simple circuits or projects.

Simple basic working circuits are used to introduce this IC. The LM3900 can do much more than is shown here, this is just an introduction. Imagination is the only limitation with this useful and versatile device. But first the reader must know the basics and that is what this book is all about.

## ELECTRONIC DESING WITH OFF THE SHELF INTEGRATED CIRCUITS \$12.95 AB016

This practical handbook enables you to take advantage of the vast range of applications made possible by integrated circuits. The book tells how, in step by step fashion, to select components and how to combine them into functional electronic systems. If you want to stop being a "cookbook hobbyist", then this is the book for you.

See order form in this issue.



# Electronics Today Bookshelf

## RADIO AND COMMUNICATIONS

### BP96: CB PROJECTS \$7.60

**R.A. PENFOLD**  
Projects include speech processor, aerial booster, cordless mike, aerial and harmonic filters, field strength meter, power supply, CB receiver and more.

### 222: SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS \$7.60

**R.A. PENFOLD**  
In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components.

### BP91: AN INTRODUCTION TO RADIO DXing \$7.60

This book is divided into two main sections one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described.

### BP105: AERIAL PROJECTS \$7.60

**R.A. PENFOLD**  
The subject of aerials is vast but in this book the author has considered practical designs including active, loop and ferrite aerials, which give good performances and are reasonably simple and inexpensive to build. The complex theory and math of aerial design are avoided.

### BP125: 25 Simple Amateur Band Aerials \$7.60

**E.M. NOLL**  
Starting from simple dipoles through beam, triangle and even mini-rhombics (made from TV masts and 400ft of wire) this title describes several simple and inexpensive aerials to construct yourself. A complete set of dimension table are included.

### BP46: RADIO CIRCUITS USING IC's \$5.40

**J.B. DANCE, M.Sc.**  
This book describes integrated circuits and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. The chapter on amplitude modulated (a.m.) receivers will be of most interest to those who wish to receive distant stations at only moderate audio quality, while the chapter on frequency modulation (f.m.) receivers will appeal to those who desire high fidelity reception.

### BP92: ELECTRONICS SIMPLIFIED — CRYSTAL SET CONSTRUCTION \$6.80

**F.A. WILSON**  
Aimed at those who want to get into construction without much theoretical study. Homewound coils are used and all projects are very inexpensive to build.

### BP70: TRANSISTOR RADIO FAULT-FINDING CHART \$2.50

**CHAS. E. MILLER**  
Across the top of the chart will be found four rectangles containing brief descriptions of various faults; viz: — sound weak but undistorted; set dead; sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

## AUDIO

### 205: FIRST BOOK OF HI-FI LOUDSPEAKER ENCLOSURES \$3.75

**B.B. BABANI**  
This book gives data for building most types of loudspeaker enclosure. Includes corner reflex, bass reflex, exponential horn, folded horn, tuned port, klipschorn labyrinth, tuned column, loaded port and multi speaker panoramic. Many clear diagrams for every construction showing the dimensions necessary.

### HOW TO BUILD A SMALL BUDGET RECORDING STUDIO FROM SCRATCH... \$15.95

**TAB No.1166**  
The author, F. Alton Everest, has gotten studios together several times, and presents twelve complete, tested designs for a wide variety of applications. If all you own is a mono cassette recorder, you don't need this book. If you don't want your new four track to wind up sounding like one, though, you shouldn't be without it.

### BP51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING \$7.75

**M.K. BERRY**  
Electronic music is the new music of the Twentieth Century. It plays a large part in "pop" and "rock" music and, in fact, there is scarcely a group without some sort of synthesiser or other effects generator.

This book sets out to show how electronic music can be made at home with the simplest and most inexpensive of equipment. It then describes how the sounds are generated and how these may be recorded to build up the final composition.

### BP81: ELECTRONIC SYNTHESISER PROJECTS \$6.80

**M.K. BERRY**  
One of the most fascinating and rewarding applications of electronics is in electronic music and there is hardly a group today without some sort of synthesiser or effects generator. Although an electronic synthesiser is quite a complex piece of electronic equipment, it can be broken down into much simpler units which may be built individually and these can then be used or assembled together to make a complete instrument.

### ELECTRONIC MUSIC SYNTHESIZERS \$10.95

**TAB No.1167**  
If you're fascinated by the potential of electronics in the field of music, then this is the book for you. Included is data on synthesizers in general as well as particular models. There is also a chapter on the various accessories that are available.

## TEST EQUIPMENT

### BP75: ELECTRONIC TEST EQUIPMENT CONSTRUCTION \$6.80

**F.G. RAYER, T.Eng. (CEI), Assoc. IERE**  
This book covers in detail the construction of a wide range of test equipment for both the Electronics Hobbyists and Radio Amateur. Included are projects ranging from an FET Amplified Voltmeter and Resistance Bridge to a Field Strength Indicator and Heterodyne Frequency Meter. Not only can the home constructor enjoy building the equipment but the finished projects can also be usefully utilised in the furtherance of his hobby.

### THE POWER SUPPLY HANDBOOK \$15.95

**TAB No.866**  
A complete one stop reference for hobbyists and engineers. Contains high and low voltage power supplies of every conceivable type as well mobile and portable units.

## REFERENCE

### BP85: INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE \$11.75

**ADRIAN MICHAELS**  
This book will help the reader to find possible substitutes for a popular user-orientated selection of modern transistors. Also shown are the material type, polarity, manufacturer selection of modern transistors. Also shown are the material type, polarity, manufacturer and use. The Equivalents are sub-divided into European, American and Japanese. The products of over 100 manufacturers are included. An essential addition to the library of all those interested in electronics, be they technicians, designers, engineers or hobbyists. Fantastic value for the amount of information it contains.

### BP108: INTERNATIONAL DIODE EQUIVALENTS GUIDE \$8.95

**ADRIAN MICHAELS**  
This book is designed to help the user in finding possible substitutes for a large user orientated selection of the many different types of semiconductor diodes that are available today. Besides simple rectifier diodes also included are Zener diodes, LEDs, Diacs Triacs, Thyristors, Photo diodes and Display diodes.

### BP1: FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES \$5.75

**B.B. BABANI**  
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in Great Britain, USA, Japan, Germany, France, Europe, Hong Kong, and includes types produced by more than 120 different manufacturers.

### BP14: SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES \$6.75

**B.B. BABANI**  
The "First Book of Transistor Equivalents" has had to be reprinted 15 times. The "Second Book" produced in the same style as the first book, in no way duplicates any of the data presented in it. The "Second Book" contains only additional material and the two books complement each other and make available some of the most complete and extensive information in this field. The interchangeability data covers semiconductors manufactured in Great Britain, USA, Germany, France, Poland, Italy, East Germany, Belgium, Austria, Netherlands and many other countries.

### TOWER'S INTERNATIONAL OP-AMP LINEAR IC SELECTOR \$17.95

**TAB No.1216**  
This book contains a wealth of useful data on over 5,000 Op-amps and linear ICs — both pinouts and essential characteristics. A comprehensive series of appendices contain information on specs, manufacturers, case outlines and so on.

### CMOS DATABASE \$12.50

**TAB No.984**  
There are several books around with this title, but most are just collections of manufacturers' data sheets. This one, by Bill Hunter, explains all the intricacies of this useful family of logic devices... the missing link in getting your own designs working properly. Highly recommended to anyone working with digital circuits.

See order form in this issue.

## ROBOTICS

### THE COMPLETE HANDBOOK OF ROBOTICS \$15.95

**TAB No.1071**  
All the information you need to build a walking, talking mechanical friend appears in this book. Your robot can take many forms and various options — light, sound, and proximity sensors — are covered in depth.

### HOW TO BUILD YOUR OWN SELF PROGRAMMING ROBOT \$13.95

**TAB No.1241**  
A practical guide on how to build a robot capable of learning how to adapt to a changing environment. The creature developed in the book, Rodney, is fully self programming, can develop theories to deal with situations and apply those theories in future circumstances.

### BUILD YOUR OWN WORKING ROBOT \$10.95

**TAB No.841**  
Contains complete plans — mechanical, schematics, logic diagrams and wiring diagrams — for building Buster. Buster is a sophisticated experiment in cybernetics you can build in stages. There are two phases involved: first Buster is leashed, dependent on his creator for guidance; the second phase makes Buster more independent and able to get out of tough situations.

## VIDEO

### BP100: AN INTRODUCTION TO VIDEO \$7.60

**D.K. MATHEWSON**  
Presents in as non-technical a way as possible how a video recorder works and how to get the best out of it and its accessories. Among the items discussed are the pros and cons of the various systems, copying and editing, international tape exchange and understanding specifications.

### Tab1519: ALL ABOUT HOME SATELLITE TELEVISION \$22.95

Covers such aspects as where to buy, problems in setting up your TVRO station and how to solve them, antenna siting and equipment selection.

### Tab1490: VIDEO CASSETTE RECORDERS: BUYING, USING AND MAINTAINING \$14.95

A complete handbook for the video enthusiast. You'll learn about how the systems work and how to choose as well as take a technical look at the inside workings. There are also sections on making your own video recordings.

## MISCELLANEOUS

### PH255: COMPLETE GUIDE TO READING SCHEMATIC DIAGRAMS, 2nd Edition \$11.95

**J. DOUGLAS-YOUNG**  
Packed with scores of easy-to-understand diagram and invaluable troubleshooting tips as well as a circuit finder chart and a new section on logic circuits.

### BP101: HOW TO IDENTIFY UNMARKED IC'S \$2.75

**K.H. RECORR**  
Originally published as a feature in 'Radio Electronics', this chart shows how to record the particular signature of an unmarked IC using a test meter, this information can then be used with manufacturer's data to establish the application.

### BASIC TELEPHONE SWITCHING SYSTEMS \$17.95

**TAB No.1166**  
The Revised Second Edition of this book, for trainee and engineer alike, includes updated statistical data on telephone stations, and new and improved signaling methods and switching techniques. It also includes E & M signaling interface for electronic central offices and automatic number identification methods used in step-by-step, panel and crossbar central offices.

### PH252: DIGITAL IC's: HOW THEY WORK AND HOW TO USE THEM \$10.95

**A. BARBER**  
The dozens of illustrations included in this essential reference book will help explain time-saving test procedures, interpreting values, performing voltage measurements, and much more!

### AUDIO AND VIDEO INTERFERENCE CURES \$8.95

**KAHANER**  
A practical work about interference causes and cures that affect TV, radio, hi-fi, CB, and other devices. Provides all the information needed to stop interference. Schematic wiring diagrams of filters for all types of receivers and transmitters are included. Also, it supplies simple filter diagrams to eliminate radio and TV interference caused by noisy home appliances, neon lights, motors, etc.

### BP121: How to Design and Make Your Own PCB's \$7.60

**R.A. Penfold**  
The emphasis is on practical rather than theoretical techniques. Starts by giving simple methods of copying from magazines, carries on with photographic methods of producing PCBs and continues with layout design.



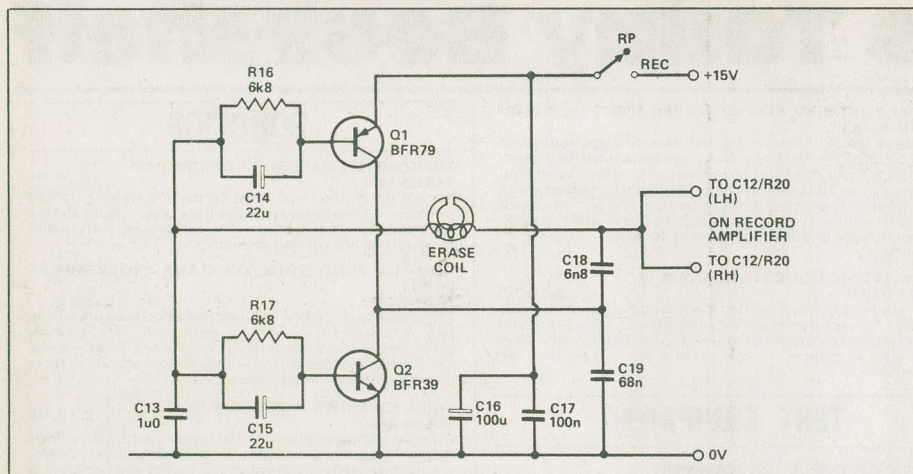


Fig. 15. A cassette recorder bias and erase oscillator.

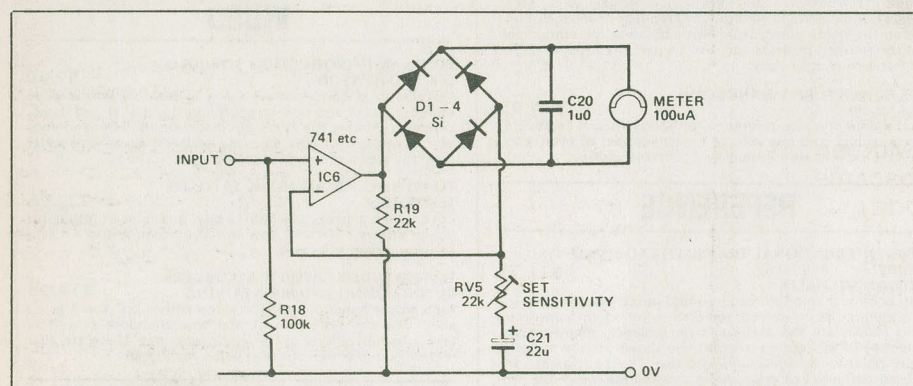


Fig. 16. A simple recording level meter circuit.

V supplies. It has to provide a means for adjusting the record signal level. It has to provide a modicum of bass lift, say +3 dB at 50 Hz and +6 dB at 30 Hz, to compensate for the specified roll-off in the replay curve. It has to provide the specified de-emphasis at 70 $\mu$ S or 120  $\mu$ S as required, and finally, it has to generate a peak, of +15 dB or so, at 15 kHz, to offset the head losses.

A circuit which will meet these requirements, and give a high quality performance, is shown in Fig. 14. In this, IC3 is a simple unity gain buffer amplifier, which has a low output impedance but yet allows a high impedance input to the record level control. R9, R10, C6 and S2 generate the 70 and 120 $\mu$ S de-emphasis characteristics. Since we have calculated suitable values for these for the replay amp., we can use these again. R11 is a trimmer resistor which we can use to assist in getting an optimally flat overall frequency response, by lessening the extent of this de-emphasis. IC4 is a gain stage with a low-frequency gain of 5.7. However, the LCR network formed by L1, C8 and RV4 is tuned to resonate at 15 kHz; this makes the gain increase at this frequency to an extent which is governed

by the Q of the circuit, which can be adjusted by RV4 (for the tuned circuit,  $f_0 = \frac{1}{2} LC$ ).

R11, R12 and C9 generate the boost at 50 Hz (3180  $\mu$ S, the time constant of C9R11) and the levelling off at 30 Hz (5300  $\mu$ S, the time constant of C9 (R11 + R12)). IC5 is another straight gain stage, with a gain of 5.7, and this drives the record head through C11 and R19.

Overall, the gain of this amplifier is 30 at 1 kHz, which allows a 5 V RMS output from IC5 for a 170 mV input. Bias is applied to the head directly from the bias oscillator circuit.

## Bias and Erase Oscillator

In reel-to-reel recorders, and in the rather more up-market cassette decks, a separate transformer would be used, both as the coil in the LC erase oscillator, and as a transformer coupling from a secondary winding to drive the erase coils and HF bias circuitry. However, in cassette recorders, provided it is not proposed to use 'metal' tape (for which very high erase voltages across the erase head are needed to achieve the required 60 dB erasure of previously recorded signals), it is quite satisfactory to use the erase head itself as

the coil in the oscillator circuit, and up to 25 V RMS can be generated by the oscillator circuit shown in Fig. 15. A small proportion of this is then bled off through an RC network to bias the record head.

The actual RMS bias voltage across the head for optimum recording characteristics must be determined by experience for the record head and tape being used, but it will probably lie somewhere between 5.5 and 10 V RMS, as measured by a wide-bandwidth AC milli-voltmeter. Understandably, from Figs. 10 and 11, there is no such thing as a 'correct' bias voltage setting. All that one can do is to try to choose a voltage at which all of the conflicting tape characteristics are partially satisfied, in your own judgment. As simple a solution as any is to design the record and replay amps so that they give a reasonably good frequency response, and then trim the 'bias' voltage so that the overall frequency response is as level as possible. Obviously, if one has good instruments and a lot of time to experiment, a better compromise value could be found.

## In Conclusion

These then are the basics of tape recording, and the circuits shown above, when used with a suitable cassette mechanism, an adequate power supply (derived for example from a pair of + and - output 12 or 15 V IC stabilizers and a decent quality pair of supply line bypass capacitors) and some form of recording level indicator which could well be a simple one-IC AC millivoltmeter of the form shown in Fig. 16, could be used to make a quite high performance DIY cassette recorder. However, being realistic, I do not really believe that anyone would want to build a cassette recorder — unless of course, they had most of the parts already at hand — when they could buy one, ready built, and with all the trimmings, for about two thirds of the wholesale price of the components.


Nevertheless, it is useful to know what kind of circuitry is employed in tape recorders, and what the problems and limitations are, so that one might rebuild or modify existing unsatisfactory equipment, or simply know where the strengths and weaknesses of the method lie. Also, because every tape or cassette recorder represents the end product of a very large number of design compromises, which affect distortion, modulation noise, overload characteristics, flatness of response and background noise level, as well as the straightforward HF bandwidth, cassette and reel to reel tape recorders differ in sound quality, one from another, very much more than, say, audio amplifiers or tuners do. Evaluation of the effect of these many compromises is truly an appropriate field for the 'subjective' listener.

ETI


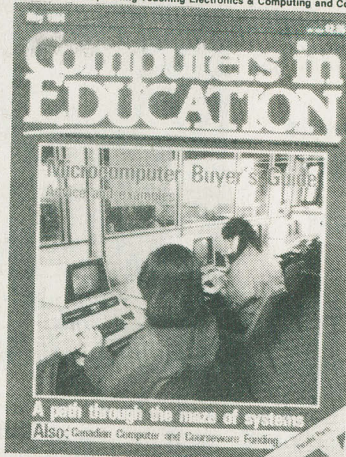
# Computers in EDUCATION

A Moorshead Publication, Incorporating Teaching Electronics & Computing and Computers in the Classroom.



Computers in Education is Canada's magazine for the teacher or others involved with microcomputing, and comes from Moorshead Publications, the publishers who became industry leaders with Electronics Today, Computing Now!, and soon Software Now!.

There are news articles on the latest events and technology, beginner's guides to languages and software, software and book reviews, build-it-yourself projects, technical tips, and more.

In recent issues, for instance, Computers in Education covered the Icon educational computer and user's reactions to it, Logo, word processing for the classroom, simple cures for hardware problems, how disk systems work, a BASIC tutorial, and more.

## YES, I want to subscribe!

Send me 10 issues of Computers in Education  
Payment of \$25 is enclosed ☐; I prefer 20 issues at \$45 ☐; Bill me ☐. I understand that if I am not completely satisfied, I may cancel my subscription at any time and receive a refund.

Please indicate occupation and level at which you teach: (if applicable)

- |                                      |   |   |                                     |
|--------------------------------------|---|---|-------------------------------------|
| <input type="checkbox"/> Principal   | <input type="checkbox"/> Librarian          | <input type="checkbox"/> Teacher/Lecturer | <input type="checkbox"/> Consultant |
| <input type="checkbox"/> Other _____ |   |   |                                     |
| <input type="checkbox"/> Elementary  | <input type="checkbox"/> Jr. High School    |   |                                     |
| <input type="checkbox"/> High School | <input type="checkbox"/> Community College  |   |                                     |
| <input type="checkbox"/> University  | <input type="checkbox"/> Board of Education |   |                                     |
| <input type="checkbox"/> Government  | <input type="checkbox"/> Other _____        |   |                                     |

Name \_\_\_\_\_

Name of School (if applicable) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

Province \_\_\_\_\_ Postal Code \_\_\_\_\_

MAIL TO: Moorshead Publications, Suite 601, 25 Overlea Blvd.,  
Toronto, Ontario M4H 1B1



# Book of the Month

## An Introduction to Radio DXing


by R.A. Penfold

List Price: \$7.60

Number BP91

## An Introduction to Radio DXing

R.A. PENFOLD

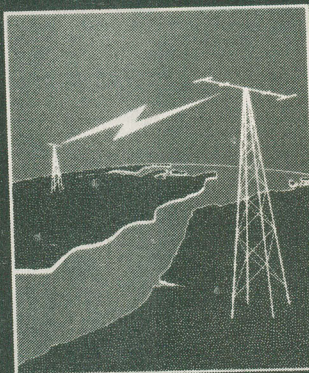

Radio DXing, the art of tuning in to distant radio broadcasts, is a hobby enjoyed by many. This book contains two sections: one dealing with amateur band reception, and the other with broadcast bands. Advice on equipment and techniques, as well as a number of related projects are also included.

Available from: Moorshead Publications 25 Overlea Blvd. Suite 601, Toronto, Ontario M4H 1B1 (416) 423-3262

See order form in this issue. All prices include shipping. No sales tax applies.

# Apple Wordstar Fixer

Apples and Wordstar are not entirely friendly. Apple compatible systems equipped with Videx type eighty-column cards do a number of unpleasant things to this popular word processor. While there are simple cures for this... they all involve some delicate code hacking.

The Fixer solves this problem. Place it on the same disk as your copy of WS.COM, type FIXER and after a suitable amount of disk noise, you will have APWS.COM on there too. This version of Wordstar includes special patching and unhooking code which runs each time you boot Wordstar, and makes your fruit behave as it should. It releases the control K's, translates the left arrow key to a delete character, and patches Unitron keyboards.

In addition all of this, the fixer allows you to set some of the defaults of Wordstar which the MicroPro INSTALL Package doesn't really get to. All of these features are menu driven in English for absolute non-technical operation.

Fixed Wordstar will run in either 44K or 56K CP/M.


Only

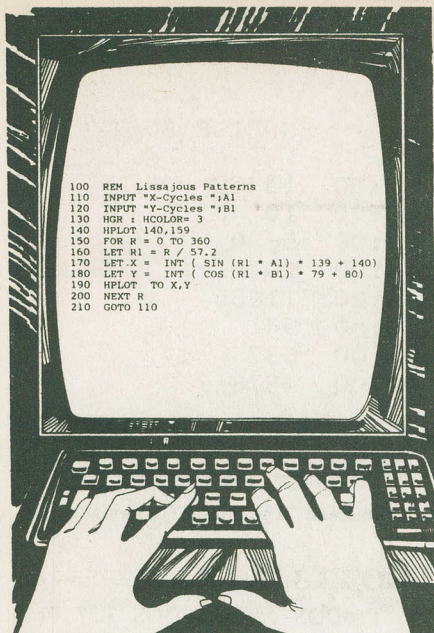**\$19.95**

*Ontario residents please add seven percent*

**Electronics Today Software**  
**25 Overlea Boulevard, Suite 601**  
**Toronto, Ontario**  
**M4H 1B1**





A look at Apple's new Disk Operating System.

# Computing Today

## Apple ProDOS

by Yin H. Pun

HAILED AS the successor of the aging DOS 3.3, ProDOS has beautiful structure, powerful in all respects; it has similarities to many main-frame operating systems. Here is a comparison of ProDOS to the usual Apple DOS 3.3.

ProDOS was released in January 1984, and it is highly structured and more complex than DOS 3.3, having borrowed from CP/M and Pascal. ProDOS even supports the use of a clock card (A Thunderclock or similar) since all files are dated when they are created or modified. ProDOS permits the use of a "binary" tree called a "pathway" that tells which way a program is loaded. The speed of the loading and saving is about 2 to 5 times faster than an unmodified DOS 3.3.

### Hardware Requirements

ProDOS needs no special modification of the basic hardware, an Apple II and a disk drive with controller; no new disk controller PROMs are necessary. However, it does require 64K of RAM and Applesoft in ROM at least; Apple II and II pluses must have a 16K RAMcard. Apple IIes and IIc's already have 64K built-in. ProDOS, like the DOS 3.3, PASCAL and CP/M operating systems, is recorded on 16-sector disks (whereas DOS 3.2 is a 13-sector disk). A ProDOS disk may be read on the sector level with no difficulty. This means that a ProDOS may be copied with a normal 16-sector copy program, such as the popular COPYA on the DOS 3.3 system master. However, the way the information is organized on the disk is totally different.

### The User's Disk

A disk of utilities is provided with ProDOS, along with a User's Disk Manual. It contains a FILER program, a disk utility analogous to DOS 3.3's FID and COPYA,

used to copy files and whole disks. ProDOS, following the Pascal convention, calls disks "VOLUMES". A "VOLUME" may be a floppy or a hard disk, and is treated in the same way from the user's point of view. CONVERT is to ProDOS as MUFFIN is to DOS 3.3. It converts DOS 3.3 and ProDOS files back and forth. However, not all files may work under their foreign environments due to the differences in the two operating systems. The

STARTUP program shows what you have in the slots of your computer and can set the time if you do not have a clock card. All of these utilities include a helpful tutor which can be requested at any time to describe the use of a command. The classic, ANIMALS, an animal guessing game that learns while you play it, is included too.

### New Catalog

Most of the DOS 3.3 commands are retained in ProDOS. However, the CATALOG command is different in its usage. CATALOG results in a very informative 80-column listing, but is rather hard to read when you have only 40 columns since everything "wraps around". CAT results in a truncated 40-column listing. The DISK VOLUME number is replaced by a "prefix", the title of the disk. It can be up to 34 characters long. The directory also tells when files were created and updated if a clock card is installed. The "ENDFILE" column indicates the number of bytes that a file takes up. The "SUBTYPE" indicates the starting address of binary files and the number of records in random access text files. Instead of using the regular slot and drive parameters in the CATALOG command (i.e. CATALOG, S6, D1), you can specify the prefix instead (i.e. CATALOG/USERS.DISK/). ProDOS will go through each available disk drive and search for the disk. Otherwise it will say "PATH NOT FOUND". Don't be intimidated when you see the word "BLOCKS": ProDOS again follows the PASCAL convention of calling two disk sectors (512 bytes of memory) a "BLOCK". Therefore, files can only have an even number of sectors. A ProDOS disk stores the same total amount of memory as a DOS 3.3 disk: 280 BLOCKS or 560 sectors. The ProDOS directory presents a

#### ]CATALOG

#### DISK VOLUME 254

```
*A 003 HELLO
*I 003 APPLESOFT
*B 006 LOADER.OBJO
*B 042 FPBASIC
*B 042 INTBASIC
*A 003 MASTER
*B 009 MASTER CREATE
*I 009 COPY
*B 003 COPY.OBJO
*A 009 COPYA
*B 003 CHAIN
*A 014 RENUMBER
*A 003 FILEM
*B 020 FID
*A 003 CONVERT13
*B 027 MUFFIN
*A 003 START13
*B 007 BOOT13
*A 004 SLOT#
```

Fig 1. A directory listing of a DOS 3.3 disk (The DOS 3.3 System Master) by the "CATALOG" command.



/USERS.DISK

NAME	TYPE	BLOCKS	MODIFIED	CREATED	ENDFILE	SUBTYPE
*PRODOS	SYS	31	1-JAN-84 0:00	1-JAN-84 0:00	15360	
*BASIC.SYSTEM	SYS	21	15-NOV-83 0:00	15-NOV-83 0:00	10240	
*FILER	SYS	51	1-JAN-84 0:00	1-JAN-84 0:00	5600	
*CONVERT	SYS	42	1-NOV-83 0:00	1-NOV-83 0:00	20481	
*STARTUP	BAS	24	15-OCT-83 0:00	15-OCT-83 0:00	11465	
*MOIRE	BAS		15-OCT-83 0:00	15-OCT-83 0:00	941	
*HYPNOSIS	BAS	3	15-OCT-83 0:00	15-OCT-83 0:00	637	
*ANIMALS	BAS	10	15-OCT-83 0:00	15-OCT-83 0:00	4578	
BLOCKS FREE:	88	BLOCKS USED:	192	TOTAL BLOCKS:	280	

Fig 2. An 80-column directory listing of a Pro DOS disk (The USER's DISK) by the "CATALOG" command. The "CAT" command lists only the left half in 40 columns.

significant improvement over the old DOS 3.3 directory.

## Command Differences

A number of DOS commands are missing from ProDOS and will cause a syntax error if they are used. The INIT command to format a disk is no longer supported. A disk must be initialized using the FILER program on the USER'S DISK. MON, NOMON and MAXFILES are also not supported by ProDOS.

The VERIFY command does not check for the integrity of a file on the disk; it only checks if that file exists. Also it is no longer possible to DELETE a text file if it has been OPENed.

For example:

```
10 D$ = CHR$(4)
20 PRINT D$ "OPEN FILE"
30 PRINT D$ "DELETE FILE"
40 PRINT D$ "OPEN FILE"
50 PRINT D$ "WRITE FILE"
```

will work nicely under DOS 3.3, but not under ProDOS. Simply insert: 25 PRINT D\$ "CLOSE FILE" to close the file before DELETEing it.

Control-D must precede all ProDOS commands in a PRINT statement, just like DOS 3.3. However, the concatenation of CHR\$(13) and CHR\$(4) to clear the DOS input buffer to ensure that a DOS command is issued (especially after a GET statement) does not work.

For example:

```
10 D$ = CHR$(13) + CHR$(4)
20 PRINT D$ "BLOAD
PROGRAM"
```

will work under DOS 3.3 but will not work under ProDOS. Use instead:

```
10 D$ = CHR$(4)
20 PRINT: PRINT D$ "BLOAD
PROGRAM"
```

Since ProDOS requires 64K of RAM, Integer BASIC cannot be loaded into the language card and cannot be supported at all.

All filenames must be only 15 characters long. Characters may be any combination of uppercase letters, digits and periods; spaces, punctuation marks and lowercase letters are not allowed.

Other than these major deletions, all of the DOS 3.3 commands are still present, including "BLOAD" and BSAVE", which have retained their original usage. The binary file start address and length cannot be found at locations \$AA72 and \$AA60 respectively anymore. The directory "ENDFILE" and "SUBTYPE" tell you this.

## The .SYS File

The ".SYS" (system) file type is similar to CP/M's ".COM" files. They are machine language programs executed by typing a hyphen followed by the name. "Load" or "RUN" commands are not necessary. To execute the FILER, simply type "-FILER".

## An Annoyance Killed

A major annoyance that I am glad to see cured is the execution of the "PR#" and "IN#" commands used to reroute output or input to printers, modems and 80-column cards via the slots. In DOS 3.3, if you type "PR#4" and there is no I/O peripheral card in slot number 4, you would probably lose control over the computer. If you are lucky, you may break into the monitor safely, but sometimes the program flow goes on a rampage, murdering your program and DOS itself. Normally, you have to restart the machine from the very beginning by turning the machine off and on again, certainly losing all its memory contents. ProDOS changes the output or input vector to the slot, it actually checks to see if a peripheral card with ROM memory is present. If it isn't, a "DEVICE NOT PRESENT" error results. This new error message also prints out if you try to access a non-existent disk drive in another slot.

## Is DOS 3.3 Dead?

Does ProDOS obsolete DOS 3.3? Probably with time it will, just as DOS 3.3 replaced DOS 3.2. However, I still relish the simplicity of DOS 3.3 and it's adequate for my application programs. I hate to see Integer BASIC die away along with it. DOS 3.3 took a big step from DOS 3.2 in increasing the disk memory storage from 124K to 143K by increasing the sectors per track from 13 to 16. ProDOS took no step in increasing memory storage; the disk itself still uses only 35 tracks with 16 sectors per track (in keeping with older disk drives). It should be simple to fit ProDOS for use with 40 tracks in the same way as DOS 3.3. (from my article in TechTips, E.T.I. May 1984).

Nevertheless, I am generally impressed with Apple's new disk operating system, and hope to soon harness the full potential of it. **ETI**

## DOSDIAL

### The Apple Terminal Package

There are plenty of terminal programs for the Apple II and its emulators. Some dial, some download, some even nurse your poor motherless wombats when they're lonely and scared at two in the morning. However, only DOSDIAL is this splendidly cheap.

DOSDIAL is a hybrid Applesoft and machine code package for fast operation and easy modification. It features a phone number library and automatic dialing. It operates on any fruit with a PDA 232C serial card and an autodial modem. A complete source file of the assembler code is included to allow it to be quickly patched for other serial cards.

Only

**\$16.95**

Ontario residents add seven percent  
Computing Now! Software  
25 Overlea Boulevard, Suite 601  
Toronto, Ontario  
M4H 1B1





# VMOS CIRCUITS

Explore the possibilities of VMOS transistors; they're close to being a voltage-controlled resistor.


by R.A. Penfold

THERE ARE three basic types of power FETs; the VMOS type, power MOSFETs, and V-JFETs. This article will primarily be concerned with VMOS power FETs because these are readily available at reasonably low prices. Low, medium and high power devices can be obtained, and although only N channel devices were originally produced, P channel devices are now produced commercially as well. Power MOSFETs are available to the amateur user, although they are relatively expensive. These are primarily designed for use in audio amplifiers (but are also suitable for a variety of other applica-

tions), and will be dealt with in the examples of audio circuits. Like power MOSFETs, V-JFETs are mainly intended for use in high quality high power audio amplifiers. However, they are depletion mode devices, whereas VMOS and power MOSFETs are enhancement mode devices. In other words, a V-JFET is switched full on when it has a gate to source voltage of zero, and is switched off by reverse biasing its gate (as in the case of an ordinary JFET). VMOS and power MOSFETs are switched off if the gate to source voltage is made zero, and are switched on by applying a forward bias to the gate. In

this respect they are like ordinary bipolar transistors, or the MOSFETs fabricated in CMOS IC's. V-JFETs are more difficult to use than the other two types of power FET, and would not seem to be available to amateur users. Therefore, they will not be considered further here.

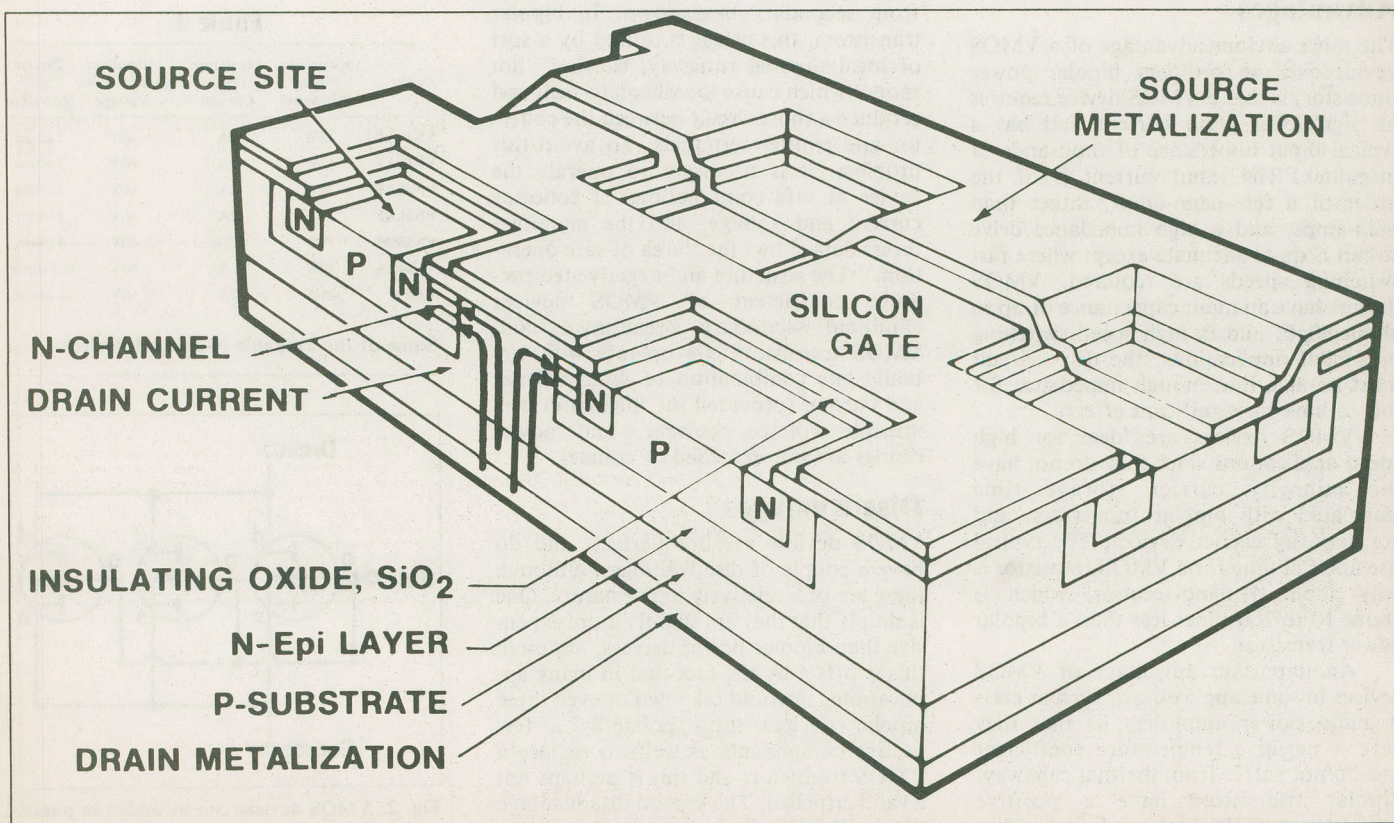An ordinary field effect transistor has an "on" resistance that is usually in the range of 100 to 500 ohms, and so producing a useable power FET is not just a matter of producing a device that is capable of dissipating high power without being destroyed; it is also necessary to obtain a much lower "on" resistance. The struc-



The construction of a FET chip, courtesy of Motorola.



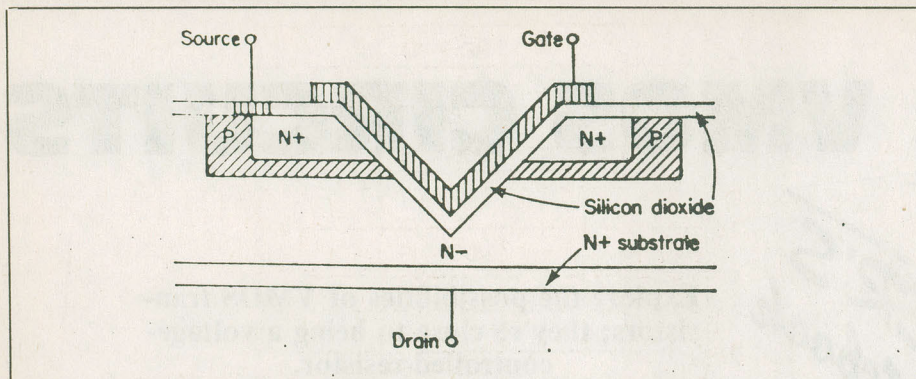


Fig. 1. A cross-section illustrating the construction of a VMOS device.

ture of a VMOS FET is therefore substantially different to that of an ordinary MOSFET, and Fig. 1 shows a cross-section that illustrates the internal structure of a VMOS device. With an ordinary MOSFET (or JFET) the current flows horizontally between the drain and source terminals, but the structure of a VMOS device is such that this current flow is vertical, and a low "on" resistance is obtained. Another necessary characteristic of VMOS devices is that they have a far higher gain than conventional FETs, so that a gate signal of a few volts peak to peak is sufficient to produce a change in drain current of perhaps an ampere or more.

## Advantages

The most obvious advantage of a VMOS device over an ordinary bipolar power transistor, is that a VMOS device requires no significant input current and has a typical input impedance of thousands of megohms. The input current is of the order of a few nano-amps, rather than milli-amps, and a high impedance drive circuit is quite adequate except where fast switching speeds are required. VMOS devices have an input capacitance of up to about 50pF, and in high speed switching or similar applications, the drive circuit must be at a low enough impedance for this to have no significant effect.

VMOS devices are ideal for high speed applications since they do not have the minority carrier storage time associated with bipolar transistors, and are majority carrier devices. The typical rise and fall time for a VMOS transistor is only about 4 nano-seconds, which is about 10 to 100 times less than a bipolar power transistor.

An important advantage of VMOS devices in some applications, such as class B audio power amplifiers, is that they have a negative temperature coefficient and do not suffer from thermal runaway. Bipolar transistors have a positive temperature coefficient, and thus when they heat up in use they tend to conduct

more heavily. This can produce increased current flow and dissipation in the device, which causes further heating and a further increase in current flow. This process can continue until the device becomes overheated and is destroyed. Since VMOS transistors have a negative temperature coefficient, internal heat makes them conduct less heavily, giving slightly reduced current flow and no possibility of thermal runaway. This is not to say that a VMOS device cannot be destroyed by overheating since the reduction in current flow, due to heating, is not very large and is not sufficient to make it impossible to over-power the device.

A further important advantage of VMOS devices is that they do not suffer from secondary breakdown. In bipolar transistors, this effect is caused by a sort of local thermal runaway, causing "hot spots" which cause the silicon to melt and produce a short circuit between the collector and emitter terminals. To avoid this problem, it is necessary to operate the device at safe combinations of collector current and voltage, and the manufacturers data shows the "area of safe operation." The structure and negative temperature coefficient of VMOS devices eliminate secondary breakdown, and VMOS transistors can operate with virtually any combination of drain voltage and current (provided the maximum permissible voltage, current, and power ratings are not exceeded of course).

## Disadvantages

VMOS devices are not perfect, and do have a couple of disadvantages, although these are of a relatively minor nature. One is simply that they are slightly more expensive than bipolar power devices, although this is offset by the fact that in many applications, it would take two or even three bipolar devices (plus possibly a few passive components as well) to replace a VMOS transistor, and this is perhaps not a valid criticism. The second disadvantage is that most of the current devices have a comparatively high "on" resistance. This

means that the voltage developed across a VMOS device when switched full on and passing a high current, is likely to be somewhat more than would be the case for a bipolar device operating under similar conditions. This can result in reduced efficiency in some applications. However, devices having "on" resistance of only about 0.2 or 0.3 ohms are now produced, and two or more devices can be connected in parallel, as shown in Fig. 2, to give reduced "on" resistance. Although this simple parallel method of connection does not work well with bipolar transistors, where the positive temperature coefficient can result in one device passing a steadily increasing percentage of the total current flow, until it eventually overheats and is destroyed, this does not occur with VMOS transistors due to their negative temperature coefficient. In fact, the circuit tends to be self stabilizing with the two devices taking a virtually identical share of the current flow. Of course, the transistors used should all be of the same type, or should have similar characteristics, or a greatly unequal current could flow through them and the stabilizing action might be inadequate to properly compensate for this. The "on" resistance is equal to the "on" resistance of a single device divided by the number of devices used.

Table 1

Device	Maximum Power Dissipated	Maximum Drain Current	Maximum Drain-Source Voltage	Typical "on" Resistance
VN46AF	15W	2A	40V	2 ohms
VN66AF	15W	2A	60V	2 ohms
VN67AF	15W	2A	60V	2 ohms
VN88AF	15W	2A	80V	3 ohms
VN10KM	1W	0.5A	60V	4 ohms
VN64GA	80W	12.5A	60V	0.3 ohms
VMP4	25W	2A	60V	2 ohms

Some of the available N-channel devices.

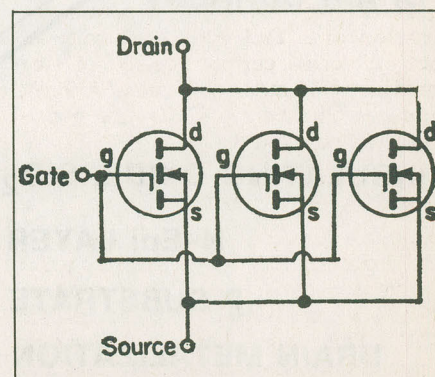


Fig. 2. VMOS devices can be added in parallel to reduce "on" resistance.



## Output Characteristic

Although it is normal to refer to the "on resistance" of a VMOS transistor, it should perhaps be pointed out that it is not a true resistance that is provided between the drain and source terminals of the device. Up to a point there is virtually a linear relationship between applied voltage and the current flowing through the device, and the device does provide what for all practical purposes can be regarded as true resistance. However, above a certain threshold level, increased drain to source voltage has little effect on the current passed by the device. The greater the gate bias supplied to the transistor, the greater the threshold current. This effect is shown in Figure 3, which shows the output characteristic of a typical VMOS device. This is similar to the output characteristic of normal FETs, but the currents involved are, of course, very much higher.

When designing circuits using VMOS transistors, it should be born in mind that the gate voltage versus drain current, characteristic of a VMOS device, is very different to the base voltage versus collector current, characteristic of a bipolar transistor. Simply changing a bipolar transistor (or Darlington Pair) for a VMOS device may not necessarily give good results, and could, in certain circumstances, fail to work at all. A bipolar transistor does not start to conduct significantly until the base to emitter voltage equals about 0.5 volts or so (for a normal silicon device anyway), and an increase of only about 200 mV or so is needed in order to bias bipolars into saturation.

## 10 Watt Amplifier

Figure 4 shows the schematic of a good quality 10 watt RMS amplifier using a quasi-complementary, class B VMOS output. The source follower TR3 drives the output on positive-going cycles, and bootstrapping via D1 and C6 improves the output swing. IC1 has 100% negative feedback over TR4, and produces the complement of TR3. R9 is adjusted to set the quiescent current drain of the amplifier to 30 mA. An input of 450 mV produces full power at the output with a distortion of about 0.1%.

## Class A Amplifier

Figure 5's circuit produces 7 watts RMS into 8 ohms. TR3/TR5 form a constant current source which sets a current of about 1.3 amps through output transistor TR4. This high quiescent current eliminates crossover distortion. TR4 and TR5 should have generous heatsinks, since the transistors dissipate full power at all times.

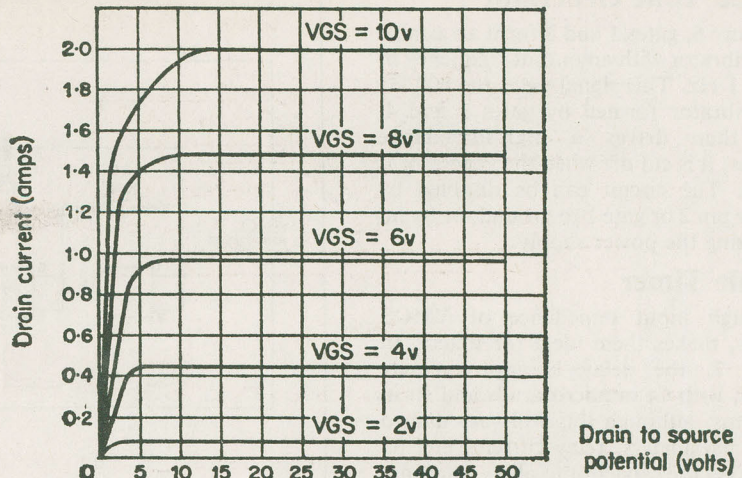


Fig. 3. Typical output characteristic of a VMOS transistor.

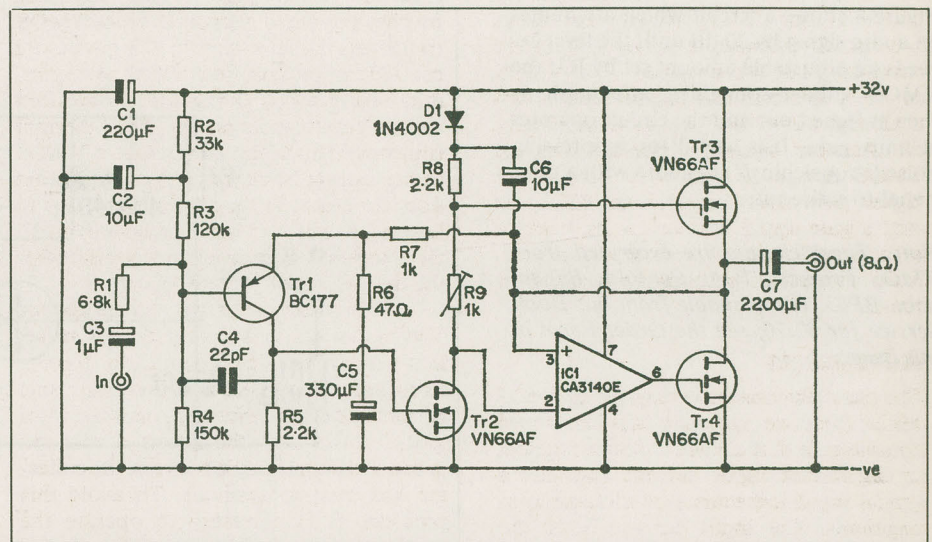


Fig. 4. A quasi-complementary VMOS amplifier giving 7 watts RMS.

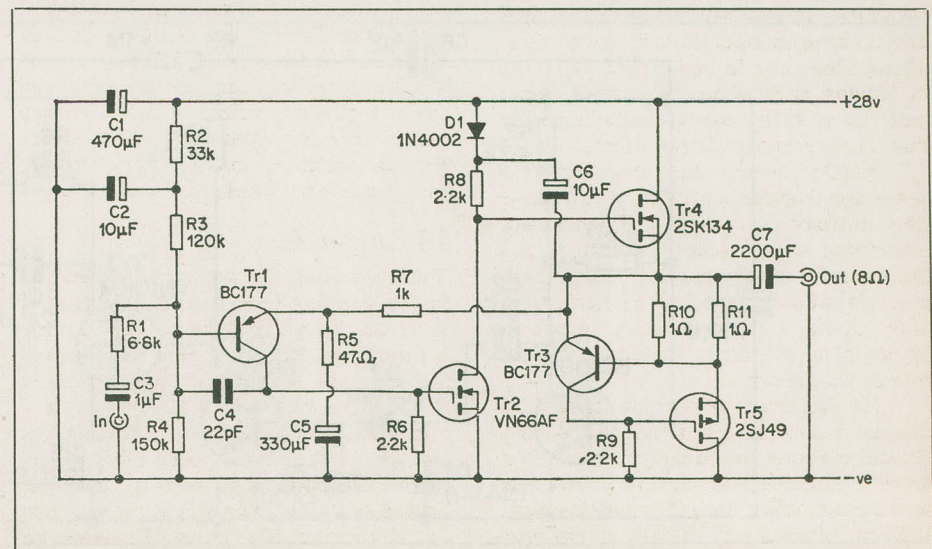


Fig. 5. The circuit diagram of a 7 watt RMS class A amplifier.



## Designer's Notebook

### Pulsed Tone Generator

In Figure 6, gates 1 and 2 form an astable multivibrator with an output frequency of about 1 Hz. This signal gates the 800 Hz multivibrator formed by gates 3 and 4. TR1 then drives a high-impedance speaker; it is cut off when the generator is muted. The circuit can be disabled by pulling pin 2 or gate 1 to ground, or by interrupting the power supply.

### Simple Timer

The high input impedance of VMOS devices, makes them ideal for timers. In Figure 7, the delay is approximately  $.3R_tC_t$ , with  $C_t$  in microfarads and  $R_t$  in megohms, although this will vary due to device parameters, relay current, etc. S1 discharges the capacitor to allow resetting; R1 prevents arcing during discharge.

### Noise Gate

Figure 8 shows a circuit which attenuates an audio signal by 20 dB until the level exceeds an adjustable amount set by R3; the VMOS voltage-controlled attenuator is then switched out and the circuit operates at unity gain. It is useful for suppressing noise ("squelching") in audio with a poor signal-to-noise ratio.

*Note: These circuits are excerpted from VMOS Projects, R.A. Penfold, Babani book BP83. It's available from our Book Service for \$7.70; see the Order Form in this issue.*

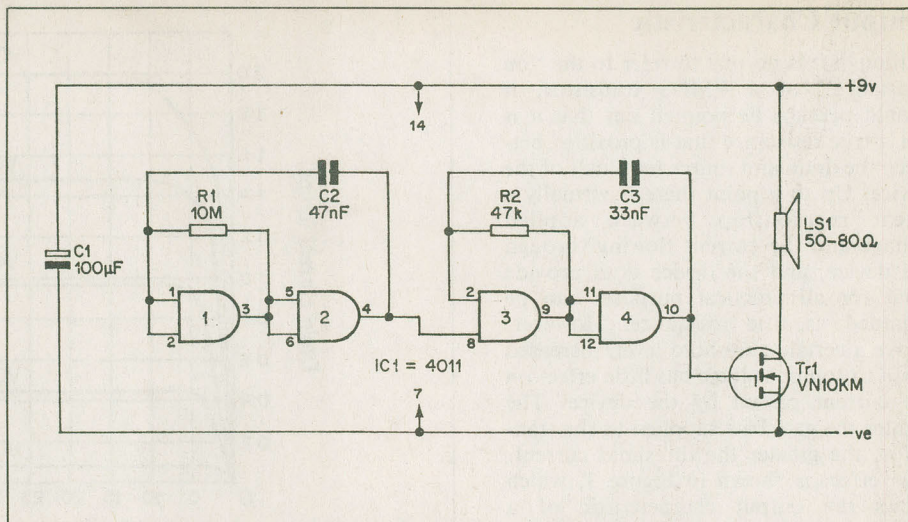


Fig. 6. The circuit diagram of a pulsed tone generator.

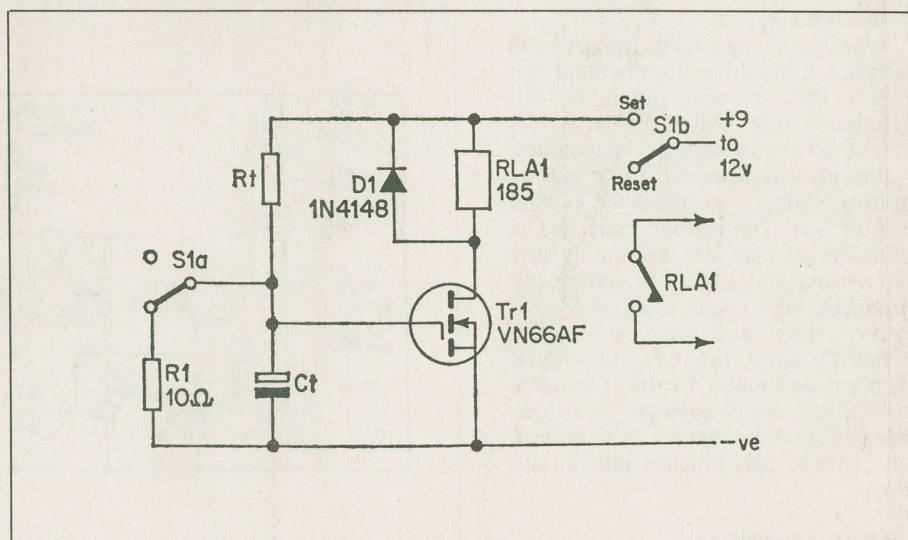


Fig. 7. An ultra-simple VMOS timer circuit.

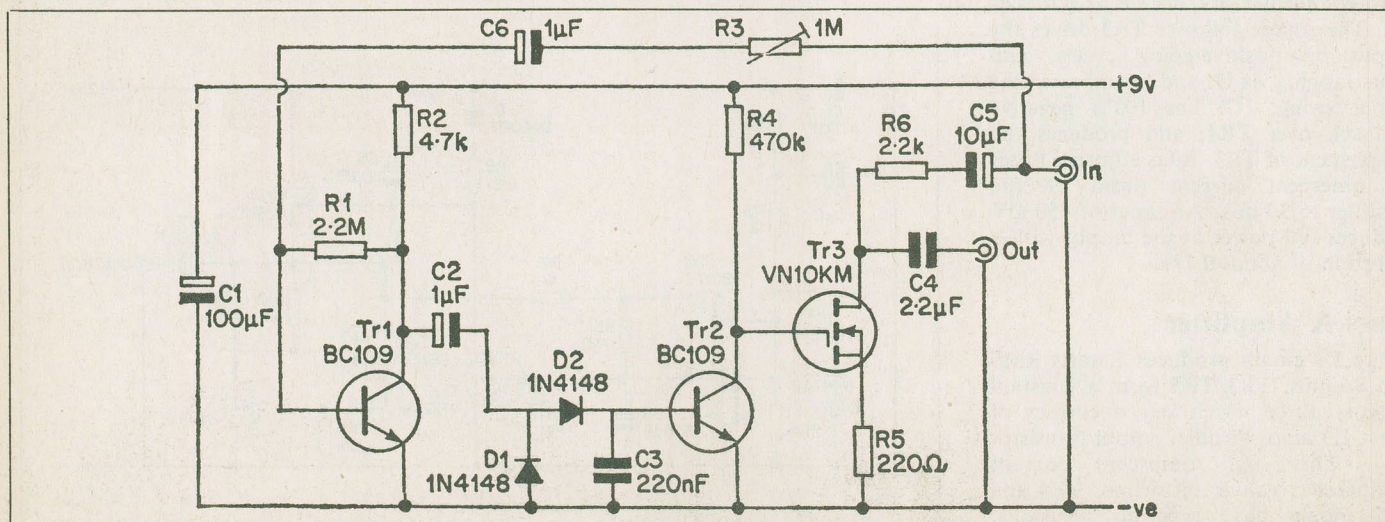


Fig. 8. The circuit diagram of the noise gate.

ETI



This Month in

# Computing Now!

Canada's Personal Computing Magazine

## Computer Survey

Another one? Will it never end? Not as long as manufacturers keep turning out the latest, greatest, death-defying plastic box with buttons on the front. Go from total bewilderment to organized confusion with our 160-plus computer survey.

## Down to the Ships in C

We stayed up nights working on that pun, and while it isn't Nobel quality, you must admit it isn't bad. A look into the C language, one of the more versatile compiler languages around. C for yourself (sorry!).

## Godzilla Meets All the BBS Numbers in the World

Bulletin Board System numbers aren't all that easy to find; you won't get much help from Ma Bell, whose information service looks askance at these things. Get a modem and the latest CN! and stay up all night doodling the lines.

## Computer Museum

They want to build a computer museum in Toronto? They can't be serious. They are? Maybe it makes sense. Computers become ancient history as soon as the latest model is released. Take a look at an ambitious project: a shrine to hi-tech.

## Graphics Toolkit Review

We did okay fitting the PC board and running the software, but we couldn't figure out what to do with the socket wrenches and the radial arm saw. Mind you, after we got the Apple to display all sorts of graphics with 640 by 384 pixel resolution, we were impressed.



On  
Newstand  
Across  
Canada  
Now


# K.E.M. COMPUTER AND ELECTRONICS

## ELECTRONICS PARTS

<b>MEMORIES</b>		
ROM	2716	\$8.25
	2732	8.25
	2764 250nS	13.50
	27128	35.50
RAM	6116P 150nS	10.45
	4116 200nS	2.95
	4164 150nS	9.25
<b>CPUs</b>		
	6802	6.29
	6809E	17.95
	68000 8MHz	74.98
	8085A	11.55
	8086	37.98
	8088	32.00
	Z80A 4MHz	5.95
Peripherals, CMOS, TTL		Available
<b>MAGNETIC SENSOR</b>		\$3.75
<b>INFRA-RED SENSOR</b>		7.50
<b>ULTRA SONIC TRANSDUCER</b>		
TX or RX		4.80
<b>OPTICAL FIBER DATA LINK</b>		
1 meter Cable with TX & RX		19.50
<b>STEPPING MOTORS</b>		
Several Types		Available
Stepping Motor Control IC		16.50


## EQUIPMENT FOR PCB PRODUCTION

<b>ETCHING AGITATOR TANK with</b>	
Air Pump & Thermometer	\$34.50
<b>HEATER for ETCHING TANK</b>	
	29.95
<b>MINI HANDY DRILL</b>	
Drill Stand	23.50
AC Adaptor	20.25

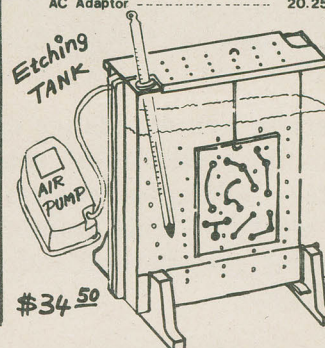
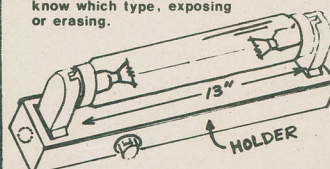
## UV LAMP WITH HOLDER --- \$26.98

FOR Photosensitive PCB Exposing  
or UV-EPROM Erasing.  
When you order, please let us  
know which type, exposing  
or erasing.



## PCB HANDICRAFT KIT --- \$14.95

Positive Photo-sensitive Printed  
Circuit Board Handicraft Kit  
All necessary materials, PCB,  
Etchant, Developer, etc. 11 items

## ELECTRONICS KITS

KEM Original Series (See Last ETI Issue)  
Full documents including circuit diagram  
for every item --- \$4.00  
(incl. postage)

Plus \$3.00 each item for postage &  
handling charge. Plus provincial sales tax.  
C.O.D. mail order accepted.

## KAIENTAI ELECTRONICS MERCHANTS LTD

2111 KINGSWAY, VANCOUVER, B.C. V5N 2T4

MAIL TO: P.O. BOX 69126 STATION 'K'  
VANCOUVER, B.C., CANADA V5K4W4

PHONE: (604) 435-9697

Circle No. 30 on Reader Service Card



Retail Stock  
Reduction

## B.T.W. Electronic Parts

**MICRO INSTRUCTIONAL:** Complete audio cassette  
training for microcomputers and related software.

**50% OFF SUGGESTED RETAIL**

**MODE ELECTRONICS:** Plugs, jacks, adaptors, switches  
and more small parts.

**50% OFF SUGGESTED RETAIL**

**EDUKIT EDUCATIONAL:** Strobe Light Kit, Colour  
Organ, Digital Designer, etc.

**25% OFF SUGGESTED RETAIL**

**SAMS BOOKS:** Large selection of books in stock.

**30% OFF SUGGESTED RETAIL**

**INTEGRATED PLASTICS:** Drawers and boxes of  
various sizes.

**35% OFF SUGGESTED RETAIL**

**ETI & COMPUTING NOW! MAGAZINES**

**35% OFF SUGGESTED RETAIL**

**OK TOOL:** Wire wrap tools and accessories.

**25% OFF SUGGESTED RETAIL**

**GLOBAL SPECIALTIES:** Breadboards and accessories.

**25% OFF SUGGESTED RETAIL**

1542 WARDEN AVENUE - SCARBOROUGH, ONTARIO M1R 2S8 - (416) 441-1733

Circle No. 19 on Reader Service Card



# Machine Code Programming Part 4

Every month we plunge deeper into the mysteries of machine code — taking our readers with us, we hope. This month, Bob Bennett goes beyond the index registers.

LAST MONTH I gave examples of instruction of the form **Ld (pq),A** etc., and showed how two bytes are pushed back onto the stack. I also left you with the question of what happens if you push HL and pop DE. The answer is that both HL and DE now hold the data that was in HL originally.

One last thing, for the moment, regarding the stack: when you have finished with your machine code program and wish to return to BASIC, for example, then you must make sure that everything that you pushed onto the stack has been popped off. This is because when you GOSUB, and call to USR (machine code) program is a GOSUB, then the return address is pushed onto the stack. When the time to return comes along, then the address is popped off the stack, but if you have left some pushes un-popped, so to speak, then some very funny things can happen.

Whether you use pq to represent an address, or mn a number, doesn't matter as long as you the programmer know what is happening. However, what is significant is the presence or absence of brackets in the instruction, as I mentioned last month. Fig. 11 shows part of a program with a Z80 instruction to load HL with

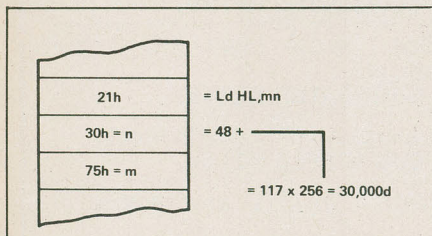


Fig. 11. Z80 instruction to load HL with 30 000 decimal.

30,000d or 7530h. Note how the low byte, the one in L, goes straight after the instruction. Some of you will be familiar with the BASIC instruction, **PRINT PEEK (address) + 256 x PEEK (address + 1)**; now you can match up the request

with Fig. 11. The difference between the two instructions **2A — Ld HL, (pq)** and **21 — Ld HL,mn** should now be apparent. The first instruction loads the contents of the address pq into L, and the contents of pq + 1 into H; the second instruction loads the byte n into L and the byte m into H. If the two bytes mn represent an address, then HL is said to be pointing to that address.

## Taking The Indirect Route

The Z80 instruction **77 — Ld(HL),A** is an example of indirect addressing, which if you work it out, means load the contents of the A register into the address which is pointed to by the HL pair. This is the machine code equivalent of the BASIC instruction **POKE (address), with whatever.**

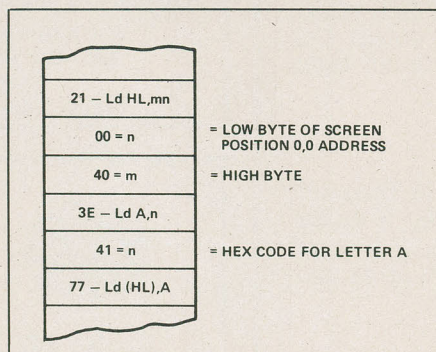


Fig. 12. One way of printing a screen position 0,0.

Earlier I explained that the display file is a series of addresses, with each address holding a byte of information relating to the screen display. I also gave the address 16384d - 400Ch as being the address of screen position 0,0 for no particular computer. Fig. 12 shows how to poke the code for the letter A onto the screen at position 0,0 using one method, and Fig. 13 shows a different method. However, an explanation is required for the method used in Fig. 13.

Suppose that you didn't know the address of the position 0,0 on the screen, but the system variable called D File held the address. If the address of D File was 19634d - 400Ch, this would mean that 400Ch would hold the low byte of the address of position 0,0 and 400Dh would hold the high byte.

One last example in this section is the Z80 instruction **7E — Ld A,(HL)**, which is the machine code equivalent of the

BASIC instruction **PEEK (address)**. Of course, registers other than A and HL can be used, but you should by now be able to identify the other instructions. Just in case you are wondering about the term indirect addressing, the instruction **77 — LD (HL),A** pokes the contents of register A into the address via the HL pair. What I haven't mentioned yet is the use of such instructions in a program, so here is a short explanation using the two instructions given above.

Suppose instead of poking the letter A onto the screen, we had poked the code for 1 (this could be the start of a score, or the first try at something or other). Later on in the program we will want to test for the limit, say 9, and if we have reached it, then finish, otherwise increase (increment) the score and carry on. The instruction **7E — LD A,(HL)**, where HL points at the screen position of the number, will load A with the number on the screen. Comparing register A with the limit, 9, we can either finish if A equals 9, or increment A, poke it back onto the screen, and carry on with the program. I'll be covering the compare instructions later on, but it does involve the use of the flags. Things should be starting to fall into place now, but it does require a little thought.

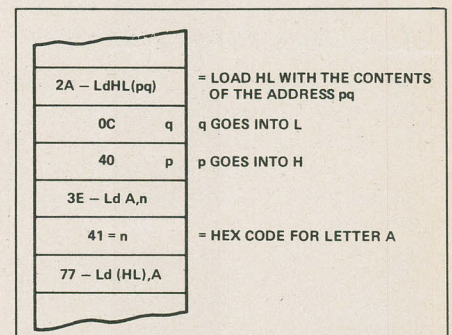


Fig. 13. Another way of printing a screen position 0,0.

## Fingering The Index

Because the index registers, X and Y, allow great flexibility in machine code programming, this section will cover a lot of ground. As you get to know how the index registers work, the easiest way to visualize them is as pointers to a table — the X registers moving horizontally, and the Y registers moving vertically. This doesn't happen literally of course, but the table concept can easily be programmed.



# = COMPUTER MAIL ORDER =

= CANADA =

**ONTARIO/QUEBEC**  
**1-800-268-3974**

**TORONTO**  
**828-0866**

**OTHER PROVINCES**  
**1-800-268-4559**

We Carry a Wide Selection of Software From:  
Artworx, Broderbund, Commercial Data, Creative Software, Epyx, Atarisoft, Hes, Sirius,  
Microspec, Synapse, Thorn, Spinnaker, Timeworks + Many More. Call us for prices!

(All equipment under full warranty in Canada.)  
Price subject to change without notice.  
(All orders Shipped within 48 hrs, upon payment.)

## COMPUTERS

APPLE .....	CALL
COLUMBIA .....	CALL
COMPAQ .....	CALL
EAGLE .....	CALL
FRANKLIN .....	CALL
HEWLETT PACKARD .....	CALL
IBM .....	CALL
SANYO .....	CALL

## HAND HELD

HEWLETT PACKARD	
HP11C .....	119.00
HP12C .....	160.00
HP15C .....	160.00
HP16C .....	160.00
41CV .....	339.00
41CX .....	399.00

## DISK DRIVES

INDUS	
GT ATARI Drive .....	549.00
MSD	
MSD-1 C64 Drive .....	519.00
MSD-2 C64 Drive .....	855.00
PERCOM .....	CALL
RANA	
1000 (Atari) .....	479.00
Elite 1 .....	389.00
Elite 2 .....	579.00
Elite 3 .....	799.00
TARGA .....	CALL
TALLGRASS .....	CALL
TANDON	
TM-100-2 DS/DD .....	339.00
TM-50-2 DS/DD .....	349.00
TRAK	
ATD-2 .....	565.00

## MODEMS

ANCHOR	
Mark II (Atari) .....	129.00
Mark VI (IBM) .....	279.00
Mark VII (AA/AD) .....	193.00
Mark XII (1200 Bd.) .....	489.00

## HAYES

Smartmodem 300 .....	356.00
Smartmodem 1200 .....	799.00
Smartmodem 1200B .....	749.00
Micromodem II e .....	439.00

## NOVATION

J-Cat .....	163.00
Smartcat 103 .....	289.00
Smartcat 103/212 .....	649.00
Autocat .....	356.00
212 Apple Cat .....	929.00
PC-Cat .....	549.00

## MONITORS

AMDEK	
Video 300 .....	\$229.00
Video 300 A .....	239.00
Video 310A IBM .....	249.00
Colour 1+ .....	429.00
Others .....	CALL
BMC	
12" Green .....	125.00
12" Amber .....	135.00
GORILLA	
12" Green .....	139.00
12" Amber .....	149.00
NEC .....	CALL
PANASONIC .....	CALL
PRINCETON GRAPHICS	
HX-12 .....	749.00
QUADRAM	
Quadcolor RGB .....	809.00
SAKATA .....	CALL
TAXAN .....	CALL
USI .....	CALL
ZENITH	
Amber .....	159.00
Green .....	149.00
Colour .....	699.00

## CARDS

AST RESEARCH .....	CALL
QUADRAM .....	CALL
HERCULES	
Graphic card .....	598.00
PLANTRONICS	
Colorplus .....	699.00

## ACCESSORIES

KEYTRONIC	
KEYBOARDS .....	CALL
KOALA PAD	
All Computers .....	CALL

## INTERFACES

Batteries Included	
Bus Card .....	CALL
80 Col. Card .....	CALL
CARDCO	
Int/Graphics .....	119.00
TYMAC	
C64 to EPSON OKI .....	148.00
MPC	
Apple Dumping GX. ....	CALL
PKASO	
Universal Card .....	225.00


## Dealer Enquiries Invited

Write or telephone for our FREE catalog

To order: Send money order, certified cheque, personal cheques must clear  
our bank, VISA or MASTERCARD. (Include card # and expiry date &  
signature) Add 5% for shipping and handling. Minimum \$5.00 per order.

Ontario residents add 7% P.S.T.

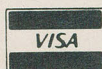Computer Mail Order Canada 2505 Dunwin Drive, Unit 3 • Mississauga, Ontario L5L 1T1



## PRINTERS

BMC	
401 Letter Quality .....	\$923.00
BX-80 Dot Matrix .....	399.00
C. ITOH	
Gorilla Banana .....	299.00
Prowriter 8510P .....	550.00
Prowriter 1550P .....	899.00
F10-40 .....	1529.00
F10-55 .....	1999.00
DAISYWRITER	
2000 .....	1499.00
COMUWRITER	
CW2. .LQ 12CPS .....	749.00
EPSON	
RX80 .....	449.00
RX80FT .....	525.00
FX80 .....	749.00
FX100 .....	1049.00
JUKI	
6100 .....	769.00
OKIDATA	
82 .....	499.00
83 .....	875.00
84 Par .....	1425.00
84 Ser .....	1595.00
92 .....	675.00
93 .....	1059.00
MANNESMANN TALLY	
Spirit 80 .....	469.00
160L .....	895.00
180L .....	1229.00
SMITH CORONA	
L1000 .....	589.00
STAR	
Gemini 10X .....	399.00
Gemini 15X .....	CALL
BROTHER	
HR 15 .....	689.00
TTX .....	CALL
DISKETTES	
BASF	
BA1D SS/DD W/Case .....	28.99
BA2D DS/DD W/Case .....	35.99
ELEPHANT	
EL1 SS/DD .....	27.99
EL2 SS/DD .....	29.99
EL3 DS/DD .....	39.99
MAXELL	
MXD1 SS/DD .....	37.99
MXD2 DS/DD .....	54.99
NASHUA	
ND1D SS/DD W/Case .....	26.99
ND2D DS/DD W/Case .....	38.99
VERBATIM	
VE1 SS/DD .....	31.99
VE2 DS/DD .....	43.99
VE1C SS/DD W/Case .....	34.99
VE2C DS/DD W/Case .....	46.99



## Machine Code Programming

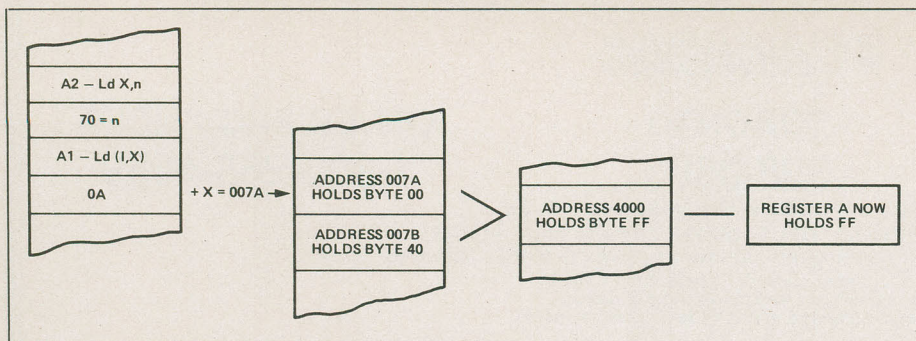


Fig. 14. Pre-indexing addressing from the 6502 set.

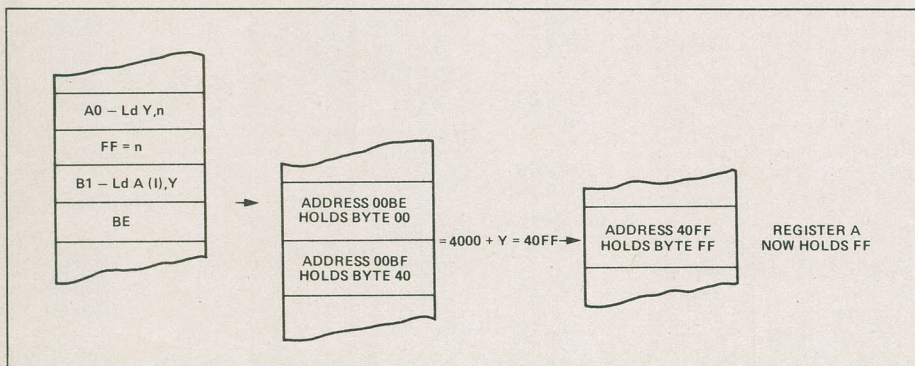


Fig. 15. Post-indexing indirect addressing from the 6502 set.

Because I wrote about indirect addressing in the last section, I'll give a couple of examples from the 6502 set using indirect and indexed addressing together. Pre-indexed indirect addressing is the grand title of the first example, and Fig. 14 will make what's happening clearer.

The instruction **A1 — Ld A,(I,X)**, requires a second byte after the op-code (A1). This second byte is added to the contents of the X register to get the address of the first of two sequential bytes in zero page of the memory. These two bytes form the address of the byte to be loaded into the accumulator (or A register). In the example, I've assumed that the X register holds 70h and that the second byte of the instruction is 0Ah. These two are then added together to get 7Ah (any carry bits will be lot), which is used as a pointer to locations 007Ah and 007Bh in the memory. The contents of these two locations are treated as a 16-bit address (low byte in the lower address) and in our example, this is 4000h. This is the address which holds the byte to be loaded into the accumulator, in this case FFh, to finish the instruction. Note that the X register still contains 70h at the end of the instruction. A most useful mnemonic would be **A — (byte 2 + (X))**, which illustrates quite clearly what is happening. Although I mentioned zero page addressing above, you could have reasoned out what was go-

ing on without it, because the X register will only hold one byte.

The second example from the 6502 set is **B1 — Ld A(I),Y** which is a post-indexed indirect instruction, with the mnemonic **A — A ((Y) + (byte 2))**. Before you look at Fig. 15, and before you read my explanation, see if you can work out what it does; think of the use of brackets.

The second byte, in this case BE, is address 00BE, and 00BE and 00BF hold the two bytes of an address, in this case 4000h. The byte in the Y register, which is FFh, is now added to 4000h to make 40FFh, and in address 40FFh is the data that is loaded into the A register. What could be simpler?

Please note that only certain index registers can do particular jobs in the 6502 set. I leave it as an exercise for you to work out how the two prefixes pre- and post- are justified.

The Z80 CPU has a host of instructions involving index register IX and IY. The instructions for the IX and IY pairs are the same as those for the HL pair with the prefix DD for IX and FD for IY instructions. As an example, I'll take the Z80 op-code 77 — **LD(HL),A**, which I used in the previous section. The instruction **DD77 — LD (IX + d),A** is the indexed equivalent. This is quite straightforward; it means: poke the contents of A into the

address formed by adding d to IX. That letter "d" means that there are three bytes in the instruction and "d", for displacement, is the third byte. This byte is treated as an 8-bit signed 2's complement number and thus has a value between -128d and +127d. (80h = -128d; 00h = 0d; and 7Fh = +127d). If IX held 4000h and we wanted to load the A register into address 4079h, and the full instruction would be: **DD 77 79**.

By now you should be able to recognize just about every addressing mode that you may come across. Before I carry on though, I would like to just clear up something I touched upon at the beginning of this month's article, when I was discussing pushing and popping.

Apart from the fact that we can't use line numbers in machine code, we do have the equivalent to GOSUB instructions where we GOSUB to an address (location). The 6502 instruction set has only the one instruction to GOSUB and that is 20 — **JSR**, where JSR means jump to subroutine. Now don't confuse this jump with the relative jumps and the like, that I wrote about earlier. Just as in BASIC, this jump to a subroutine expects a RETURN, which with the 6502 is 60 — **RTS** or return to subroutine.

The Z80 set has quite a few GOSUB instructions, although they are labelled **CALL**, with the simplest being **CDpq — CALL pq**. All of the flag conditions can be used for CALLs in the Z80 set; for example, **CCpq — CALL Zpq**, which means, when the result of the last instruction is zero, GOSUB pq. Again flag conditions can be used for a return, such as **DB P RET C**, when carry flag is set. The straightforward return in the Z80 set is C9. A word of warning, though, keep track of your calls to subroutines, and make sure that the returns match up. If in doubt, re-read this month's opening section.

## A Logical Conclusion

A seemingly innocuous one-byte instruction is increment, or add one to. This can apply to single registers, pairs, index registers and even inc,(HL). The 6502 has single byte instructions for incrementing its X and Y registers only. Increment is one of three add instructions which involve the use of absolute binary arithmetic. All this means is that we will be using binary, but with no fractions and no negative or positive numbers. This will become clearer as we go along anyway.

Taking a single register first, as you would expect, increment will just add 1 to the contents of that register. This is all very well until the contents of that register reach FF, which is the maximum number that one register can hold. So now what happens? Figure 16 should be of some



help, and if you don't understand binary addition, then this explanation will put you right. Remember that a binary digit, or bit, can only be either 1 or 0, if we add two 1s together, the answer must be 0 and carry one over to the left. Starting at bit 0, the one on the right in Fig. 16, work your way to the leftmost bit which is bit 7.

Contents of register = FF = 11111111 binary  
1 INC or add 1  
Contents of register = 00 = 00000000

Fig. 16. Incrementing the contents of a full register.

You should finish up with all the bits at 0, which means that the register now holds zero. So you see, incrementing a full register, or register pair, simply means that we start at zero again, and the zero flag should be set. I say *should* be set, because it's always advisable to check on the flags situation in the instructions set.

By the way, what happened to the last carry to the left, the one after we added 1 to bit 7? The answer in the case of incrementing is that it was discarded, but with the next two add operations, it is important as it affects the carry flag. The 6502 also has 2- and 3-byte instructions for incrementing (and decrementing) memory locations directly and indirectly.

In the Z80 set, you can add register to register, such as **ADD A,B**, or add pairs such as **ADD HL,DE**. Again, index registers can be involved, and even an instruction such as **ADD A,(HL)**. Usually the only register that you can add a constant to is register A, in instructions such as **ADD A,n**. Figure 17 shows the simple addition of two registers, which is quite straightforward. Again, when the two numbers added together come to more than one register can hold, then the register that is being added to will pass through zero. This time something different happens, so let's take a look at an example.

Contents of register A = 50 decimal = 00110010 binary  
Contents of register B = 100 decimal = 01100100 binary  
Contents of register C = 150 decimal = 10010110 binary

Fig. 17. Adding two full registers together.

Suppose register A held D1 or 209, and register B held B0 or 176, and the instruction was **ADD A,B**. Fig. 18 shows what happens, but I'll put it into words as well. Adding 209 and 176 gives an answer of 385; subtracting 256 leaves 129, which is what finishes up in register A.

Just to prove what a glutton for punishment I am, I will now go through the binary addition in Fig. 18. Bit 0, the rightmost bit, is where we start, and  $0 + 1$  equals 1, so a 1 goes on the bottom line. Bits 1, 2, and 3 are 0 in both registers, so 0 goes on the bottom line in each case. Bit 4

in both registers is 1, so down goes 0 and carry to the left. Two 1's make a carry from bits 5 and 6; this 1 goes into bit 7 position on the bottom line. These two 1's above the bottom line in bit 7 position, give a carry to the left, and this last carry sets the carry flag 7.

Contents of register A = 209 decimal = 11010001 binary  
Contents of register C = 176 decimal = 10110000  
A carry to the left sets the carry flag

Fig. 18. What happens when two registers add ed together come to more than 255 decimal.

The third add instruction is **ADC**, which stands for add with carry, and is really straightforward. What happens is that all the above rules apply, plus the fact that the current value of the carry flag is added on to the total, and the carry flag altered according to what happens during the current instruction. In other words, if there is a carry over from bit 7, then the carry flag will be set, otherwise reset. The 6502 has no register to register arithmetic, but uses memory locations — especially zero page locations — instead, but always with **ADC**.

The subtraction instructions follow exactly the same pattern as the addition instructions with regard to the registers, etc. The first **SUB**traction is **DEC**rement, or decrease by 1, then **SUB** and finally **SBC** or subtract with carry. As you might expect, if you decrement a register, or register pair, which holds zero, then the number will zoom round to FF or FFF. Rather than giving you an example of subtracting in binary, why not have a go yourself? Write down two decimal numbers, take the smaller from the greater, convert the two numbers to binary, underneath write down the answer from the decimal subtraction converted to binary. Now work out how you can arrive at the answer.

## AND The Rest

Usually there are three logical instructions that you can use which are: **AND**, **OR** and **XOR**. Taking **AND** as the first example, it usually comes in the form **AND,r** where r is another register such as **AND,C**. There should be an instruction such as **AND,n** where n is any number up to FF, and you may get **AND(HL)** and even **AND(IX + d)**. Your CPU instruction set should show what **AND** instructions you can use. Whatever the instruction, everything is **AND**ed with register A, the accumulator.

Register A holds FF = 11111111  
Register B holds 0F = 00001111  
Register A holds 0F = 00001111

Fig. 19. The result of the instruction **AND B**.

Assuming that register A holds FF and register B holds 0F, Fig. 19 shows what happens when the instruction **AND,B** is met. The explanation couldn't be easier: if the bits in A and B are both 1, then that bit remains the same in register A.

Check with your CPU instruction set, but an **AND** instruction will usually alter all of the flags, with the carry flag always being set. If, during the writing of your program, you are not sure of the status of the carry flag, then **AND A** or **AND FF** will always reset it for you. Another use for **AND**ing is to mask off certain bits, and this is worth an explanation.

In the first part of this series, I made a passing mention to a refresh register, which is used to ensure that data isn't lost from **FAM** by the simple expedient of each address from time to time. What happens is that this register, **R**, starts off at zero and is incremented until it reaches 7F, it is then discharged and starts at zero again. So at any time, register **R** will hold a number between 00 and 7F. The Z80 set has an instruction **ED 5F — LD A,R**, which, is used from time to time in a program, gives the effect of putting a random number in **A**. If you want to make sure that this 'random' number doesn't go above a certain number, all you have to do is **AND,x** where x is your limit; note, however, that if you chose an x that is not equal to  $2^n - 1$ , this operation will not return a truly random number (why?).

The refresh register is actually 8 bits, but only the 7 lower bits are incremented automatically. The 8th bit can be set or reset by using the **Ld R,A — ED 4F**, which transfers the contents of the **A** register to the refresh register. The refresh register will then be incremented from the value, but the **MSB** will stay in its current state.

ETI

## FACT:

The Arthritis Society has a wide array of information available on the control and treatment of arthritis. Contact the office nearest you for information.

THE ARTHRITIS SOCIETY



# CIRCUIT IDEAS


## Temperature Controlled Switch

This thermistor-based temperature switch can be set for one of two temperature ranges.

THIS simple temperature controlled switch allows the switching on and off of any electrical device when a preset temperature is reached in the range of -10 to 100 degrees C.

Thermistors are special forms of resistors manufactured from heavy metal oxides and designed to have strongly varying resistance versus temperature characteristics.

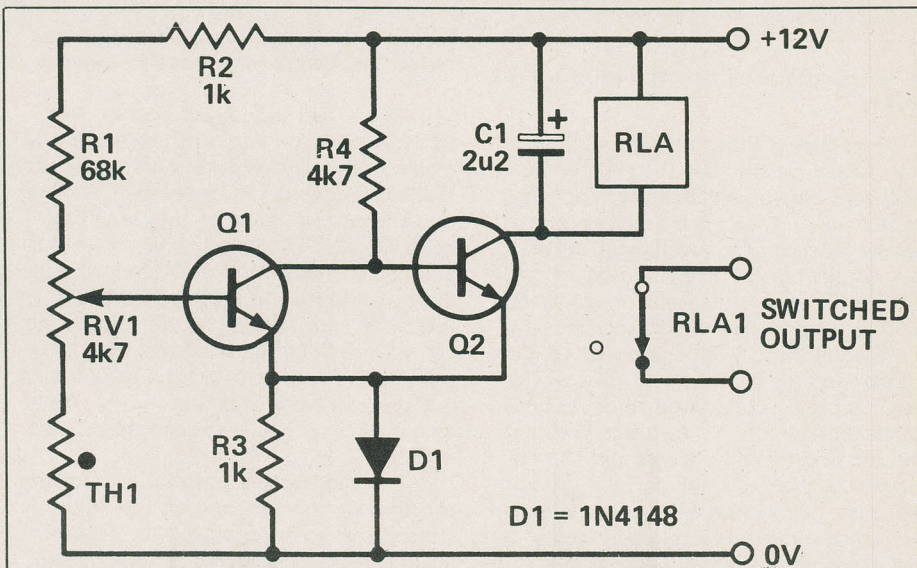It is possible to obtain thermistors whose resistance either increases (positive



temperature coefficient), or decreases (negative temperature coefficient) with rising temperature. For a typical negative temperature coefficient resistor, the change in resistance with temperature is between three and six per cent per degree Kelvin rise.

The thermistor should be a negative coefficient type with a resistance of 5K to 10K at the temperature of interest. The transistors are any small-signal type, such as 2N3904.


The preset, RV1 allows the operating temperature to be set, and is adjusted so that below the desired trip point, the voltage on the base of Q2 is sufficient to keep it switched on. As the thermistor heats up, the voltage on the base of Q1, which is derived from the potential divider chain of R1, R2, RV1 and TH1, will drop, eventually allowing Q1 to switch off. As soon as Q1 switches off, the voltage on the base of Q2 rises and the relay is switched on. The diode, D1, provides temperature compensation for the two transistors, and C1 acts as a back EMF absorber for the relay.

As shown, the range of the circuit will be for temperatures between 35 to 100 degrees centigrade. If R1 is replaced by a 10k resistor, then a range centred on zero degrees will result.

When the relay is inoperative, the consumption of the circuit is very small, in the order of 2 to 3mA; it may thus be powered from either batteries, or a small DC power unit.

ETI

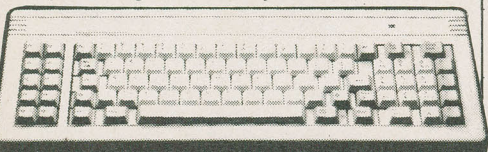**New capacitive keyboard for IBM™ and Apple II™**  
Unique Design Plus Many Built-In Functions



IBM is a Registered Trade Mark of International Business Machines Corp.

**TERMS:** Send cheque or money order (allow 2 weeks for personal cheque). Credit Cards welcome. No COD. Quebec residents add 9% sales tax. Add 5% for shipping and handling. Minimum order \$10.00, 20% restocking fee for returned merchandise. Prices and availability subject to change without notice. Do not send Cash.

**INFINITE CANADA INC.**

785 Plymouth Ave.,  
Suite 123, TMR. Que. H4P 1B3  
Tel: 514-342-6454

**Peripherals for IBM & Compatibles**

- Multifunction Card
- Modem Card
- 12 Bit AD/DA Converter
- Mother Board (No Bios)
- Hard Disk & Network Systems

Apple Peripherals Image processor

Auto Modem 300 Baud

**Special \$199.00**



**Copyright**

All material is subject to worldwide copyright protection. All PCB patterns are copyright and no company can sell boards to our design without our permission.

**Liability**

While every effort has been made to ensure that all constructional projects referred to in this magazine will operate as indicated efficiently and properly and that all necessary components are available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate efficiently or at all whether due to any fault in the design or otherwise and no responsibility is accepted for the failure to obtain component parts in respect of any such project. Further no responsibility is accepted in respect of any injury or damage caused by any fault in design of any such project as aforesaid.

**Editorial Queries**

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letter ETI Query. We cannot answer telephone queries.

**Binders**

Binders made especially for ETI are available for \$9.25 including postage and handling. Ontario residents please add provincial sales tax.

**Back Issues and Photocopies**

Previous issues of ETI Canada are available direct from our office for \$4.00 each; please specify by month, not by feature you require. See order card for issue available.

We can supply photocopies of any article published in ETI Canada; the charge is \$2.00 per article, regardless of length. Please specify both issue and article.

**Component Notation and Units**

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. ETI has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier: thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1 uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.6ohms is 5R6.

**PCB Suppliers**

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information on PCBs and kits. Similarly do not ask PCB suppliers for help with projects.

K.S.K. Associates, P.O. Box 266, Milton, Ont. L9T 4N9.

B—C—D Electronics, P.O. Box 6326, Stn. F, Hamilton, Ont. L9C 6L9.


Wentworth Electronics, R.R. No. 1 Waterdown, Ont. L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185, USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.

Beyer & Martin Electronic Ltd., 2 Jodi Ave., Unit C, Downsview, Ontario M3N 1H1.

Spectrum Electronics, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.

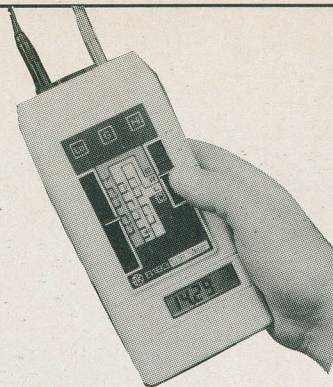**Digital LCR Meter**

The Avo B183 combines the measuring modes of inductance, capacitance and resistance, in one 9V battery operated hand-held instrument. Primarily suited to field service applications and the testing of discrete components, this small light-weight meter is ideal for the field service technician and quality assurance engineer, who wishes to quickly measure component values. There are six inductance ranges from 2mH to 200H; seven capacitance ranges from 200pF to 200uF; and seven resistance ranges from 20 ohms to 20M ohms. All readings, together with the decimal point, are clearly shown on a 3½ digit LCD. Measurements are made at a frequency of 1 kHz or 100 Hz depending on the range selected on the simple, positive action, eight-position slide switch. A similar four-position switch is used to select the function. For further details about the Avo B183 LCR meter, contact: Metermaster, division of R.H. Nichols Co. Ltd., 214 Dolomite Drive, Downsview, Ontario M3J 2P8.

Circle No. 42 on Reader Service Card.

A computer unlike any other in the world, possibly the forerunner of a whole new generation of super-computers, is in existence in a lab on the University of Waterloo campus. It is the brainchild of Dr. Neil Ostlund, a professor in the computer science department, and his fellow researchers. They have put together the new machine with equipment valued at close to a quarter of a million dollars, which Ostlund has received from the Intel Corporation. The Ostlund super-computer is a "prototype" model, used basically as a research instrument. The computer, which is called Waterloop V2/64, is a "high performance multiple processor." Its outstanding characteristic is that it consists of many (64) small, central processing units rather than one large one; traditional architecture for high speed mainframe computers involves only one large CPU. The new computer is said to be the equivalent of 10 VAX 11 computers. Ostlund's 64 CPU's are linked closely together in what he calls a "systolic loop" system; that is, data pulses from microprocessor to microprocessor within the system much as the contraction of the heart causes blood to pulse through the body in the human circulatory system.

# for your information

**Viewing Interval Programming (VIP)**, which allows the consumer to program the television to turn on and off automatically, or block out channels for up to a full week, is being introduced on two new Trinitron® TV's from Sony of Canada's TV and Consumer Video Division. This may be an especially attractive benefit for parents who want to prevent their children from viewing certain programs. The new VIP is featured in one of Sony's new 28-inch colour console models (KV-2675R) and the deluxe 20-inch model, (KV-1975R).

**Electronic Time Switch**

An economical single-channel time switch, featuring an easy-to-read LCD digital display has been introduced by Davis Controls Ltd., P.O. Box 160, Islington, Ont. M9A 4X2 (416)233-3211. The

Arrow/Cesco Electronics Ltd. announces the availability of the Motorola MC68020 to the Canadian marketplace. The MC68020, an advanced high performance 32-bit microprocessor device, uses a 2 micron HCMOS process utilizing 200,000 transistors integrated onto a 375 x 350 mil die, and is placed in a 114 lead pin grid array package. The MC68020 contains full 32-bit address and data busses with additional addressing modes to further support high-level language development.

compact and light-weight unit can be panel, wall or DIN rail mounted, and is ideally suited for controlling on/off times in industrial commercial and HVAC applications. Programming is fast and simple using clearly marked pushbuttons. Up to 10 individual programs can be stored in the unit's memory, with each program consisting of a switch-on time, switch-off time, and the day or days of the week when the switching is to take place. All information is displayed during programming.

The LCD display provides continuous monitoring of clock time, day of the week and switching status. A built-in rechargeable battery maintains off functions during loss of power.


Circle No. 36 on Reader Service Card.

## THE BRUNELLE Commander —SERIES—

Providing Sine, triangle, square, pulse and ramp outputs over the 0.2Hz to 2MHz frequency ranges.

Dependability you can count on. Meets toughest demands!

Model  
3030  
Function  
Generator

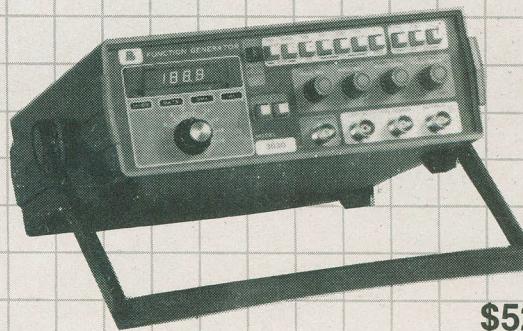

**\$529**

**Featuring**

- Accuracy of  $\pm 5\%$
- VCF input
- Variable DC offset
- TTL or CMOS pulse output

- Measurement range from 0.1Hz to 10MHz
- High input sensitivity of 20mv RMS
- 2 year warranty
- Digital display

BRUNELLE



INSTRUMENTS

BRUNELLE INSTRUMENTS INC.  
826 Belvedere St.  
Sherbrooke, Quebec J1H 4B8  
Tel: 1-819-569-1408 Telex: 05-836266


Mail orders accepted. Send certified cheque or money order. Add \$3.00 for shipping. Quebec residents add 9% P.S.T.

**Available from:**  
• Active Components Stores across Canada  
• Fathom Atlantic, Dartmouth, Nova Scotia

Circle No. 10 on Reader Service Card



for your information

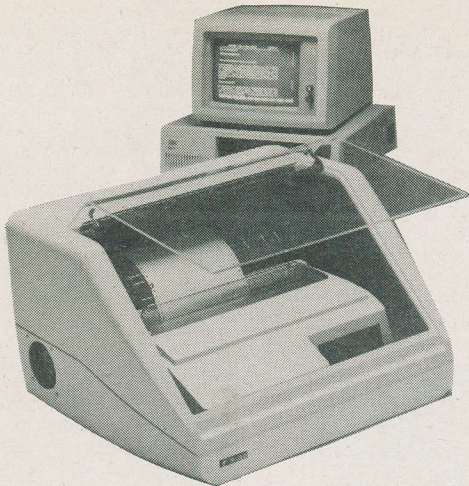


### Acoustical Covers

Trigild Limited of Mississauga, Ontario has announced the introduction of a new line of sound control enclosures designed to keep noisy computer printers quiet. The new "Special Edition Series" of Acousticovers are injection molded of Structural Foam. Use of this material has enabled Trigild to increase product efficiency, in some instances reducing printer noise by up to 90%. At the same time, Trigild has created a

design that is compatible with today's microcomputer products. Special Edition Acousticovers are available to fit most popular dot matrix and letter quality printers. For more information, contact Ole Pedersen, Trigild Limited, 5195 Tomken Road, Mississauga, Ontario, Canada L4W 1P1. Telephone (416)624-5037, Telex: 06-960193.

Circle No. 41 on Reader Service Card.

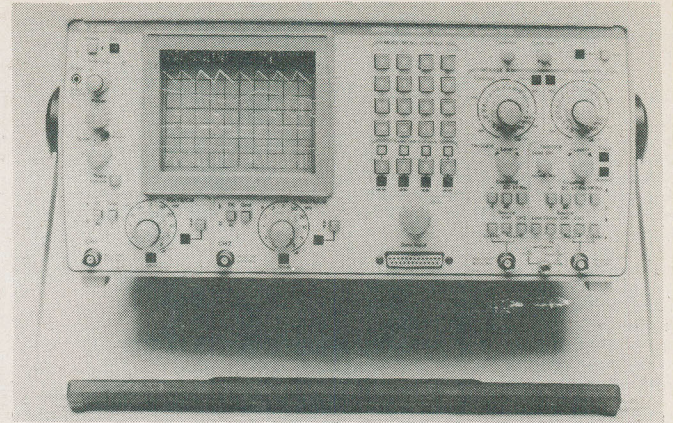

### 100 MHz Digital Scope

An intelligent and powerful 100 MHz digital storage oscilloscope, featuring internal waveform processing and the ability to operate in either non-storage or storage mode, is now available in Canada from the Electronic Instruments & Systems Division of Allan Crawford Associates Ltd., 6503 Northam Dr., Mississauga, Ont. (416)678-1500. The dual-trace Gould model 5110 can acquire and display two waveforms simultaneously for precise and repeatable

time comparison measurements or accurate waveform characterization. Comprehensive automatic calculation capabilities, such as rise time, period and peak-to-peak values, provide rapid and accurate answers at the push of a button or under program control. The 5110 has an 8-bit digitizer for better than 0.4% vertical resolution and two 1024 byte memories. Comprehensive front panel keypad allows for direct selection of panel setups, calculation modes, and memory modes.

Circle No. 40 on Reader Service Card.

## PROBES FOR SALE

FROM THE BEST SOURCE FOR OSCILLOSCOPE PROBES  
AND DMM/VOM TEST LEAD SETS.

- Low cost
- High Quality
- Excellent Performance
- Slender, Flexible Cable
- Wide Range of Choice
- Switchable X1 and X10 Attenuation Factor
- 100 MHz Bandwidth

**MODEL SP100**  
**\$50<sup>10</sup>**

**BCS**  
ELECTRONICS  
LIMITED

980 Alness St. Unit 7,  
Downsview, Ontario,  
M3J 2S2  
(416) 661-5585  
TELEX 065-28109

**Your Probe Specialists**

Coline Canadian Sales & Stocking Source

Store Hours: Monday to Friday 9:00 am to 5:00 pm,  
Saturday 10:00 am to 1:00 pm.

An enhanced release of Digital Research's CP/M™ operating system that takes full advantage of the keyboard and memory of the QX-10 Business Computer, has been introduced by Epson Canada. Version B 2.20 of the CP/M-80 operating system ("B-release") permits QX-10 users to access an expanded library of powerful CP/M-based software programs titled the "Executive Tool Kit." In addition, Version B-release provides software developers with broad opportunities to produce powerful new software packages for the QX-10. Among the new software packages for the QX-10 that take advantage of B-release's features, are Micropro's WordStar 3.3™, SpellStar™, MailMerge™, Change Labs MicroPlan™, GraphPlan™, and Aston-Tate's d-Base II™. The new operating system consists of the standard CP/M file manager and console command modules augmented by a customized BIOS (Basic Input/output System) module that uses all of the QX-10's 256K bytes of memory and the unique human-engineered (HASIC) keyboard. B-release allows the CP/M software packages to make use of the QX-10's special basic English command keys, which include STOP, UNDO, INSERT, PRIOR/NEXT PAGE and BOLD/ITALIC print styles. This new operating system also permits users to take advantage of all the features offered by the Epson line of dot matrix printers.



# Product Mart *Where Buyers Find Sellers*

**AMAZING** Scientific and Electronic Devices for the Hobbyist and Serious Experimenter. Handheld Lasers, Phasers, High Voltage, Micro transmitters, Security, Surveillance, Psychonic and much more. Catalogue \$1.00. Mail order only. **DUKER ENTERPRISES**, 8307 — 160 Street Edmonton, Alberta T5R 2H2.

**MUSIC SYNTHESIZER** & accessories for your Apple — digital oscillator, interface card; hardware & software compatible with Soundchaser & alphaSyntauri systems. 61N keyboards from \$325. Write for list. Dealer inquiries invited. **CLASSIC ORGAN CO.**, 300-12 Don Park Road, Markham, Ont. L3R 3A1 (416) 475-1263.

**SATELLITE-TV** disk (Apple) with data and information programs, azimuth and elevation calculator. \$19.95 cheque or money-order. **GILBERT ENTERPRISES**, 63 Weston St., London, Ont., N6C 1R4.

**ELECTRONIC** Parts and Supplies for Industry, students and Dealer trade. We can special order. Stereo components, satellite supplies, television, V.H.F. Radios and all antennae. **G.W. COLOR-TRONICS LTD.** 616 Cheadle Street, West Swift Current, Sask. S9H 3X4 (306) 773-3672.

**TEST-EQUIPMENT.** High quality reconditioned Tektronix, H.P., scopes, generators, analysers, etc. \$50 ± \$5,000. Calibrated to original specifications. Free illustrated catalogue **ALDONICS**, Box 2980, Dept. ETI, Ottawa, "D", Ont. K1P 5W9.

**T.V./STEREO INTERFACE** Improves T.V. sound by playing it through the stereo. Provides voltage isolation. For a complete package, send \$29.95 plus \$2.50 shipping and handling to: **P.B. ELECTRONICS**, P.O. Box 4176, Station 'C', Ottawa, Ontario K1Y 4P3

**THE** bottom line on Software: Super Software has it! First and foremost. For business, education, personal productivity and games for the computer. Plus the accessories **SUPER SOFTWARE INC.** 103-4600 #3 Road, Richmond, B.C. V6X 2C2 (604) 278-7638.

**EFSTONSCIENCE**, 3350 Dufferin St., Toronto, Ont. M5A 3A4 (416) 787-4581. Jenson Tools, Kits, Cases, Hard to find electronic instruments, Edmund Scientific Telescopes, Microscopes, Scientific living specialties. Catalogue available.

**DISK ALIGNMENT TROUBLE? DISK-CHECK™** all-in-one alignment meter can also be used for diskette quality evaluation. Displays actual amplitude of disk signal. No software required. Adjust Radial Alignment, check Hysteresis, Write function, Noise level. Includes strobe light for disk Speed adjustment. Can be hooked up during normal disk operation. Complete instructions included. Some disassembly required, may void warranty. No additional equipment required. Supports most disk drives: APPLE Disk II, Commodore 1541, Osborne I, IBM PC Tandon, TRS80 MPI, Shugart, TEAC. Only \$129.95. **VERBATIM 5-1/4"** Cleaning kit jacket and two throw-away cleaning disks: \$10.95. Ten replacement throw-away cleaning disks: \$17.95. Also, **SAMS COMPUTERFACTS™** series covers every circuit, chip and control with full schematics, disassembly instructions, logic charts, troubleshooting hints... Specify Apple II & II+ or Commodore 64 or VIC-20 or TI99-4A, only \$26.95. Order now from **ADDAX MICRO INC.** 208 Taschereau, Greenfield Park, Quebec, J4V-2H4, (514) 465-6056. Money order, Visa or Master Card (don't forget card expiry date). Add \$4.00 postage and handling, Quebec residents add 9% sales tax.

**Z80 MICRO-CONTROLLER**...parallel I/O, keypad commands. Complete plans, ROM monitor, \$39.95. Source & doc on 8" SSSD disk, use with Z80-64k CPM-2.2 computer, \$25.95. **DISCOUNTED**, ch/m.o. Build-N-Learn how controller hdwe/sfwe controls machines/robots... order today, **CONTROLLER**, P.O. Box 3775, Station B, Winnipeg, Manitoba Canada R2W 3R6.

**SPECIAL KITS** — (1) Rumble filters \$13.52, (2) Mag/Cer preamp \$8.15, (3) 741 amp \$14.30, (4) variable timer \$18.51, (5) loudness control \$11.23, (6) simulated stereo \$17.75, (7) dice-LED \$14.40, (8) scratch filter \$18.33, (9) 3 channel mixer \$13.92, (10) doorbell \$32.25. Schematic & instructions included. Free sample parts pak w/order. New parts price list available. Incl \$0.60 for mailing. Add 10% P&H, Ont. Res. add 7% P.S.T. Send cheque / Moneyorder to **ELECTRON COMPUTERS**, P.O. Box 613, Stn. 'U', Toronto, Ontario. M8Z 5X9. (416) 259-8709.


**AUTODIAL-CARD** for Apple II+/IIe. Features pulse dialing and software supplied on diskette. Plugs into telephone jack or your modem. \$49.95. **VISA/MASTER-CARD. W.H.S. ENTERPRISES**, 34 Epsom Cres., Winnipeg, Manitoba, R3R 0X2,

**SOFTWARE**, 100 question Z80 assembly language quiz. For study, review or same. On 8" SSSD disk, use on Z80-64k CPM-2, 2 computer, \$25.95. **DISCOUNTED**, ch/m.o. **Z-QUIZ**, P.O. Box 3775, Stn. B, Winnipeg, Manitoba Canada R2W 3R6.

**ATTENTION** Electronic Hobbyist's Capacitors, Resistors, P.C. Boards, etc. send \$1.00 for catalog to **A.G.M. ENTERPRISES**, 2203, Beaconsfield, suite 4, Montreal H4A 2G9.

**R.A.E. INDUSTRIAL ELECTRONICS LTD.** Distributors of electronic parts and equipment, serving the following locations: Vancouver B.C. (604)291-8866; Edmonton AB (403)451-4001; Saskatoon SK (306)652-6424; Winnipeg MB (204)786-8401; Toronto, Ont (416)736-1750; Dartmouth N.S. (902)465-2350; Moncton, N.B. (506)855-2200; Head office 3455 Gardner Court, Burnaby B.C., V5G 4J7 (604)291-8866.
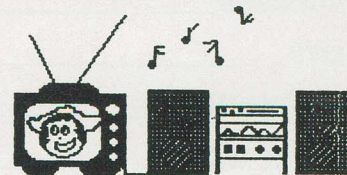
## IMPROVE THE SOUND QUALITY OF YOUR TELEVISION !!



**T.V./STEREO INTERFACE** improves T.V. sound by playing it through the stereo. Provides voltage isolation. For a complete package, send \$29.95 plus \$2.50 shipping and handling to: **P.B. ELECTRONICS** P.O. BOX 4176, STATION 'C', OTTAWA, ONTARIO, K1Y 4P3

\* Ontario residents please add 7% P.S.T. (\$2.10)

Advertising in the **Product Mart** section allows you to reach over 30,000 Canadian readers nation wide for \$1.00 per word (minimum 25 words). Please contact us for further details on the various sizes and styles available. Moorshead Publications, Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1, (416) 423-3262



# Product Mart *Where Buyers Find Sellers*

## DID YOU KNOW?

That HOBBILT ELECTRONICS is the only truly Canadian company devoted to serving hobbyists and student?

Did you know that HOBBILT gives student discounts all year round whether in store or by mail?

Did you know that HOBBILT doesn't offer wholesale prices?

We're just better priced!

Did you know that \$1.00 and your name and address gets you the new 1984 catalogue? Well, now you know!

**HOBBILT ELECTRONICS**, 7454 Langelier, St. Leonard (Mtl), Quebec H1S 3B7

**TRS-80** Color computer owners: PBH printer interface \$124.95, Slic-stic \$74.95 P+H = \$2.00. Full warranty: **ISLAND CUSTOM ELECTRONICS**, Box 2203, Charlottetown, P.E.I. C1A 8B9. (Catalogue \$1.00).

**NEED** Computer Information? Great selection of books and magazines, knowledgeable service, supplies. Mail, telephone, special orders welcome. **MICA COMPUTER BOOKS** 3727 West 10th, Vancouver, B.C. (604)222-2221.

**C64 RS232 INTERFACE** \$49.95. Complete with two cables and connectors to interface a printer and a modem. Modem listing included. C64 assembler \$9. 95. disk version \$14.95. VIC-20 clearance 8k RAM \$49.95. RAM/EPROM board \$6.95. Free flyer. **CPM**, Box 123, Waterloo, Ont. N2J 3Z9.

**CARDINAL INDUSTRIAL ELECTRONICS** Canada's foremost electronic supply house. Featuring quality product lines in every category of electronics. Edmonton AB (403) 483-6266; Calgary, AB (403) 259-6817; Saskatoon, SK (306) 934-3443.

**ELECTRONIC Parts and Supplies** for industry, Students and Dealer Trade. We can special order. Stereo Components, Satellite Supplies, Television, V.H.F. Radios and all Antennae. **G.W. COLOR-TRONICS LTD.**, 616 Cheadle Street, West. Swift Current, Sask., S9H 3X4 Tel: (306)773-3672.

**1984 WORLD RADIO-TV HANDBOOKS** \$23 + \$2 S&H, WSI 1984 Catalogue \$2.00, **WSI RADIO**, Box 400, Kitchener, Ontario N2G 3Y9.



LET'S  
SEE  
YOU  
DO  
IT!



**PARTICIPATION** ©

# Product Mart *Where Buyers Find Sellers*

NAME \_\_\_\_\_ COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ PROVINCE \_\_\_\_\_

POSTAL CODE \_\_\_\_\_ TELEPHONE \_\_\_\_\_

NO. OF WORDS \_\_\_\_\_ AMOUNT ENCLOSED \_\_\_\_\_

Please print the following in the next available issue of ☐ **ELECTRONICS TODAY**, ☐ **COMPUTING NOW**,  
or ☐ **BOTH**. My cheque is enclosed. SIGNATURE \_\_\_\_\_


NOTE: A 3 line heading can be added to your advertisement for \$30. Also, the whole advertisement can be reversed for effective presentation also for \$30.



# OSCILLOSCOPES!
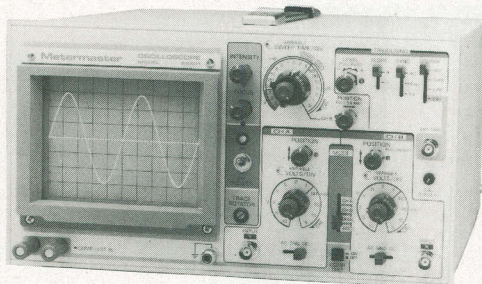
## The Best Buys Available

**Model 65601**  
Dual Trace Bench/Portable Scope




**\$ 695<sup>00</sup>**

Probes & FST  
included

Featuring at no extra cost . . . . . 'The Component Tester'

- 20 MHz (–3dB) Bandwidth
- 6" CRT Display
- Fully Automatic Triggering
- Trace Rotator
- 5 mV Vertical Sensitivity
- HF Rejection

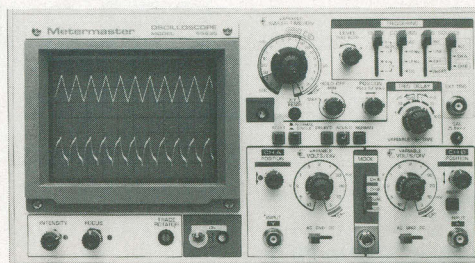**Model 65635**  
Dual Trace Bench/Portable Scope



**\$ 895<sup>00</sup>**

Probes & FST  
included

- 35 MHz (–3dB) Bandwidth
- Delayed Sweep (selectable)
- Single Sweep (selectable)
- 6" CRT Display
- 1 mV Optimal Sensitivity
- X-Y or X-Y-Z Operation
- 120V AC Line Operation
- x5 Sweep Magnifier

# MULTIMETERS!


## Go for Quality --- Go for The Best Value

**Models 78020, 78021, 78022**

- AUTO ZERO
- AUTO POLARITY
- 3½ DIGIT LCD
- FULL OVERLOAD PROTECTION ON ALL RANGES
- RECESSED – SAFETY DESIGNED INPUT TERMINALS


Supplied with:

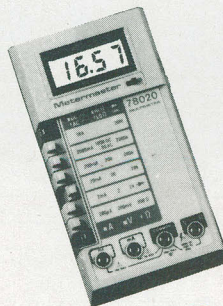- 28 Page Operating and Maintenance Manual
- Calibration Certificate Traceable to NRC
- Schematic with complete Parts Listing
- Safety Test Leads
- One-year Warranty



**\$ 139<sup>00</sup>\***

- ◆ ±0.1% DC
- ◆ 2000 hrs Bat. life

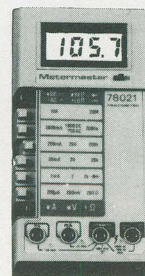

**\$ 99<sup>00</sup>\***

- ◆ ±0.25% DC
- ◆ 10 Amps AC+DC
- ◆ 200 hrs Bat. life



**\$ 89<sup>00</sup>\***

- ◆ ±0.25% DC
- ◆ 200 hrs Bat. life

\* F.S.T. extra

### Metermaster

A Div. of R.H. NICHOLS CO. LTD.

Head Office: 80 Vinyl Court, Woodbridge, Ontario L4L 4A3



5% Discount for Cash,  
Certified Cheque, or Money Order  
DEALER INQUIRIES INVITED

All prices F.O.B.  
Downsview, Ontario  
subject to change with-  
out notice. P.S.T. extra  
where applicable.

TORONTO (416) 851-8871 • MONTREAL (514) 337-0425 • EDMONTON (403) 432-7746 • OTTAWA (613) 238-7007

Circle No. 22 on Reader Service Card.



# Tek's best-selling 60 MHz scopes: Now 25 ways better for not a penny more!

**Now Tek has improved its 2213/2215 scopes with brighter displays. Greater accuracy. And more sensitive triggering. At no increase in price.**

The 60 MHz 2213 and dual time base 2215 have been the most popular scopes in Tektronix history. Now, Tek introduces an "A" Series update with more than 25 specification and feature enhancements—things you have asked for such as single sweep—all included at no added cost.

**A brighter display and new vertical amplifier design provides sharp, crisp traces.**

That makes the 2213A/2215A a prime candidate for tasks like TV troubleshooting and testing, where fast sweeps are typical.

**New features include 10 MHz bandwidth limit switch, separate A/B dual intensity controls (2215A only), and power-on light:** additions customers have suggested for

giving these scopes the final measure of convenience.


**Triggering, sweep accuracy, CMRR and many more major specifications are better than ever.** Check the performance chart: not bad for scopes already considered the leaders in their class!

**The Price: Still \$1902\* for the 2213A and \$2298\* for the 2215A. Or, step up to the 100 MHz 2235 for just \$2718\*. Prices include two 10X probes, 15-day return policy, world-wide service back-up and comprehensive 3 year**

**warranty. Ask about our extended warranty.**

**Talk to our technical experts.**

Vancouver	604-438-4321
Calgary	403-230-1836
Edmonton	403-434-9466
Winnipeg	204-632-4447
Toronto	416-675-3865
Ottawa	613-225-2850
Montreal	514-697-5340
Dartmouth	902-469-9476

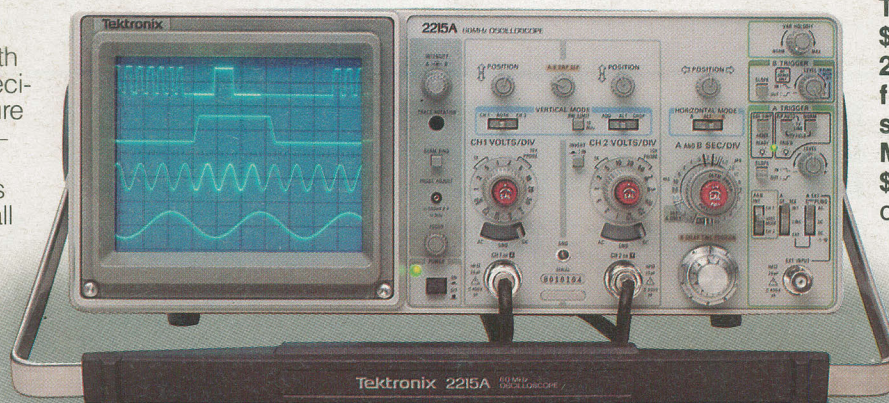

Specification enhancement	2213/2215 "A" Series	2213/2215
CRT brightness	14 kv accel. potential	10 kv accel. potential
Vertical accuracy	3%, 0° to 50°C	3%, +20° to 30°C
Chop rate	500 kHz	250 kHz
Input capacitance	20 pF	30 pF
CMRR	10 to 1 at 25 MHz	10 to 1 at 10 MHz
Channel isolation	100:1 at 25 MHz	Not specified
A Trigger sensitivity (int)	0.3 div at 5 MHz	0.4 div at 2 MHz
TV triggering	1.0 div compos. sync	2.0 div compos. sync
Sweep accuracy (in 10X)	4%, 15° to 35°C	5%, 20° to 30°C
Delay jitter	20,000 to 1 (2215A) 10,000 to 1 (2213A)	10,000 to 1 (2215) 5,000 to 1 (2213)
Holdoff Range	10:1	4:1

\*Duty and F.S.T. included.  
Prices subject to change without notice.  
All scopes are UL listed and CSA approved. 3-year warranty includes CRT and applies to 2000 family oscilloscopes purchased after 1/1/83

**Tektronix Canada Inc.**  
P.O. Box 6500  
Barrie, Ontario  
L4M 4V3

**Tektronix**  
COMMITTED TO EXCELLENCE